 


Differential Amplifier



Differential Amplifier

1. The differential amplifier amplifies the difference between two input voltage signals
2. If V_1 & V_2 are two input signals wrt ground & V_o is the output voltage then

The ideal output voltage given as

$$V_o \propto (V_1 - V_2) \text{ Or } V_o = A_{vol}(V_1 - V_2)$$

A_{vol} is called the **open loop voltage Gain**

Generally in ideal case:

$$\text{if } V_1 = V_2 \quad (V_1 - V_2) = 0$$

$$\text{if } V_1 \neq V_2 \quad (V_1 - V_2) \neq 0$$

Differential Amplifier

But Practically speak:

Differential mode input voltage as $V_d = V_1 - V_2$ (Signal of Interest)

Common mode signal component

(Typically reference level or noise level, not desired)

$$v_{cm} = \frac{v_1 + v_2}{2}$$

The circuit which amplifies the difference between the two input signals is called **differential Amplifier**

We can write the output voltage in the general form

$$V_o = A_d V_d + A_{cm} V_{cm}$$

Performance parameters:

The ability of a differential amplifier to reject a common-mode signal is described in terms of the common-mode rejection ratio (CMRR). The CMRR is a figure of merit for the diff-amp and is defined as

$$\text{CMRR} = \left| \frac{A_d}{A_{cm}} \right|$$

For an ideal diff-amp, $A_{cm} = 0$ and $\text{CMRR} = \infty$. Usually, the CMRR is expressed in decibels, as follows:

$$\text{CMRR}_{\text{dB}} = 20 \log_{10} \left| \frac{A_d}{A_{cm}} \right|$$

Applications

- Basic building block in many Analog circuits
- High speed switching circuits
- Operational Amplifier-Many electronic Applications
- Integrated circuits

Essential Formulas

Region	NMOS	PMOS
Saturation	$v_{DS} \geq v_{DS}(\text{sat})$ $i_D = K_n [v_{GS} - V_{TN}]^2$	$v_{SD} \geq v_{SD}(\text{sat})$ $i_D = K_p [v_{SG} + V_{TP}]^2$
Transition Point	$v_{DS}(\text{sat}) = v_{GS} - V_{TN}$	$v_{SD}(\text{sat}) = v_{SG} + V_{TP}$


$$K_n = \frac{\mu_n C_{ox} W}{2L} = \frac{k'_n}{2} \cdot \frac{W}{L}$$

$$K_p = \frac{\mu_p C_{ox} W}{2L} = \frac{k'_p}{2} \cdot \frac{W}{L}$$

$$C_{ox} = \epsilon_{ox} / t_{ox}$$

μ_n, μ_p	Mobility of electrons, holes
ϵ_{ox}	Oxide permittivity
t_{ox}	Oxide thickness
W, L	Channel Width, Length
$k'_n = \mu_n C_{ox}$ $k'_p = \mu_p C_{ox}$	Process conduction parameter (provided by manufacturer)

 MOSFET Differential Amplifier (DC Analysis)



with matched transistors $M1$ and $M2$ biased with a constant current I_Q .

We assume that $M1$ and $M2$ are always biased in the saturation region.

Two matched MOS transistors ($M1$ and $M2$) are joined
Same Technology: V_{th}, L, W .


Same: μ, C_{ox} , and k'

Two circuits joints symmetrically

Same Load R_D

Source Terminals Joined

Equal gate bias (v_{G1}, v_{G2}) (Zero)

 

Device biased using constant current source I_Q

DC Transfer characteristics

Assume M1 and M2 are matched and neglecting their output resistances

$$i_{D1} = K_n (v_{GS1} - V_{TN})^2$$
$$i_{D2} = K_n (v_{GS2} - V_{TN})^2$$

Taking square roots and subtracting

$$\sqrt{i_{D1}} - \sqrt{i_{D2}} = \sqrt{K_n} (v_{GS1} - v_{GS2}) = \sqrt{K_n} \cdot v_d$$

where

$$v_d = v_{G1} - v_{G2} = v_{GS1} - v_{GS2}$$

If $v_d > 0$,

then $v_{G1} > v_{G2}$ and $v_{GS1} > v_{GS2}$ which implies that $i_{D1} > i_{D2}$

$$i_{D1} + i_{D2} = I_Q$$

$$\left(\sqrt{i_{D1}} - \sqrt{I_Q - i_{D1}} \right)^2 = K_n v_d^2$$

$$\left(\sqrt{i_{D1}} \right)^2 + \left(\sqrt{I_Q - i_{D1}} \right)^2 - 2\sqrt{i_{D1}} \sqrt{I_Q - i_{D1}} = K_n v_d^2$$

$$i_{D1} + I_Q - i_{D1} - 2\sqrt{i_{D1}} \sqrt{I_Q - i_{D1}} = K_n v_d^2$$

$$I_Q - K_n v_d^2 = 2\sqrt{i_{D1}} \left(I_Q - i_{D1} \right)$$

$$\frac{1}{2} \left(I_Q - K_n v_d^2 \right) = \sqrt{i_{D1}} \left(I_Q - i_{D1} \right)$$

Taking square on both sides

$$\left(\frac{1}{2} \left(I_Q - K_n v_d^2 \right) \right)^2 = \left(\sqrt{i_{D1} \left(I_Q - i_{D1} \right)} \right)^2$$

$$i_{D1} \left(I_Q - i_{D1} \right) = \frac{1}{4} \left(I_Q - K_n v_d^2 \right)^2$$

$$i_{D1} I_Q - i_{D1}^2 = \frac{1}{4} \left(I_Q - K_n v_d^2 \right)^2$$

$$i_{D1}^2 - i_{D1} I_Q + \frac{1}{4} \left(I_Q - K_n v_d^2 \right)^2 = 0$$

Applying the quadratic formula, rearranging terms, and noting that $i_{D1} > I_Q/2$ and $v_d > 0$, we obtain

Applying the quadratic formula, rearranging terms, and noting that $i_{D1} > I_Q/2$ and $v_d > 0$, we obtain

$$i_{D1} = \frac{I_Q}{2} + \sqrt{\frac{K_n I_Q}{2}} \cdot v_d \sqrt{1 - \left(\frac{K_n}{2I_Q} \right) v_d^2}$$

Using Eq.(5)

$$i_{D2} = \frac{I_Q}{2} - \sqrt{\frac{K_n I_Q}{2}} \cdot v_d \sqrt{1 - \left(\frac{K_n}{2I_Q} \right) v_d^2}$$


$$\frac{-b \pm \sqrt{b^2 - 4ac}}{2a}$$

The normalized drain currents are


$$\frac{i_{D1}}{I_Q} = \frac{1}{2} + \sqrt{\frac{K_n}{2I_Q}} \cdot v_d \sqrt{1 - \left(\frac{K_n}{2I_Q}\right) v_d^2}$$

$$\frac{i_{D2}}{I_Q} = \frac{1}{2} - \sqrt{\frac{K_n}{2I_Q}} \cdot v_d \sqrt{1 - \left(\frac{K_n}{2I_Q}\right) v_d^2}$$

 These equations describe the dc transfer characteristics for this circuit. They are plotted in Figure as a function of a normalized differential input voltage $v_d/\sqrt{(2I_Q/K_n)}$



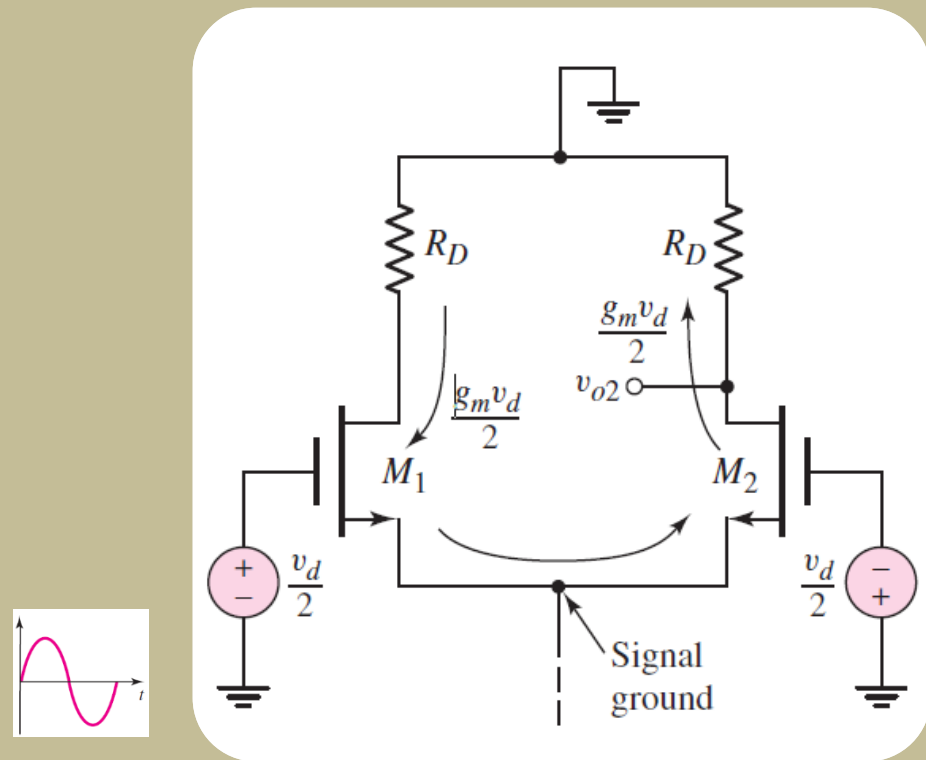
The ac equivalent circuit of the diff-amp configuration, showing only the differential voltage and **signal currents** as a function of the transistor transconductance g_m .



one-sided output voltage at v_{o2} , as follows



$$\begin{aligned}
 g_m &= 2\sqrt{K_n I_{DQ}} \\
 &= 2\sqrt{K_n \frac{I_Q}{2}} \\
 &= \sqrt{2}\sqrt{2}\sqrt{K_n \frac{I_Q}{2}} = \sqrt{2K_n I_Q}
 \end{aligned}$$
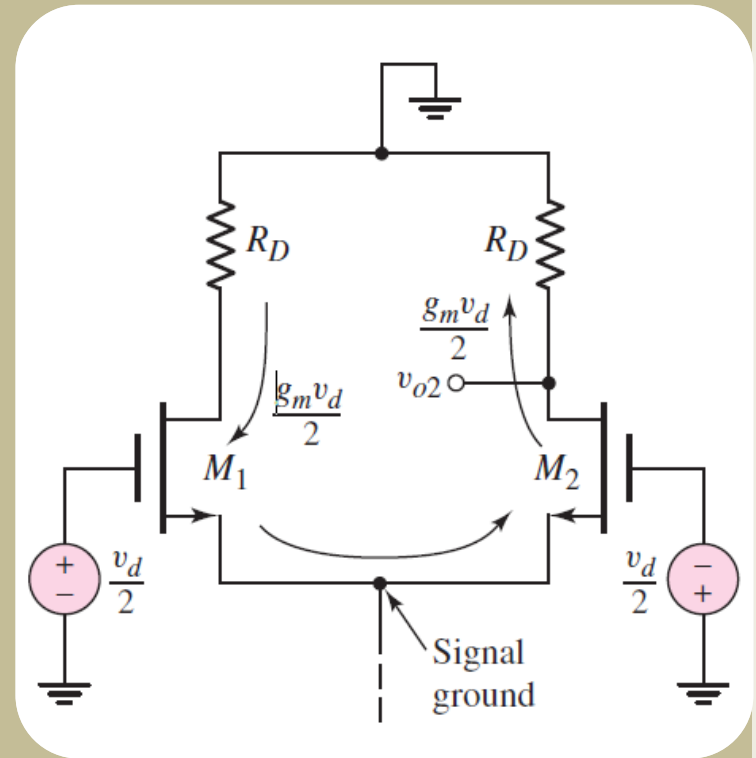
$$v_{o2} \equiv v_o = + \frac{g_m v_d}{2} R_D \xrightarrow{\sqrt{2}\sqrt{2}}$$




Then the differential voltage gain is
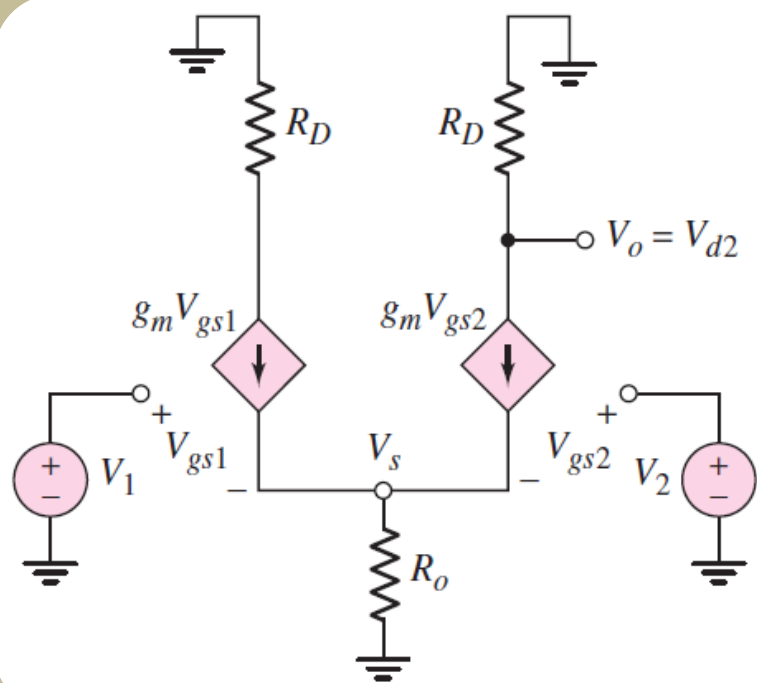 
$$A_d = \frac{v_o}{v_d} = \frac{g_m R_D}{2} = \sqrt{\frac{K_n I_Q}{2}} \cdot R_D$$



Small-Signal Equivalent Circuit Analysis

 

- We assume the transistors are matched, with $\lambda = 0$ for each transistor,
- CMRR
- The constant-current source is represented by a finite output resistance R_o .
- Transistors are biased at the same quiescent current, and $g_{m1} = g_{m2} \equiv g_m$.

$$V_1 = V_{cm} + \frac{V_d}{2}$$

$$V_2 = V_{cm} - \frac{V_d}{2}$$

$$V_{cm} = \frac{V_1 + V_2}{2}$$

$$2V_{cm} = V_1 + V_2$$

$$V_d = V_1 - V_2$$

from above equations

Writing a KCL equation at node V_s , we have

$$g_m V_{gs1} + g_m V_{gs2} = \frac{V_s}{R_o} \quad 3$$

From the circuit, we see that $V_{gs1} = V_1 - V_s$ and $V_{gs2} = V_2 - V_s$

then becomes

$$g_m (V_1 + V_2 - 2V_s) = \frac{V_s}{R_o} \quad 4$$

$$g_m (V_1 + V_2 - 2V_s) = \frac{V_s}{R_o}$$

$$g_m V_1 + g_m V_2 - 2g_m V_s = \frac{V_s}{R_o}$$

$$g_m (V_1 + V_2) = \frac{V_s}{R_o} + 2g_m V_s$$

$$V_s = \frac{g_m (V_1 + V_2)}{g_m \left(2 + \frac{1}{g_m R_o} \right)} = \frac{V_1 + V_2}{2 + \frac{1}{g_m R_o}}$$

For a one-sided output at the drain of M_2 , we have

$$V_o = V_{d2} = -(g_m V_{gs2})R_D = -(g_m R_D)(V_2 - V_s)$$

$$V_o = V_{d2} = -(g_m R_D) \left[V_2 - \frac{V_1 + V_2}{2 + \frac{1}{g_m R_o}} \right]$$

$$V_o = V_{d2} = \frac{-(g_m R_D) \left[V_2 \left[2 + \frac{1}{g_m R_o} \right] - (V_1 + V_2) \right]}{2 + \frac{1}{g_m R_o}} = \frac{-(g_m R_D) \left[V_2 + \frac{V_2}{g_m R_o} - V_1 \right]}{2 + \frac{1}{g_m R_o}}$$

$$V_o = -g_m R_D \left[\frac{V_2 \left(1 + \frac{1}{g_m R_o} \right) - V_1}{2 + \frac{1}{g_m R_o}} \right]$$

$$V_{cm} = \frac{V_1 + V_2}{2}$$

$$2V_{cm} = V_1 + V_2$$

$$V_d = V_1 - V_2$$

from above equations

$$V_1 = V_{cm} + \frac{V_d}{2}$$

$$V_2 = V_{cm} - \frac{V_d}{2}$$

Based on relationships between
input voltages V_1 and V_2 and differential – and common – mode voltages,

$$V_o = V_{d2} = \frac{-(g_m R_D) \left[\left(V_{cm} - \frac{V_d}{2} \right) \left(1 + \frac{1}{g_m R_O} \right) + \frac{V_2}{g_m R_O} - \left(V_{cm} + \frac{V_d}{2} \right) \right]}{2 + \frac{1}{g_m R_O}}$$

WKT :

$$V_o = A_{cm} V_{cm} + A_d V_d$$

Coefficients of A_{cm}

$$V_o = V_{d2} = \frac{-(g_m R_D) \left[V_{cm} \left(1 + \frac{1}{g_m R_O} - 1 \right) \right]}{2 + \frac{1}{g_m R_O}} + A_d V_d$$

$$V_o = A_{cm} V_{cm} + A_d V_d$$

Coefficients of A_{cm}

$$V_o = V_{d2} = \frac{-(g_m R_D) \left[V_{cm} \left(1 + \frac{1}{g_m R_O} - 1 \right) \right]}{2 + \frac{1}{g_m R_O}} + A_d V_d$$

$$V_o = V_{d2} = \frac{\frac{-(g_m R_D)}{g_m R_O} \cdot V_{cm}}{\frac{1 + 2g_m R_O}{g_m R_O}} + A_d V_d = \frac{-(g_m R_D)}{1 + 2g_m R_O} V_{cm} + A_d V_d$$

$$V_o = \frac{g_m R_D}{2} V_d - \frac{g_m R_D}{1 + 2g_m R_o} V_{cm}$$

The transconductance g_m of the MOSFET is

$$g_m = 2\sqrt{K_n I_{DQ}} = \sqrt{2K_n I_Q}$$

Differential-mode gain is

$$A_d = \frac{g_m R_D}{2} = \sqrt{2K_n I_Q} \left(\frac{R_D}{2} \right) = \sqrt{\frac{K_n I_Q}{2}} \cdot R_D$$

Common-mode gain is

$$A_{cm} = \frac{-g_m R_D}{1 + 2g_m R_o} = \frac{-\sqrt{2K_n I_Q} \cdot R_D}{1 + 2\sqrt{2K_n I_Q} \cdot R_o}$$

We again see that for an ideal current source, the common-mode gain is zero since $R_o = \infty$.

The common-mode rejection ratio, $CMRR = |A_d/A_{cm}|$, is found to be

$$A_d = \frac{g_m R_D}{2} = \sqrt{2K_n I_Q} \left(\frac{R_D}{2} \right) = \sqrt{\frac{K_n I_Q}{2}} \cdot R_D$$


CMRR=

$$A_{cm} = \frac{-g_m R_D}{1 + 2g_m R_o} = \frac{-\sqrt{2K_n I_Q} \cdot R_D}{1 + 2\sqrt{2K_n I_Q} \cdot R_o}$$


$$CMRR = \frac{1}{2} \left[1 + 2\sqrt{2K_n I_Q} \cdot R_o \right]$$

The value of CMRR can be increased by increasing the output resistance of the current source. The increase can be accomplished by using a more sophisticated current source circuit, such as the MOSFET cascode current mirror

 
MOSFET differential amplifier with active load



Remember....

 

 
MOSFET differential amplifier with active load



M_1 and M_2 are n – channel devices and form the diff pair biased with I_Q . The load circuit consists of M_3 and M_4 , both p – channel devices, connected in a current – mirror configuration.

A one – sided output v_O is taken from the common drains of M_2 and M_4 .

Assume Common Mode Signal

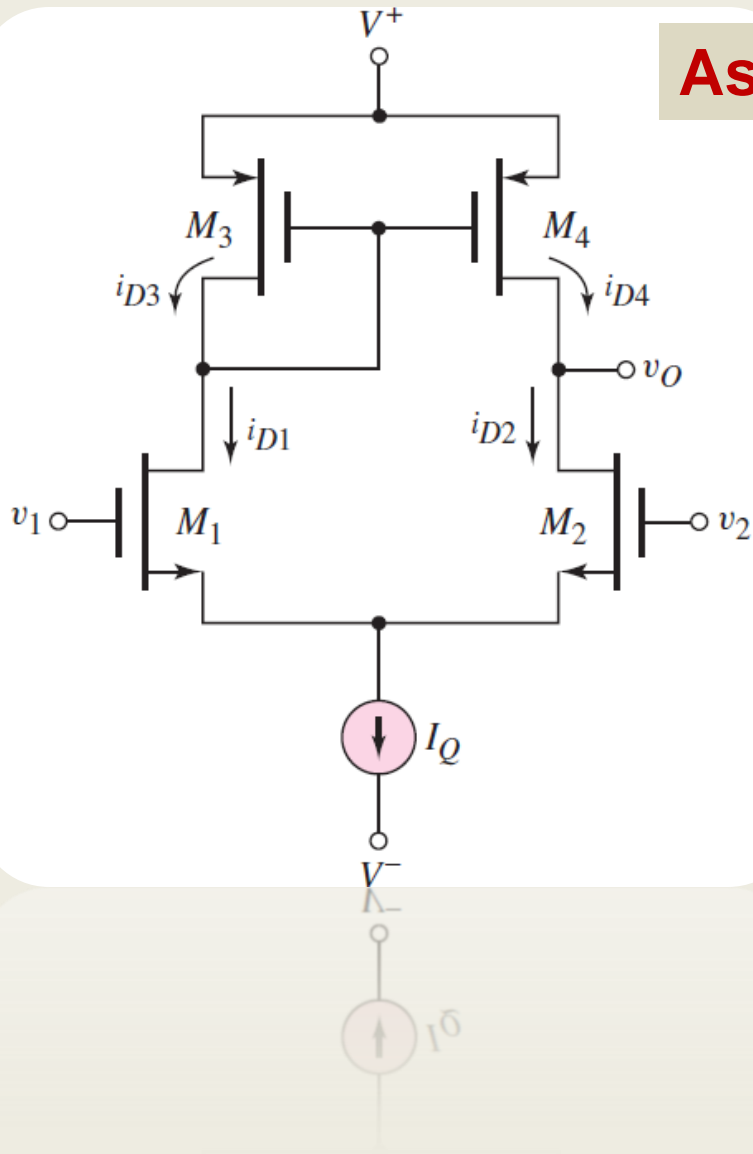

When a common – mode voltage $V_1 = V_2 = V_{CM}$ is applied :
the current I_Q splits evenly
between transistors M_1 and M_2 ,
and $i_{D1} = i_{D2} = I_Q / 2$. •
There are no gate currents,
therefore $i_{D3} = i_{D1}$ and $i_{D4} = i_{D2}$


Assume Difference Mode Signal

If a small diff – mode input voltage $V_d = V_1 - V_2$ is applied, we can write

$$i_{D1} = (I_Q / 2) + i_d$$

$$i_{D2} = (I_Q / 2) - i_d$$

$$i_d = \frac{g_m v_d}{2}$$

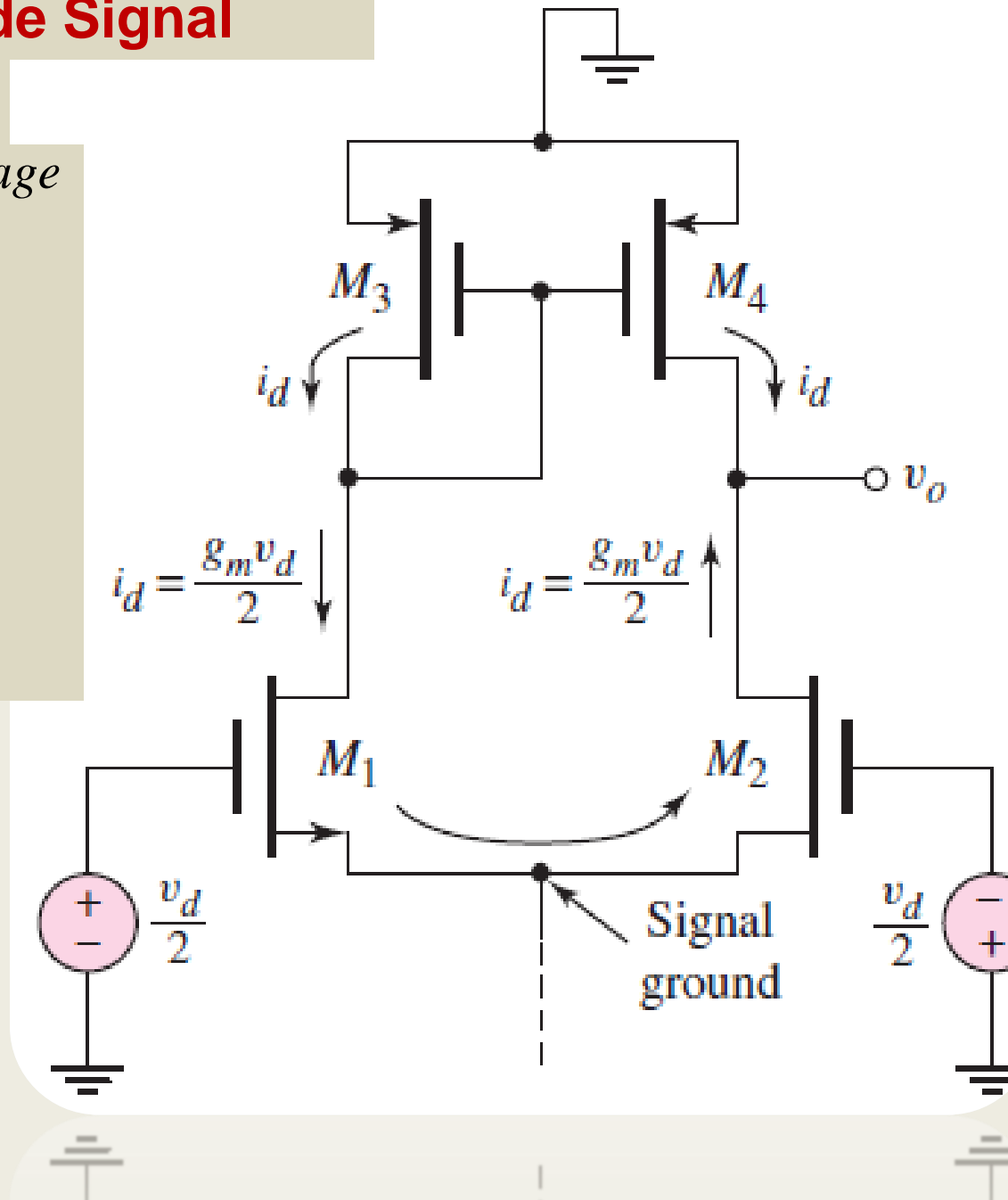


Since M_1 and M_2 are in series,




can be seen that $i_{D3} = i_{D1} = \left(I_Q / 2\right) + i_d$

Finally, the current mirror consisting of

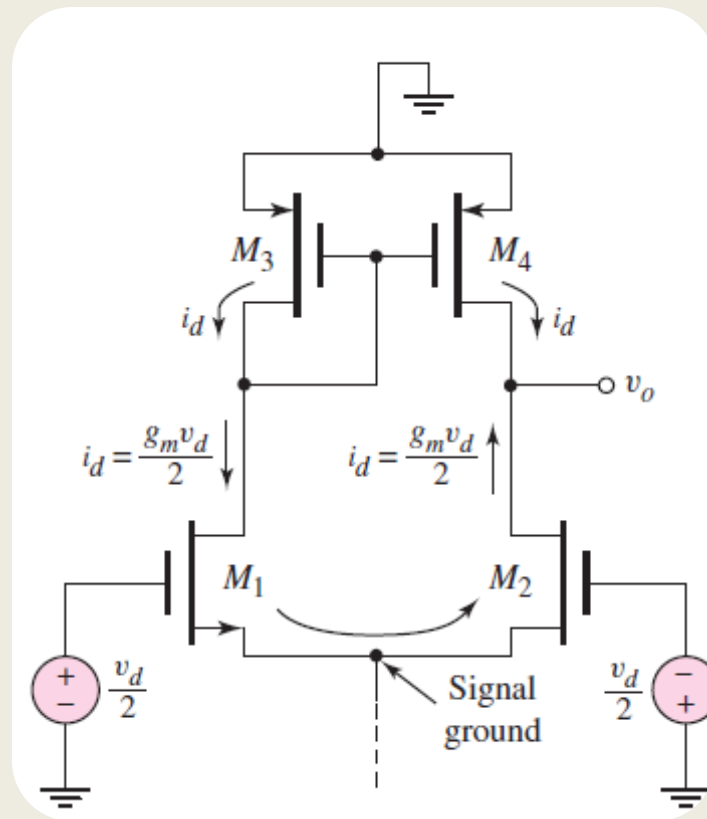M_3 and M_4 produces $i_{D4} = i_{D3} = \left(I_Q / 2\right) + i_d$



Small Signal Equivalent Circuit

  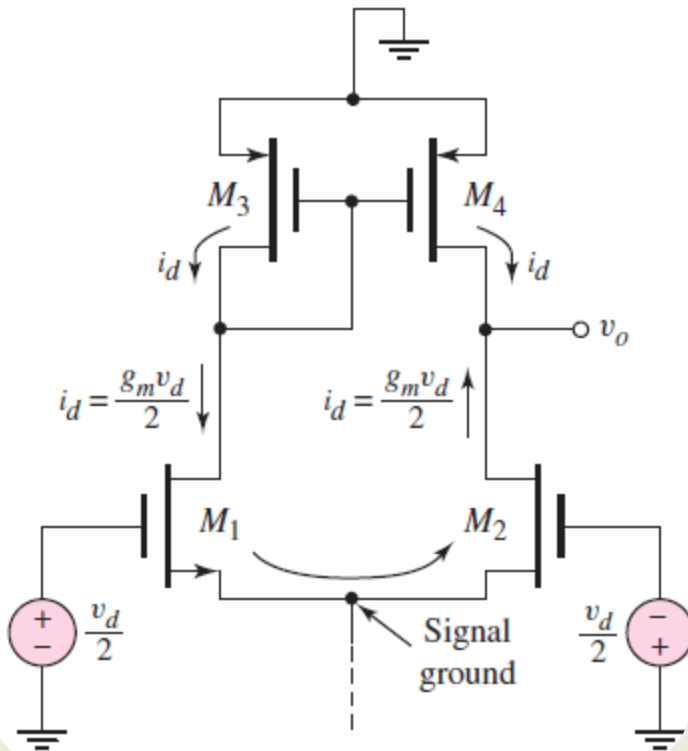

- 1.AC Equivalent Circuit
- 2.Small Signal Equivalent Circuit
- 3.Rearranged.

the Output Voltage is

$$v_o = 2 \left(\frac{g_m v_d}{2} \right) (r_{o2} \parallel r_{o4})$$

and the small-signal diff-mode voltage gain is

$$A_d = \frac{v_o}{v_d} = g_m (r_{o2} \parallel r_{o4})$$

can be rewritten in the form

$$A_d = \frac{g_m}{\frac{1}{r_{o2}} + \frac{1}{r_{o4}}} = \frac{g_m}{g_{o2} + g_{o4}}$$

$$g_m = 2\sqrt{K_n I_D} = \sqrt{2K_n I_Q}$$

$$g_{o2} = \lambda_2 I_{DQ2} = (\lambda_2 I_Q) / 2$$

$$g_{o4} = \lambda_4 I_{DQ4} = (\lambda_4 I_Q) / 2$$

then Equation becomes

$$A_d = \frac{2\sqrt{2K_n I_Q}}{I_Q(\lambda_2 + \lambda_4)} = 2\sqrt{\frac{2K_n}{I_Q}} \cdot \frac{1}{\lambda_2 + \lambda_4}$$

$$\frac{1}{R_o} = \frac{dI_D}{dV_{DS}} = \frac{1}{r_o} = \lambda I_D$$

Where

$$r_o = \frac{1}{g_o} = \frac{1}{\lambda I_D}$$

$$g_o = \lambda I_D$$