

Final Assessment Test (FAT) – November/December 2022

Programme	B.Tech.	Semester	Fall Semester 2022-23
Course Title	ANALOG CIRCUITS	Course Code	BECE206L
Faculty Name	Prof. Sangeetha R G	Slot	C2+TC2
		Class Nbr	CH2022231001118
Time	3 Hours	Max. Marks	100
If any data is missing assume and justify			

SECTION A (7 X 10 Marks)

 Answer **All** questions

1. The Common-Emitter bias configuration is shown in Figure.1

[10]

 


Figure. 1 Common-Emitter bias circuit

- (a) Find R_i , R_o , and A_v considering early voltage $V_A = \infty$, (b) Repeat part (a) for early voltage $V_A = 50$ V.
2. For the transistor in the circuit shown in Figure. 2, the nominal parameter values are $V_{TN} = 1$ V and $K_n = 0.5$ mA/V².

[10]

 


Figure 2. Voltage divider MOSFET Circuit

- (a) Determine the quiescent values V_{GSQ} , I_{DQ} , and V_{DSQ} . (b) Determine the range in I_D and V_{DS} values for a $\pm 5\%$ variation in V_{TN} and K_n .
3. For a class B amplifier providing a 20 V peak-peak signal to a $16\ \Omega$ load (speaker) and a power supply of $V_{DD} = 30\text{ V}$. Determine the
- Input power (2.5 Marks)
 - Output power (2.5 Marks)
 - Power efficiency (2.5 Marks)
 - Power dissipated by heat (2.5 Marks)
4. (a) Sketch the basic MOSFET two-transistor current mirror and explain the operation. (5 marks) [10]
 (b) Sketch a MOSFET cascode current mirror circuit and discuss the advantages of this design. (5 marks)
5. (a) Determine a circuit that is not stable in either state that utilizes timer IC. Briefly discuss the functionality. (5 Marks) [10]
 (b) Derive the expression of the duty cycle for the above circuit (5 Marks)
6. The inverting summer amplifier is given in Figure 3. [10]

 


Figure 3

- Derive the expression of output voltage in terms of input voltages V_1 , V_2 , and V_3 for the given circuit. (6 marks)
 - For the special case of $R_1=R_2=R_3=R_f$, what will be the output voltage in terms of input voltages? (2 marks)
 - For the special case of $R_1=R_2=R_3=3R_f$, what will be the output voltage in terms of input voltages? (2 marks)
7. A Non-inverting amplifier shown in Figure 4, has $R_1 = 1\text{ k}\Omega$ and $R_f = 8\text{ k}\Omega$. This opamp has $V_{ios} = 10\text{ mV}$; $I_B = 400\text{ nA}$ and $I_{os} = 50\text{ nA}$. [10]

 


Figure 4

- Find maximum output offset voltage due to V_{ios} and I_B (4 marks)
- Calculate the value of R_{comp} needed to reduce the effect of I_B (2 marks)

- C) Calculate max output offset voltage if R_{comp} calculated in (b) is connected in the circuit (4 marks)

SECTION B (2 X 15 Marks)

Answer All questions

8. (a) Explain the RC Phase shift oscillator with a neat circuit diagram and derive its frequency of oscillation. Also, design an RC phase shift oscillator so that $f_o = 500$ Hz. Assume $C = 1 \mu F$ (7 marks) [15]
- (b) (i) Design a first-order high pass filter at a cut-off frequency of 1 kHz with a pass band gain of 2. (4 marks)
- (ii) Plot the frequency response of the filter designed in part b(i). (4 marks)
9. Explain the function of a three-bit R-2R ladder digital to analog converter (DAC) with the necessary diagram and derive the expression for the output voltage. [15]

