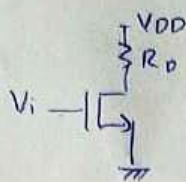


Wednesday DA key

C1-Slot.

9.



Class A power amplifier

$$V_{DD} = 10V \quad R_D = 10k\Omega \quad k_n = 0.5 \text{ mA/V}^2$$

$V_T = 1V \quad \lambda = 0$. Assume the output voltage is limited to the range between transition

point and $V_{DS} = 9V$ to minimize non linear distortion

$$V_{DS} = V_{DD} - I_D R_D$$

$$V_{DS}(\text{sat}) = V_{DS} - V_{TN}$$

$$I_D = k_n (V_{GS} - V_{TN})^2 \Rightarrow I_D = k_n V_{DS}(\text{sat})^2$$

$$V_{DS}(\text{sat}) = V_{DD} - k_n V_{DS}(\text{sat})^2 R_D$$

$$k_n R_D V_{DS}(\text{sat})^2 + V_{DS}(\text{sat}) - V_{DD} = 0$$

$$(0.5)(10) V_{DS}(\text{sat})^2 + V_{DS}(\text{sat}) - 10 = 0$$

$$V_{DS}(\text{sat}) = 1.32V$$

$$V_{DSQ} = \frac{9 + 1.32}{2}$$

$$= 5.16V$$

Q point lies midway between $V_{DS} = 1.32V$ and

$$V_{DS} = 9V$$

$$V_i = 3.84 \sin \omega t$$

$$\left(\frac{9 - 1.32}{2} \right) = 3.84$$

$$\bar{P}_L = \frac{1}{2} \frac{(3.84)^2}{10} = 0.73728 \text{ mW}$$


$$\frac{1}{2} \frac{V_o^2}{R}$$

$$I_{DQ} = \frac{10 - 5.16}{10} = 0.484 \text{ mA}$$

$$\frac{V_{DD} - V_{DSQ}}{R_D}$$

$$\bar{P}_S = V_{DD} I_{DQ} = (10)(0.484) = 4.84 \text{ mW}$$
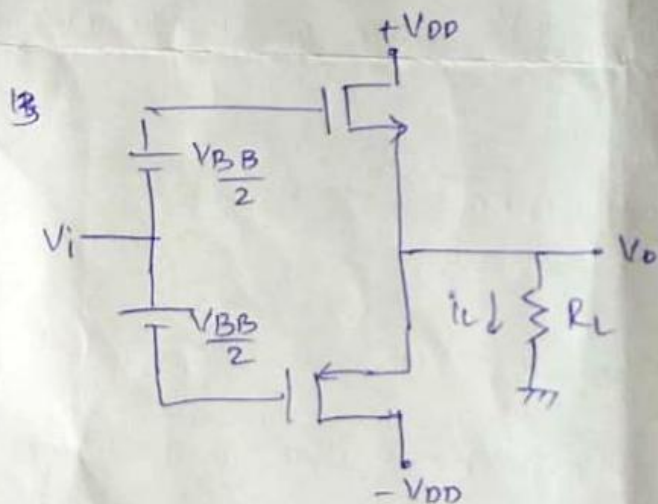
$$\eta = \frac{\bar{P}_L}{\bar{P}_S} = \frac{0.73728}{4.84} = 15.23\%$$



$$V_{DD} = 20 \text{ V}$$

$$R_L = 10 \Omega$$

$$k_n = 0.5 \text{ mA/V}^2$$

$$V_T = 1 \text{ V}$$

$$V_o = 8 \text{ V}$$

$$i_L = \frac{V_o}{R_L} = \frac{8}{20} = 0.4 \text{ A}$$

$$I_{DQ} = \frac{20}{100} i_L = \frac{20}{100} \times 0.4 = 0.08 \text{ when } v_o = 0$$

$$I_{DQ} = 0.08 = k \left(\frac{V_{BB}}{2} - V_T \right)^2$$

$$I_{DQ} = 0.08 = 0.5 \left(\frac{V_{BB}}{2} - 1 \right)^2$$

$$\left(\frac{V_{BB}}{2} - 1 \right)^2 = \frac{0.08}{0.5} = 0.16$$

$$\frac{V_{BB} - 1}{2} = 0.4$$

$$\frac{V_{BB}}{2} = 1.4$$

$$V_{BB} = 2.8$$

$$V_L = V_0 + V_{GSn} - \frac{V_{BB}}{2}$$

$$V_0 = 8V, \quad I_{Dn} \cong i_L = 0.4A$$

$$V_{GSn} = \sqrt{\frac{i_{Dn}}{K}} + V_T = \sqrt{\frac{0.4}{0.5}} + 1$$

$$= 0.89 + 1$$

$$= 1.89V$$

$$V_{GSp} = V_{BB} - V_{GSn}$$

$$= 2.8 - 1.89$$



$$= 0.91V$$

$$V_L = 8 + 1.89 - 1.4$$

$$= 8.49V$$

$$V_L = V_0 + V_{GSn} - \frac{V_{BB}}{2}$$

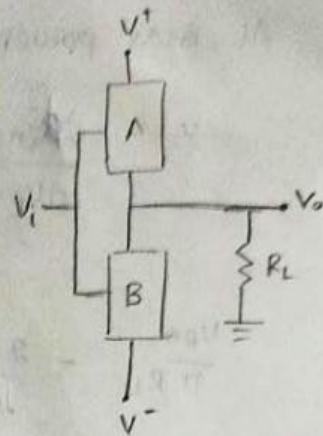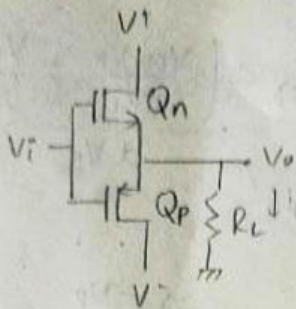11. Class B power MOSFET Conversion efficiency:



Instantaneous power dissipated at Qn

$$P_{Qn} = V_{DS} i_{Dn}$$

$$V_{DS} = V_{DD} - i_{Dn} R_L \Rightarrow V_{DS} = V_{DD} - \frac{V_p \sin \omega t}{R_L}$$

$$P_{Qn} = \left(V_{DD} - \frac{V_p \sin \omega t}{R_L} \right) \left(\frac{V_p \sin \omega t}{R_L} \right)$$

$$i_{Dn} = \begin{cases} \frac{V_p \sin \omega t}{R_L} & , 0 \leq \omega t \leq \pi \\ 0 & , \pi \leq \omega t \leq 2\pi \end{cases}$$

Average power dissipation

$$\bar{P}_{Qn} = \frac{1}{2\pi} \int_0^\pi \left(\frac{V_{DD} V_p \sin \omega t}{R_L} - \frac{V_p^2 \sin^2 \omega t}{R_L} \right) d(\omega t)$$

$$= \frac{1}{2\pi} \int_0^\pi \left(\frac{V_{DD} V_p \sin \omega t}{R_L} - \frac{V_p^2}{2R_L} (1 - \cos 2\omega t) \right) d\omega t$$

$$\bar{P}_{Qn} = \frac{V_{DD} V_p}{\pi R_L} - \frac{V_p^2}{4R_L}$$

output voltage for class-B $\Rightarrow V_o$

$$V_o = V_p \sin \omega t$$

$$i_{Dn} = \frac{V_p \sin \omega t}{R_L}$$

$$\int_0^\pi \sin^2 \omega t$$

$$= \frac{1 - \cos 2\omega t}{2}$$

$$\bar{P}_{\text{an}} = \bar{P}_{\text{ap}}$$

At max power

$$\left. \frac{\partial \bar{P}_{\text{an}}}{\partial V_p} \right|_{P_{\text{max}}} = 0 \Rightarrow \frac{d \left(\frac{V_{\text{DD}} V_p}{\pi R_L} - \frac{V_p^2}{4 R_L} \right)}{d V_p} = 0$$

$$\frac{V_{\text{DD}}}{\pi R_L} - \frac{2 V_p}{4 R_L} = 0 \Rightarrow \frac{V_p}{2 R_L} = \frac{V_{\text{DD}}}{\pi R_L}$$

$$\Rightarrow V_p = \frac{2 V_{\text{DD}}}{\pi}$$

$$\begin{aligned} P_{\text{an(max)}} &= \frac{V_{\text{DD}} V_p}{R_L \pi} - \frac{V_p^2}{4 R_L} \\ &= \frac{V_{\text{DD}}}{\pi R_L} \left(\frac{2 V_{\text{DD}}}{\pi} \right) - \left(\frac{2 V_{\text{DD}}}{\pi} \right)^2 \frac{1}{4 R_L} \quad \left[\because V_p = \frac{2 V_{\text{DD}}}{\pi} \right] \end{aligned}$$

$$\bar{P}_{\text{an(max)}} = \frac{V_{\text{DD}}^2}{\pi^2 R_L} \quad \text{which occurs when } V_p \Big|_{\bar{P}_{\text{an(max)}}} = \frac{2 V_{\text{DD}}}{\pi}$$

The avg power delivered to load is

$$\bar{P}_L = \frac{1}{2} \frac{V_p^2}{R_L}$$

Avg power supplied by each source

$$\bar{P}_{S+} = \bar{P}_{S-} = V_{\text{DD}} \left(\frac{V_p}{\pi R_L} \right)$$

Avg current is

$$V_p / \pi R_L$$

Total Average power supply by two sources

$$\bar{P}_S = 2 V_{\text{DD}} \left(\frac{V_p}{\pi R_L} \right)$$

Conversion efficiency

$$\eta = \frac{P_L}{P_S} = \frac{\frac{1}{2} \frac{V_P^2}{R_L}}{2 V_{DD} \left(\frac{V_P}{\pi R_L} \right)} = \frac{\pi}{4} \frac{V_P}{V_{DD}}$$

Maximum possible efficiency occurs when $V_P = V_{DD}$

$$\eta_{\max} = \frac{\pi}{4} = 78.5\%$$