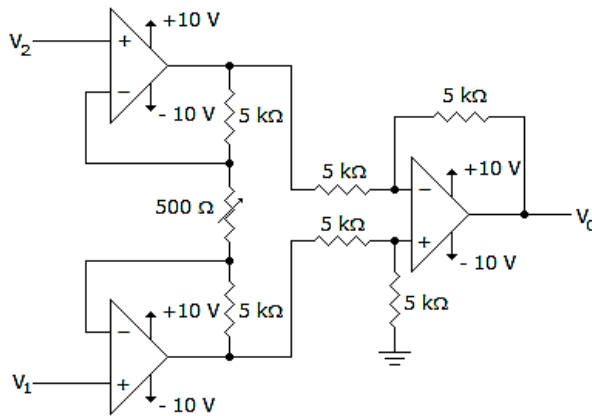



## OP-AMP Problems and Solutions

1. Calculate the output voltage for this circuit when  $V_1 = 2.5$  V and





Sol  
①  $V_o = \left(1 + \frac{2R}{R_p}\right) (V_1 - V_2)$   
 $= \left(1 + \frac{2 \times 5000}{500}\right) (2.5 - 2.25)$   
 $= (1 + 20) (0.25)$   
 $= 21 \times 0.25$   
 $= 5.25 \text{ Volt.}$

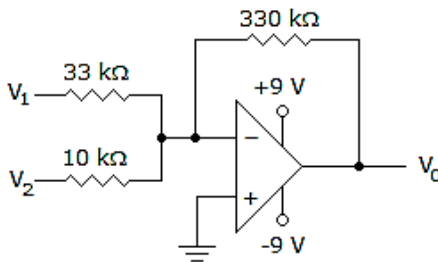2. Calculate the output voltage if  $V_1 = -0.2$  V and  $V_2 = 0$  V.




Sol  
②  $\frac{0 - V_1}{33} + \frac{0 - V_2}{10} + \frac{0 - V_o}{330} = 0$   
 $\frac{0 - (-0.2)}{33} + \frac{0 - 0}{10} + \frac{-V_o}{330} = 0$   
 $\frac{0.2}{33} - \frac{V_o}{330} = 0$   
 $\Rightarrow V_o = \frac{330 \times 0.2}{33} = 2 \text{ V.}$

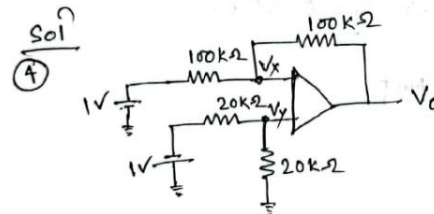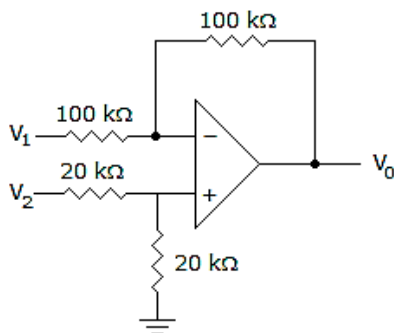4. Determine the output voltage when  $V_1 = -V_2 = 1$  V.



Sol  
④  $V_y = \frac{-1}{40} \times 20 = -0.5$   
 $\frac{-0.5 - 1}{100} + \frac{-0.5 - V_o}{100} = 0$   
 $-1.5 - 0.5 - V_o = 0$   
 $\Rightarrow V_o = -2 \text{ V.}$

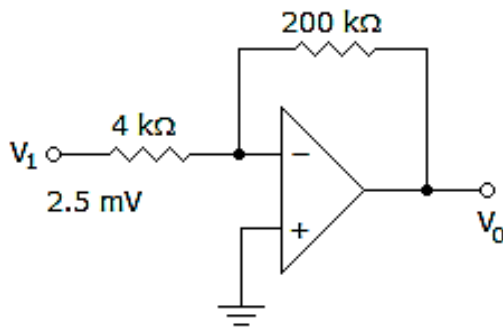7. Determine the output voltage for this circuit with a sinusoidal input of 2.5 mV.



⑦ Sol


$$\frac{0 - 2.5 \times 10^{-3}}{4 \times 10^3} + \frac{0 - V_0}{200 \times 10^3} = 0$$

$$\frac{V_0}{2 \times 10^5} = - \frac{2.5 \times 10^{-3}}{4}$$

$$\Rightarrow V_0 = - \frac{2.5 \times 2}{4} \times 10^{-1}$$

$$= -0.125 \text{ V}$$

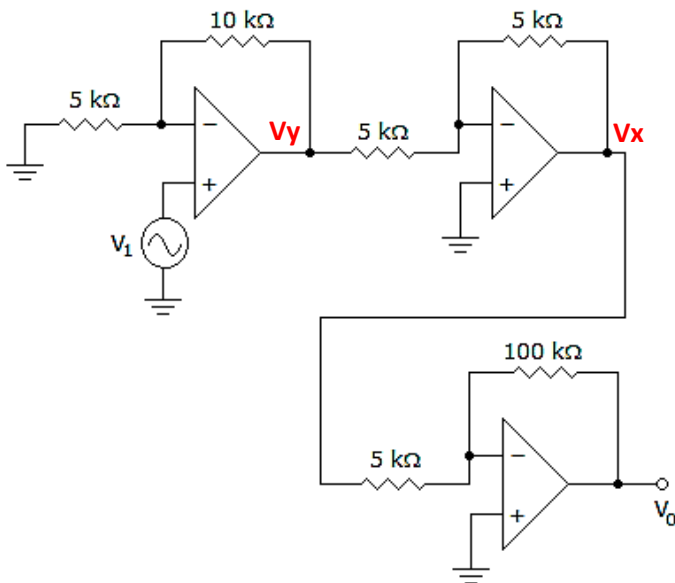10. Calculate the input voltage if the final output is 10.08 V.



⑩ Sol

$$\frac{0 - V_x}{5} + \frac{0 - V_0}{100} = 0$$

$$\frac{V_x}{5} + \frac{V_0}{100} = 0 \Rightarrow 20V_x + V_0 = 0 \quad \text{--- (1)}$$

$$V_x = -\frac{V_0}{20} = -\frac{10.08}{20} = -0.504 \text{ V}$$

$$\frac{0 - V_y}{5} + \frac{0 - V_x}{5} = 0$$

$$-\frac{V_y}{5} + \frac{0.504}{5} = 0 \Rightarrow V_y = 0.504 \text{ V}$$

Apply KCL for 1st opamp

$$\frac{V_1 - 0}{5} + \frac{V_1 - V_y}{10} = 0$$


$$\Rightarrow \frac{V_1}{5} + \frac{V_1 - 0.504}{10} = 0$$

$$\Rightarrow 2V_1 + V_1 - 0.504 = 0$$

$$\Rightarrow 3V_1 = 0.504$$

$$\Rightarrow V_1 = \frac{0.504}{3} = 0.168 \text{ V}$$

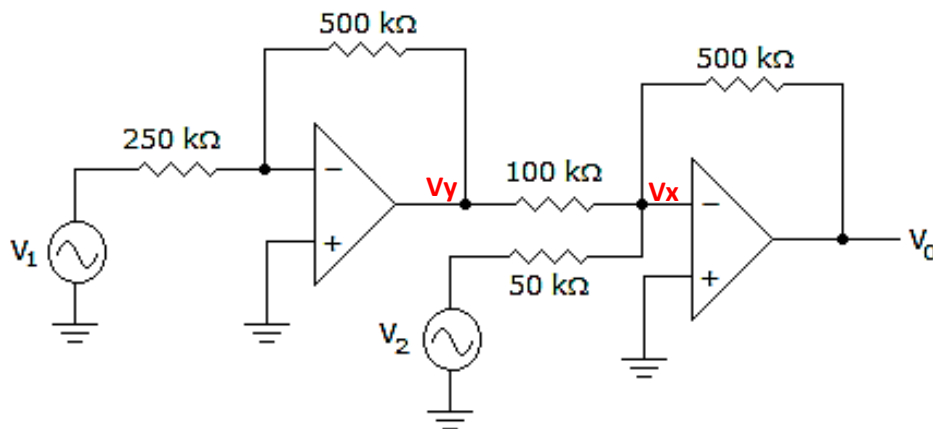13. Calculate the output voltage if  $V_1 = V_2 = 700 \text{ mV}$ .



⑬ sol

$$\frac{0 - V_1}{250} + \frac{0 - V_y}{500} = 0,$$

$$-\frac{V_1}{250} - \frac{V_y}{500} = 0,$$

$$-2V_1 - V_y = 0 \quad \text{--- ①}$$

$$V_y = -2V_1 = 1400 \times 10^{-3} \text{ V} = -1.4 \text{ V}.$$

$$\frac{0 - V_y}{100} + \frac{0 - V_2}{50} + \frac{0 - V_0}{500} = 0,$$

$$\frac{V_y}{100} + \frac{V_2}{50} + \frac{V_0}{500} = 0,$$

$$\frac{-1.4}{100} + \frac{700 \times 10^{-3}}{50} + \frac{V_0}{500} = 0,$$


$$\frac{-1.4}{100} + \frac{0.7}{50} = -\frac{V_0}{500}$$

$$\frac{-1.4 + 1.4}{100} = -\frac{V_0}{500}$$

$$\Rightarrow V_0 = 0 \text{ V. (Ans)}$$

16. Calculate the output voltage.

(16) Sol<sup>n</sup>

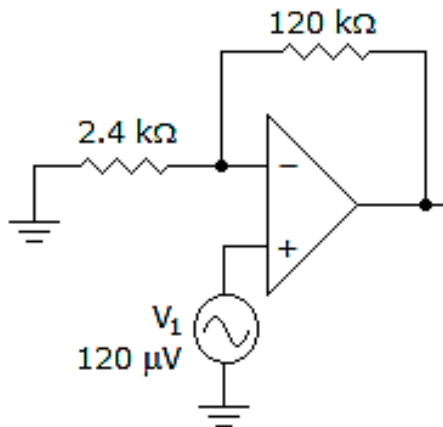

$$\frac{120 \times 10^{-6} - 0}{2.4 \times 10^3} + \frac{0 - V_o}{120 \times 10^3} = 0$$


$$\frac{V_o}{120} = \frac{120 \times 10^{-6}}{2.4}$$

$$\Rightarrow V_o = \frac{120}{2.4} \times 120 \times 10^{-6}$$

$$= \frac{1.44}{2.4} \times 10^3 \times 10^{-6}$$

$$= 6 \text{ mV. (Ans)}$$

25. Calculate  $I_L$  for this circuit.

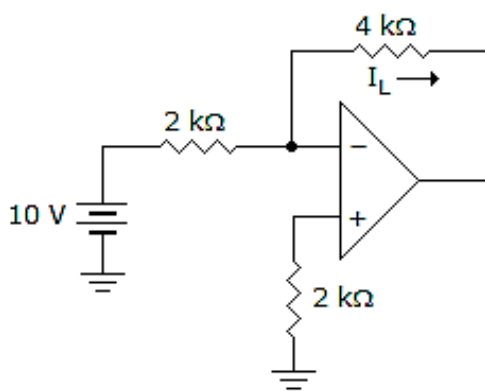

Sol<sup>n</sup>

$$\frac{0 - 10}{2 \times 10^3} + \frac{0 - V_o}{4 \times 10^3} = 0$$


$$\frac{V_o}{4} = -\frac{10}{2}$$

$$\Rightarrow V_o = -20 \text{ V.}$$

$$I_L = \frac{0 - V_o}{4 \times 10^3} = \frac{20}{4} \times 10^{-3} = 5 \text{ mA. (Ans)}$$

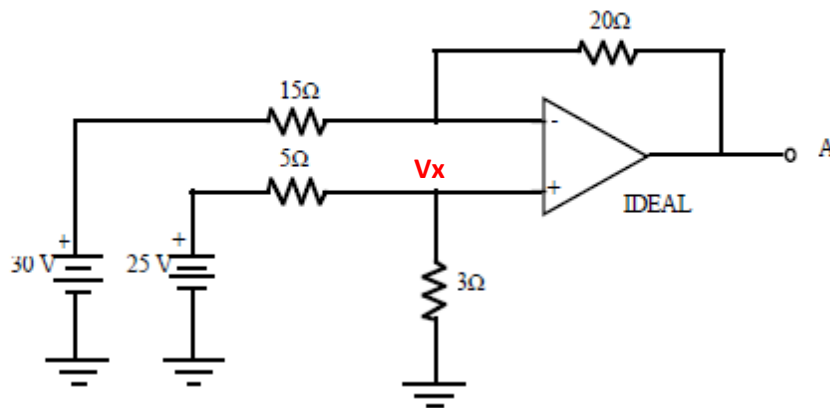26.

For the difference amplifier circuit shown, determine the output voltage at terminal A.



$$\frac{\text{sol}^n}{V_x = \frac{25}{5+3} \times 3 = \frac{75}{8} = 9.375$$

$$\frac{9.375 - 30}{15} + \frac{9.375 - V_A}{20} = 0$$


$$\Rightarrow -1.375 = -\frac{9.375 - V_A}{20}$$

$$\Rightarrow -27.5 = -9.375 + V_A$$

$$\Rightarrow \cancel{500} + 9.375 = V_A \Rightarrow V_A = -18.125 \text{ V}$$

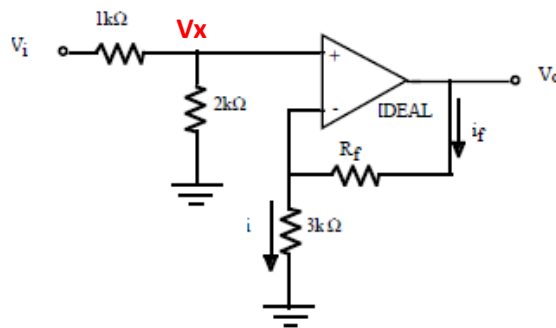27.

For the ideal op amp shown, what should be the value of resistor  $R_f$  to obtain a gain of 5?



$$(27) \quad V_x = \frac{V_i \times 2}{3}$$

$$\frac{V_x - V_o}{R_f} + \frac{V_x - 0}{3} = 0$$

$$\frac{V_x}{R_f} - \frac{V_o}{R_f} + \frac{V_x}{3} = 0$$

$$V_x \left( \frac{1}{R_f} + \frac{1}{3} \right) = \frac{V_o}{R_f}$$

$$\frac{2V_i}{3} \left( \frac{1}{R_f} + \frac{1}{3} \right) = \frac{V_o}{R_f}$$

$$\frac{V_o}{V_i} = \frac{2}{3} \left( \frac{1}{R_f} + \frac{1}{3} \right)$$


$$\Rightarrow 5 = \frac{2}{3} \left( \frac{R_f}{R_f} + \frac{R_f}{9} \right)$$

$$\Rightarrow R_f = \frac{39}{2} = 19.5$$


Q-28.

For the ideal Op-Amp circuit of figure. Determine the output voltage  $V_o$

[GATE EC 1993, IIT-Bombay]

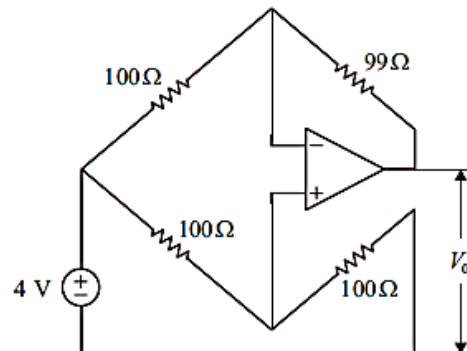

**Sol.** Circuit will reduce as follows

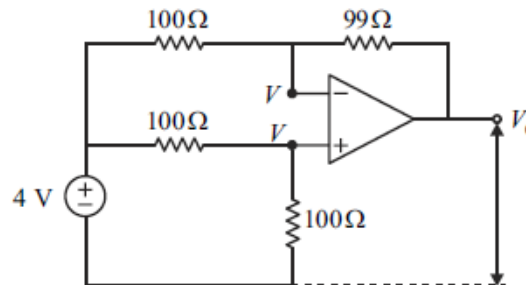

Due to virtual ground condition

$$V_+ = V_- = V$$

Apply KCL at non-inverting terminals

$$\frac{V-4}{100} + \frac{V}{100} = 0$$

$$\frac{2V}{100} = \frac{4}{100} \Rightarrow V = 2 \text{ Volts}$$

Apply KCL at inverting terminal

$$\frac{V-4}{100} + \frac{V-V_o}{99} = 0$$

Put  $V = 2$  Volts.

$$\frac{2-4}{100} + \frac{2-V_o}{99} = 0$$

$$\frac{2-V_o}{99} = \frac{2}{100}$$

$$200 - 100V_o = 198$$


$$100V_o = 2$$

$$V_o = 0.02 \text{ Volt}$$

Q-29.

For the Op-Amp circuit shown below,  $V_o$  is approximately equal to

[GATE IN 2008, IIT-Bangalore]

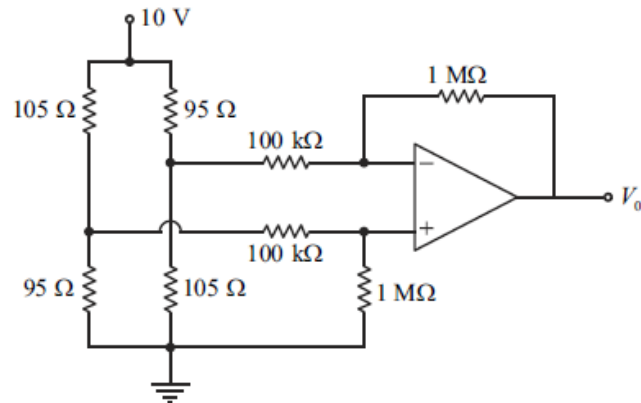



(A)  $-10\text{ V}$

(B)  $-5\text{ V}$

(C)  $+5\text{ V}$

(D)  $+10\text{ V}$

Sol.

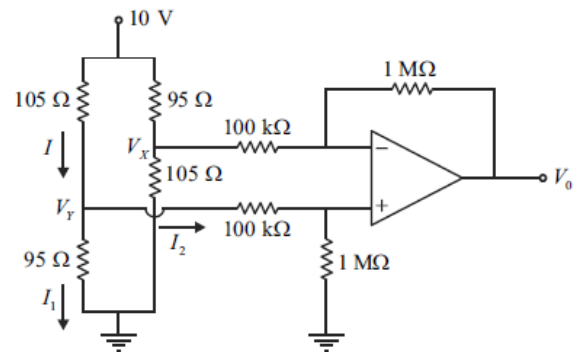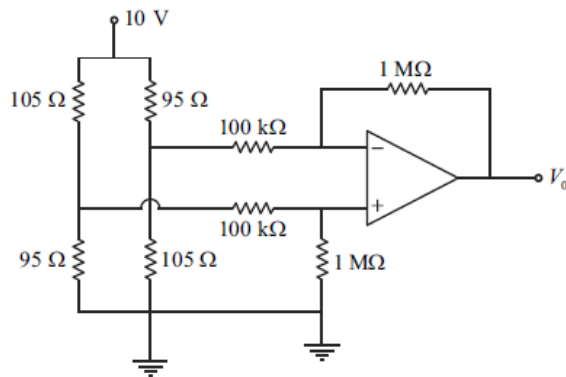


$$V_x = 10 \left( \frac{105}{200} \right) = 5.25 \text{ V}$$

$$I = I_1 + I_2$$

$$I_1 \gg I_2 \quad [\text{Due to small resistance } 95 \Omega]$$

$\Rightarrow 95 \Omega$  and  $105 \Omega$  will be in series
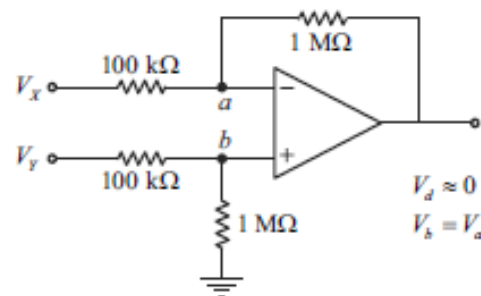
$$V_y = 10 \left( \frac{95}{200} \right) = 4.75 \text{ V} \quad [\text{By VDR}]$$



Apply KCL at 'b'

$$\frac{V_y - V_b}{100} = \frac{V_b}{1000} \quad \Rightarrow \quad 10V_y = 11V_b$$

$$V_b = \left( \frac{10}{11} \right) V_y = 4.31817 \text{ Volts}$$

Apply KCL at 'a'

$$\frac{V_x - V_a}{100} = \frac{V_a - V_o}{1000}$$

$$10V_x = 11V_a - V_o$$

$$V_o = 11V_a - 10V_x$$


$$V_o = 10(4.31187) - 10(5.25) = 47.5 - 52.5$$

$$V_o = -5 \text{ V}$$



In the circuit given below, the OP-AMP is ideal. The output voltage  $V_0$  in volt is \_\_\_\_\_.

[GATE IN 2016, IISc Bangalore]

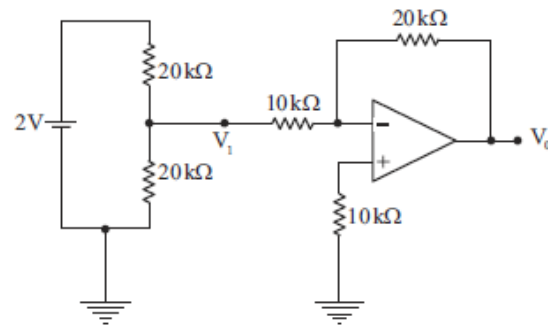

**Sol.**


$$\frac{V_1 - 2}{20} + \frac{V_1}{20} + \frac{V_1}{10} = 0$$

$$V_1 = 0.5 \text{ V}$$

$$V_0 = \frac{-20}{10} \times 0.5 = -1 \text{ V}$$

In the circuit given below, the OP-AMP is ideal. The value of current  $I_L$  in microampere is \_\_\_\_\_

[GATE IN 2016, IISc Bangalore]

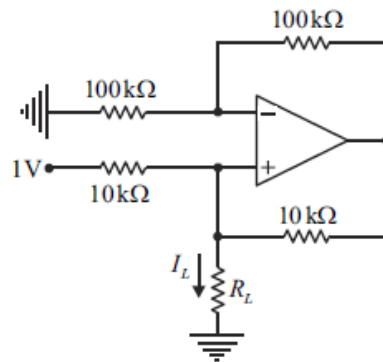

**Sol.** Applying KCL at inverting terminal,

$$\frac{V - 0}{100\text{ K}} + \frac{V - V_o}{100\text{ K}} = 0$$

$$\frac{2V}{100\text{ K}} = \frac{V_o}{100\text{ K}}$$

$$V_o = 2V$$

Applying KCL at non inverting,

$$\frac{V - 1}{10\text{ K}} + I_L + \frac{V - V_o}{10\text{ K}} = 0$$

$$\frac{V}{10\text{ K}} - \frac{1}{10\text{ K}} + I_L - \frac{V}{10\text{ K}} = 0$$

$$I_L = 0.1\text{ mA} = 100\text{ }\mu\text{A}$$

