
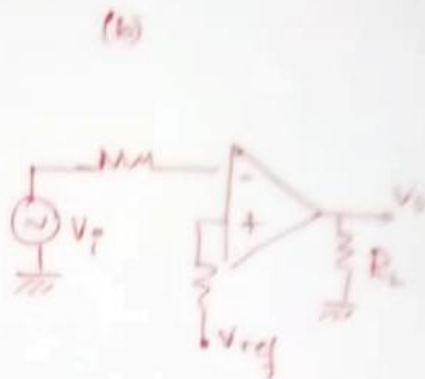


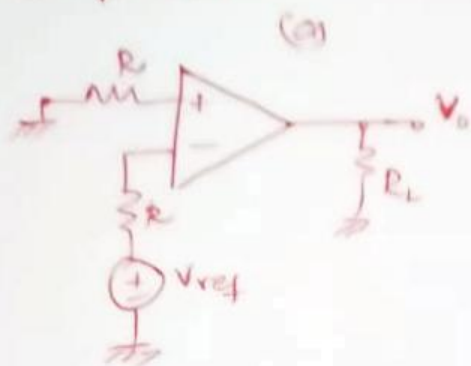20. ~~Design~~ ^{Consider} an inverting and non-inverting comparator.




Draw the input and output waveforms.

21. a) Explain the operation of Schmitt trigger in detail with suitable waveforms.

b) A Schmitt trigger with upper threshold voltage $V_{UT} = 0V$ and hysteresis width $V_H = 0.2V$ converts a $1KHz$ ~~signal~~ sine wave of amplitude $4V_{pp}$ to a square wave. Calculate the time duration of negative and positive portion of the output waveform.

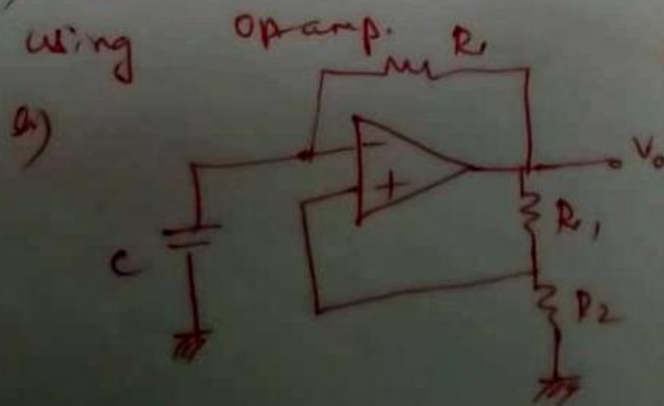32. a) Explain the operation of astable multivibrator using op.amp.




Calculate the frequency of oscillation

$$R_2 = 10k\Omega, R_1 = 11.6k\Omega$$

$$R = 100k\Omega, C = 0.01\mu F$$

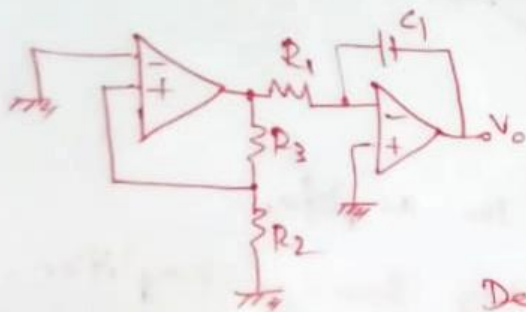33. a) Explain the working principle of triangular wave generator, derive the frequency of oscillation by



If $T = 1 \text{ ms}$,

$V_{\text{ref}} = 5 \text{ V}$

$V_{\text{sat}} = \pm 10 \text{ V}$

Design a triangular wave generator.

34. a) Explain RC phase shift oscillator with necessary conditions for sustained oscillations.
b) Design RC phase shift oscillator for $f_0 = 1 \text{ MHz}$,
Assume $C = 0.1 \mu\text{F}$, $R_1 = 10 \text{ k}\Omega$

