

Reg. No.:

Name :



**VIT**

Vellore Institute of Technology  
(Deemed to be University under section 3 of UGC Act, 1956)

**Continuous Assessment Test II – March 2023**

Programme	: B.Tech (ECE/ECM)	Semester	: WS 2022-23
Course	: Analog Circuits	Code	: BECE206L
Faculty	: Dr.Sangeetha R.G	Class Nbr	: CH2022235002479
Time	: 90 Minutes	Slot	: F1+TF1
		Max. Marks	: 50

**Answer ALL the questions**

Q.No.	Sub. Sec.	Questions	Marks
-------	-----------	-----------	-------

The transistor parameters for the differential amplifier shown in Figure 1 are  $V_{TN} = 0.5$  V,  $k_n' = 80 \mu\text{A}/\text{V}^2$ ,  $W/L = 4$ , and  $\lambda = 0$ . (a) Find  $R_D$  and  $I_Q$  such that  $I_{D1} = I_{D2} = 80 \mu\text{A}$  and  $v_{O2} = 2$  V when  $v_1 = v_2 = 0$ . (b) Draw the dc load line, and plot the  $Q$  point for  $M_2$ . (c) What is the maximum common-mode input voltage?

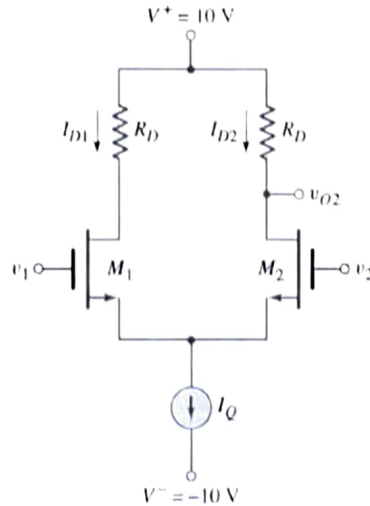


Figure 1

1. 15

2. Find an expression for the output  $V_o$  of the amplifier circuit of Figure 2. Assume an ideal op-amp. What mathematical operation does the circuit perform? 10


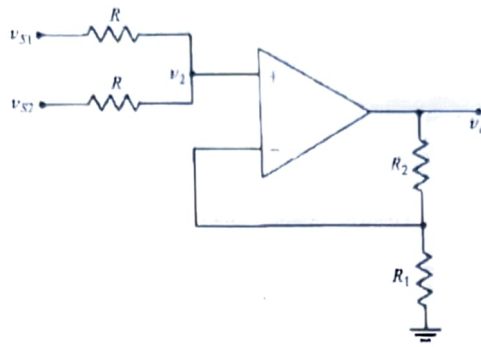


Figure 2

Calculate the output voltage in terms input voltages  $V_1$  and  $V_2$  for the circuit shown below

3.

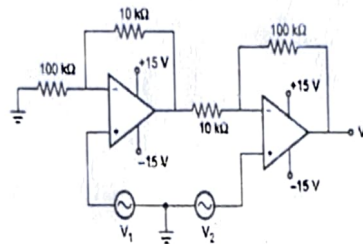

10

Figure 3

4.

The following component values are used in the circuit of op-amp astable multivibrator  $C = 0.1 \mu\text{F}$ ,  $R = 50 \text{ k}\Omega$ ,  $R_1 = 10 \text{ k}\Omega$ ,  $R_2 = 50 \text{ k}\Omega$ . The output voltage is bounded to the limits  $+10 \text{ V}$  and  $-5 \text{ V}$ . Calculate the timing periods  $t_1$  and  $t_2$ .

10

5

Design a square wave generator for  $f = 1 \text{ kHz}$  and DC supply voltage  $\pm 12 \text{ V}$ .

5

Total

50

