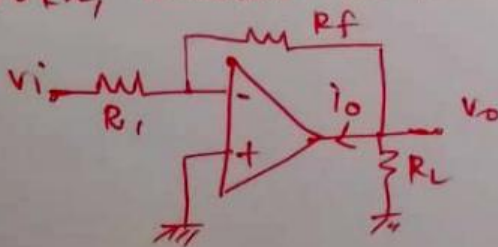


19. For the non-inverting amplifier $R_i = 1k\Omega$, $P_f = 100k\Omega$
- Calculate the maximum output offset voltage due to V_{ios} and I_B . Assume $V_{ios} = 10mV$, $I_B = 300nA$, $I_{os} = 50nA$.
 - Calculate R_{comp} needed to reduce the offset of I_B .
 - Calculate the maximum output offset voltage if R_{comp} as calculated in (b) is connected in the circuit.

20. A non-inverting amplifier with a gain of 100 is nulled at $20^\circ C$. What will happen to the output voltage if the temperature rises to $50^\circ C$ for an offset voltage drift of $0.15mV/^\circ C$?

21. For the below circuit, $R_i = 1k\Omega$, $P_f = 100k\Omega$, $R_L = 50k\Omega$, calculate the total current i_o .



22. Derive the output resistance of practical inverting amplifier.
23. Explain slew rate and derive it. Derive an equation of f_m maximum input frequency at which we can obtain an undistorted output voltage.
24. Derive the DC characteristics of operational amplifier.