
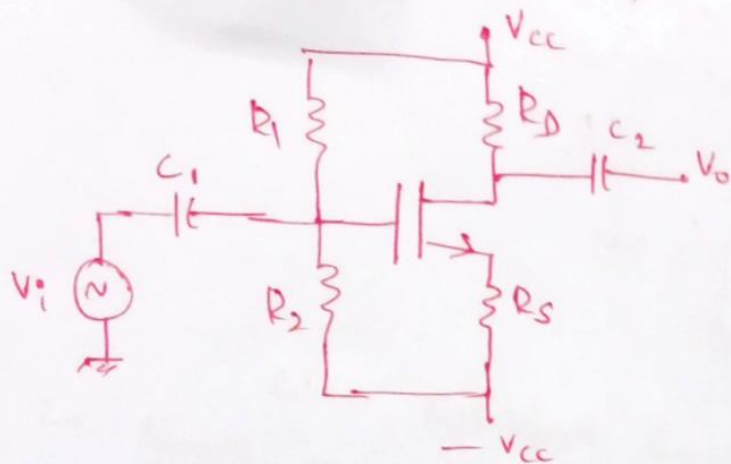


5. Consider the circuit below,

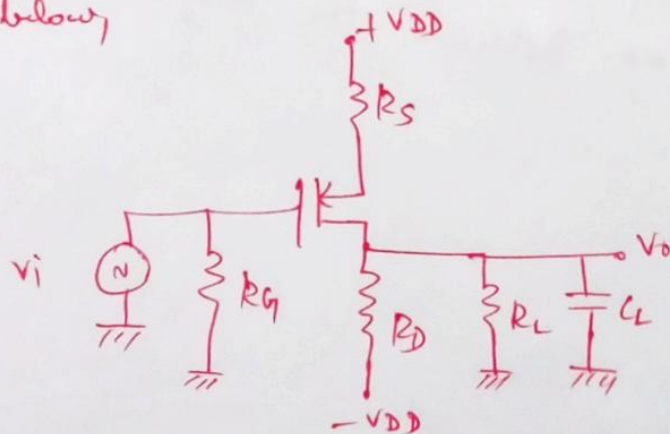


1. Derive the Q point and draw the load line
2. Derive the small signal voltage gain.
3. Let $V_{CC} = 10V$, $R_1 = 100k\Omega$, $R_2 = 50k\Omega$, $R_D = 5k\Omega$, $R_S = 1k\Omega$, $V_T = 1V$, $k_n = 0.5 \text{ mA/V}^2$, calculate ~~part (1)~~ part (1) and part (2)

6. Consider the Common Source Circuit with load capacitor below,



1. Draw & Derive the small signal voltage gain, maximum small signal voltage
2. Let $R_D = 10k\Omega$, $R_L = 100k\Omega$, $R_G = 1k\Omega$, $V_{DD} = 20V$, $C_L = 1\mu F$, calculate the maximum voltage gain. $k_n = 1 \text{ mA/V}^2$

7.

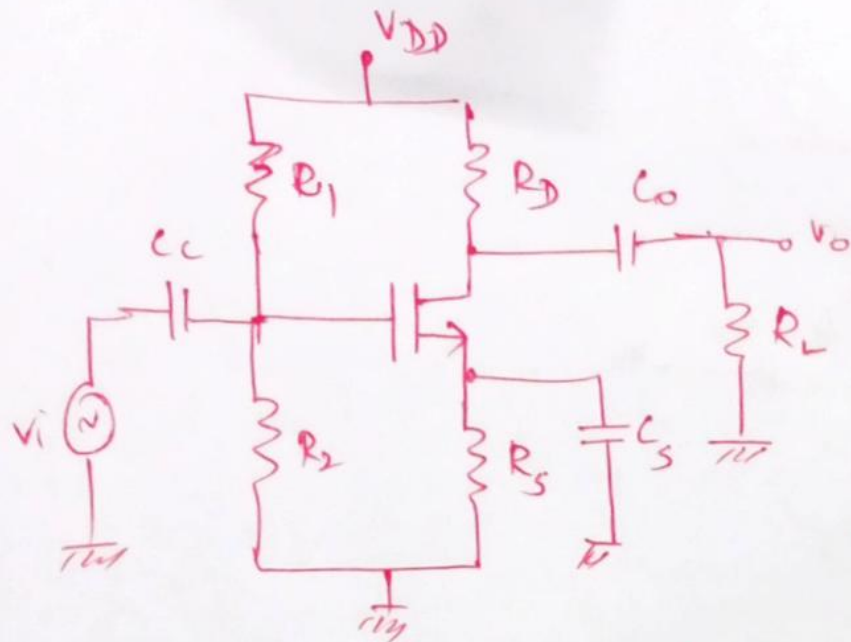

1. Derive the large signal equivalent model
2. ~~Draw~~ the small signal ~~voltage~~ equivalent circuit and find the expression for midband voltage gain.
3. Find the input resistance, output resistance and small signal voltage gain.

8. For a nchannel MOSFET, $k_n = 0.2 \text{ mA/V}^2$, $V_T = 1\text{V}$, $\lambda = 0$, $C_{gd} = 0.02 \text{ pF}$, $C_{gs} = 0.25 \text{ pF}$. The device is biased at $I_{DQ} = 0.4 \text{ mA}$. Determine the unity gain frequency.