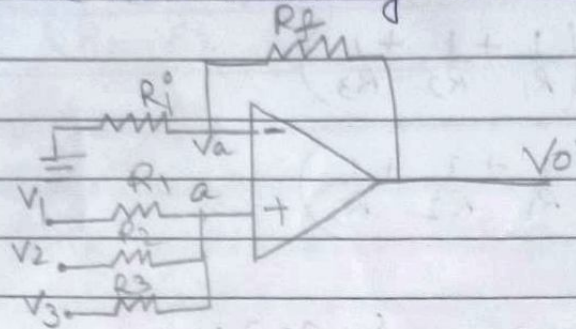


Mod-4 (part-2)

Q5. Consider the non-inverting summing amplifier.



(a) Find the gain of the amplifier.

Ans. Applying KCL at node 'a' :-

$$0 = \frac{V_a}{R_i} = \frac{V_a - V_o}{R_f} \Rightarrow \frac{V_o}{R_f} = \frac{V_a}{R_f} + \frac{V_a}{R_i} \quad \text{--- (1)}$$

$$\frac{V_1}{R_1} = \frac{V_a}{R_1} + \frac{V_2}{R_2} = \frac{V_a}{R_2} + \frac{V_3}{R_3} = 0 \quad \text{--- (2)}$$

from (1), $\frac{V_o}{R_f} = V_a \left(\frac{R_f + R_i}{R_f R_i} \right)$

$$\frac{V_o R_i R_f}{R_f (R_f + R_i)} = V_a \Rightarrow V_a = \frac{V_o R_i}{R_f + R_i}$$

$$\frac{V_1 - \frac{V_o R_i}{R_f + R_i}}{R_1} + \frac{V_2 - \frac{V_o R_i}{R_f + R_i}}{R_2} + \frac{V_3 - \frac{V_o R_i}{R_f + R_i}}{R_3} = 0$$

$$V_a = \frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3}$$

$$\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

$$V_o = \left(1 + \frac{R_f}{R_i} \right) V_a$$

$$V_o = \left(1 + \frac{R_f}{R_i} \right) \left(\frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3} \right)$$

$$\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

i) $V_1 = V_2 = V_3$

$$V_o = \left(1 + \frac{R_f}{R_i}\right) V_1 \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right)$$

$$\left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right)$$


ii) $R_1 = R_2 = R_3$

$$V_o = 1 + \frac{R_f}{R_i} \left(\frac{3V_1}{R_1} \right) = \left(1 + \frac{R_f}{R_i} \right) V_1 \left(\frac{3}{R_1} \right)$$

Here, $V_{in} = V_1 = V_2 = V_3$.

So, gain of the amplifier = $\frac{V_o}{V_{in}} = \left(1 + \frac{R_f}{R_i} \right) \frac{3}{R_1} = 1 + \frac{R_f}{R_i}$

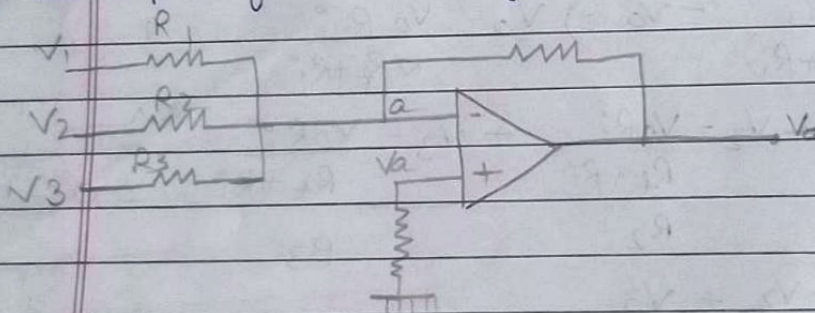(b) Repeat for inverting summing amplifier.



Applying KCL at node a,

$$\frac{V_1 - V_a}{R_1} + \frac{V_2 - V_a}{R_2} + \frac{V_3 - V_a}{R_3} + \frac{V_a - V_o}{R_f} = 0$$

$$V_a = 0$$

$$\frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3} = -\frac{V_o}{R_f}$$

$$\Rightarrow V_o = - \left(\frac{R_f}{R_1} V_1 + \frac{R_f}{R_2} V_2 + \frac{R_f}{R_3} V_3 \right)$$

If $V_1 = V_2 = V_3$

$$V_o = -R_f V_i \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right)$$

$$\text{If } R_1 = R_2 = R_3$$


$$V_o = -\frac{3R_f}{R_1} V_i$$

$$\text{Here, } V_{in} = V_1 = V_2 = V_3$$



$$\text{So, gain of the amplifier} = \frac{V_o}{V_{in}} = \frac{-\frac{3R_f}{R_1} V_i}{V_i} = -\frac{3R_f}{R_1}$$

26. Explain the working principle of half wave rectifier using op-amp.

Ans.

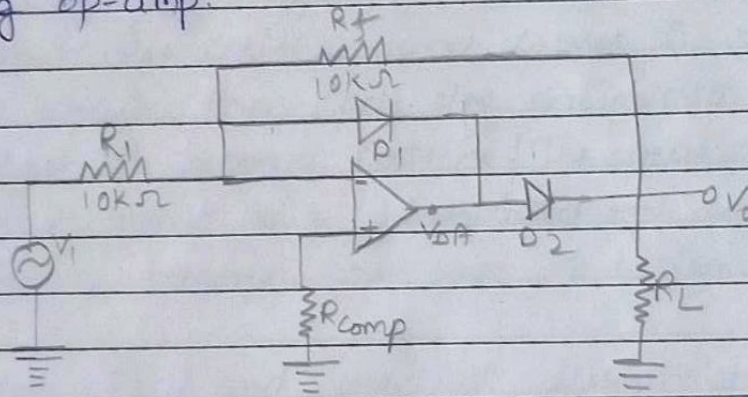

Ideal half wave rectifier

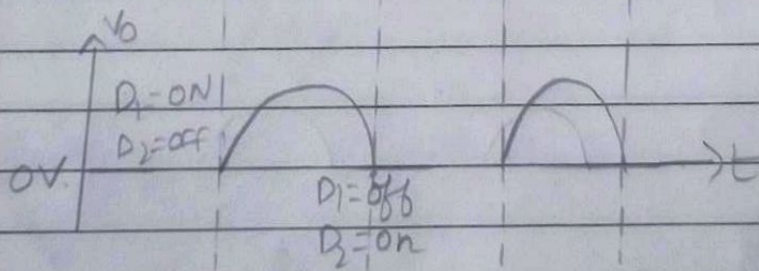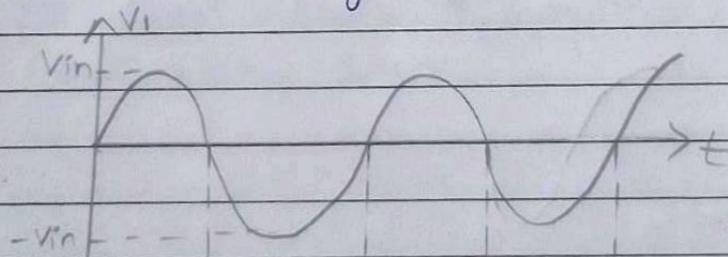


Input/output waveforms

An inverting amplifier can be converted into an ideal half-wave rectifier by adding two diodes as drawn in the diagram. When V_i is positive, diode D_1 conducts causing V_{OA} to go to ~~pos~~ negative by one diode drop. Hence Diode D_2 is reverse biased. The output voltage V_o is zero, because, for all practical purposes, no current flows through R_f and the input current flows through D_1 . For negative input, i.e., $V_i < 0$ diode D_2 conducts and D_1 is off. The negative input V_i forces the op-amp output V_{OA} positive and causes D_2 to conduct. The circuit then acts like an inverter for $R_f = R$, and output V_o becomes positive. The op-amp in the circuit must be a high speed op-amp since it alternates between open loop and closed loop operations.

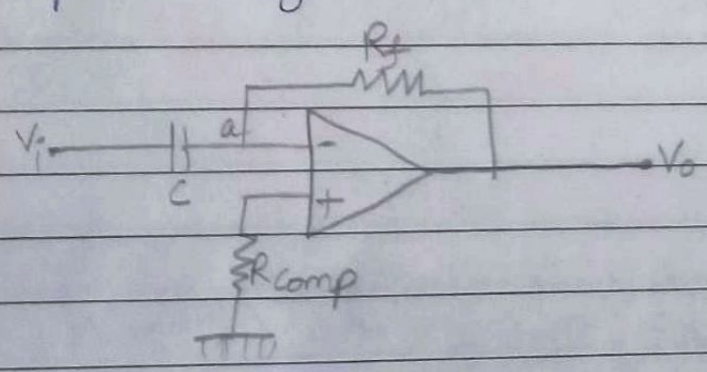Q7.) Design ideal and practical differentiator using op-amp and draw its frequency response.

Ans. For ideal differentiator, capacitor is in series with the input voltage source.



$$V_a = 0V$$

$$i_c = C \frac{dv}{dt}$$

$$= C \frac{dv_i}{dt}$$

Applying KCL at node a,

$$C \frac{dv_i}{dt} = \frac{V_a - V_o}{R_f}$$

$$= -\frac{V_o}{R_f} \quad (V_a = 0)$$

$$\Rightarrow -R_f C \frac{dV_o}{dt} = V_o$$

$$V_o(t) = V_o(s)$$

$$V_o(t) = V_o(s)$$

$$\frac{dV_o(t)}{dt} = s V_o(s)$$

Taking s domain :- $V_o(s) = R_f C (s V_o(s))$


$$\frac{V_o(s)}{V_i(s)} = -s R_f C$$

$$s = j\omega$$


$$\frac{V_o(j\omega)}{V_i(j\omega)} = -j\omega R_f C$$

$$\therefore |A| = \omega R_f C$$

Frequency response :-

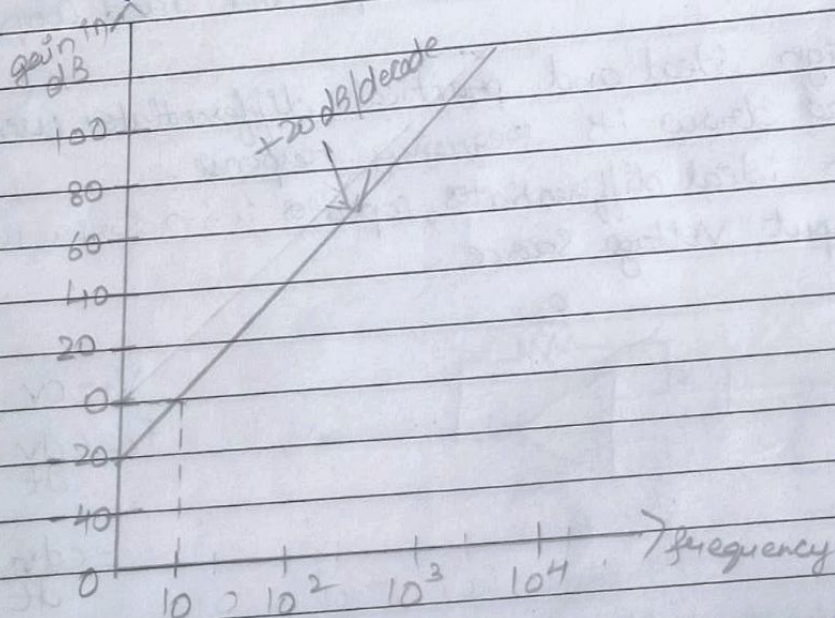

practical Differentiator:-

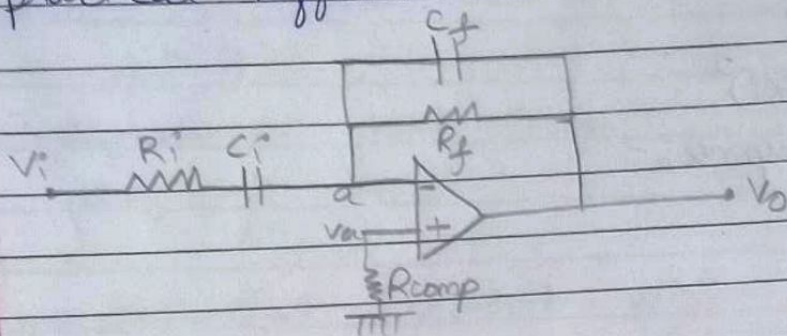

Applying KCL at node a,

$$i = \frac{V_i - V_a}{R_i + \frac{1}{j\omega C_i}}$$

$$= \frac{V_i - V_a}{R_i + \frac{1}{j\omega C_i}}$$

$$\frac{V_i - V_a}{R_i + \frac{1}{j\omega C_i}} = -\frac{V_o}{Z_f}$$

$$Z_f = R_f \parallel C_f = R_f \times \frac{1}{j\omega C_f}$$

$$= \frac{R_f + \frac{1}{j\omega C_f}}{j\omega C_f}$$

$$\frac{V_i}{R_i + \frac{1}{j\omega C_i}} = -\frac{V_o}{R_f} = \frac{V_o}{\frac{1}{j\omega C_f}}$$

$$\frac{V_i(s)}{R_i + \frac{1}{sC_i}} = -\frac{V_o(s)}{R_f} = \frac{V_o(s)}{\frac{1}{sC_f}}$$

$$\frac{V_o(s)}{V_i(s)} = \frac{-R_f}{1 + sR_i C_i} \times \frac{sC_f}{R_f + \frac{1}{sC_f}}$$


$$= -sR_f C_i$$

$$(1 + sR_f C_f)(1 + sR_i C_i)$$

$$\text{If } R_f = R_i C_i$$


$$A = \frac{-SR_i C_i}{(1 + SR_i C_i)^2}$$

• Frequency response:-

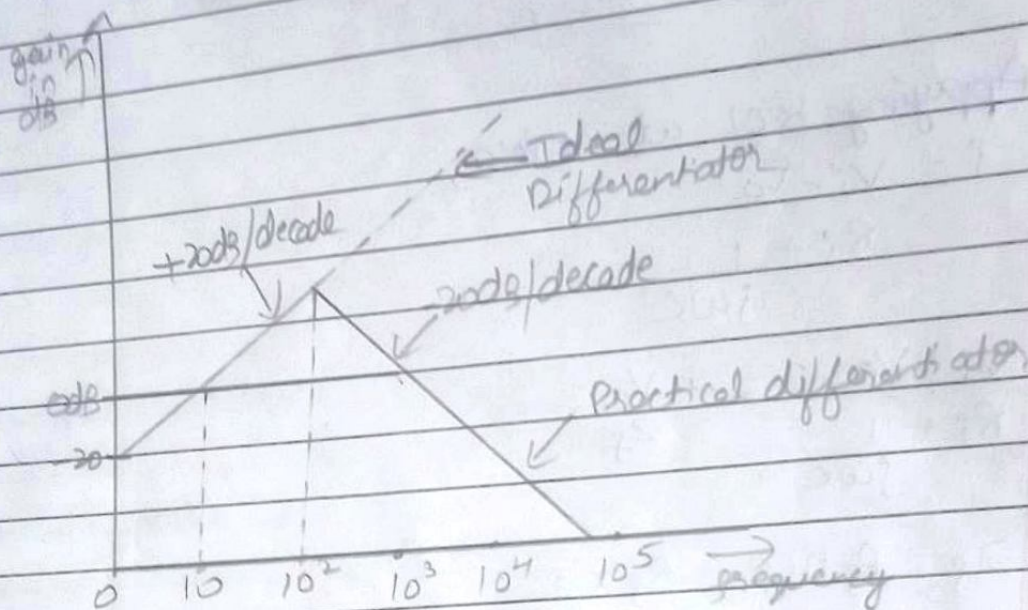

28(a) design ideal and practical integrator using op-amp and draw its frequency response.

Ans: Ideal integrator:-

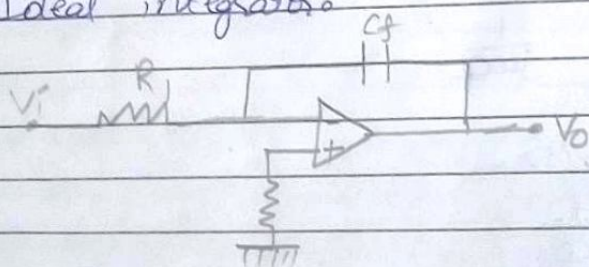

$$V_a = 0V$$

Applying KCL at node a,

$$\frac{V_i}{R_i} = V_o j\omega C_f \quad \text{or}$$

$$\frac{V_i}{R_i} = -C_f \frac{dV_o}{dt}$$


$$\frac{dV_o}{dt} = -\frac{1}{R_i C_f} V_i$$

$$= -\frac{R_f}{R_i}$$

$$1 + sC_f R_f$$


$$|A| = \left| \frac{V_o(s)}{V_i(s)} \right| = \frac{\frac{R_f}{R_i}}{1 + R_f C_f s}$$

Frequency response:-

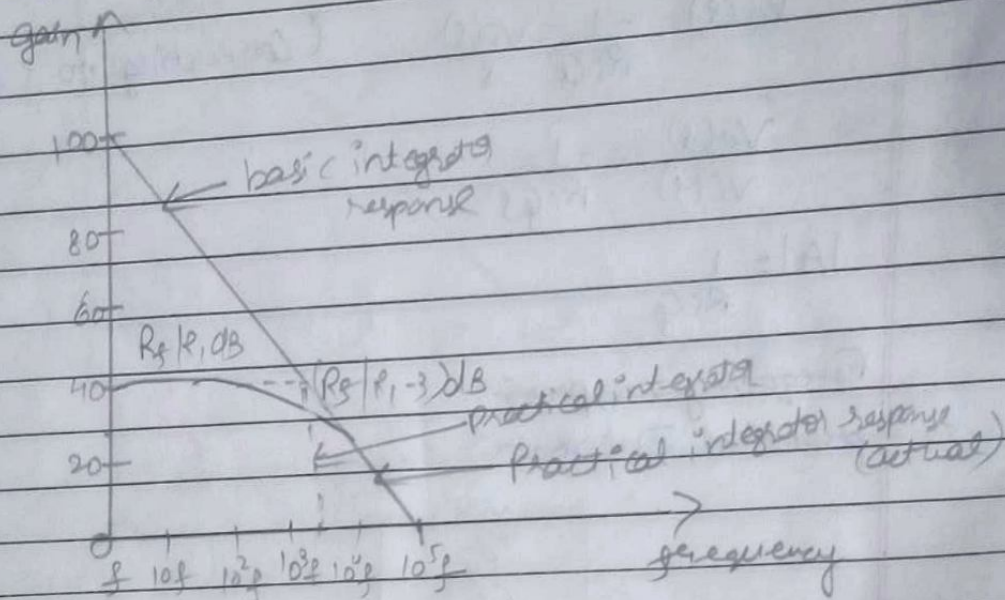

(b) Consider practical integrator, $R_i = 10k\Omega$, $R_f = 100k\Omega$, $C_f = 10nF$, determine the lower frequency level of integration and find the output if the input is 1V peak sine wave at 5KHz.

Ans: Here, $R_i = 10k\Omega$

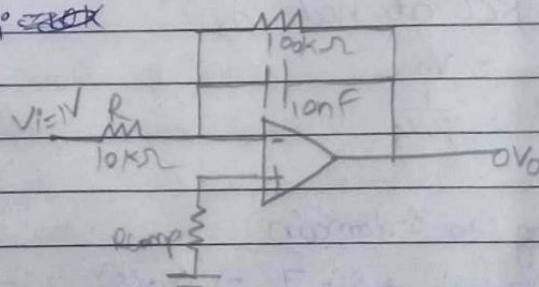

We know that the lower frequency limit of integration,
 $f = \frac{1}{2\pi R_f C_f}$

$$f = \frac{1}{2\pi \times 100 \times 10^3 \times 10 \times 10^{-9}} = 159.23 \text{ Hz}$$

Also,

$$\text{As } \omega = 5 \text{ kHz} \Rightarrow V_{in}(t) = 1 \sin 2\pi 5000t$$

we know that

$$V_{out}(t) = -\frac{1}{R_1 C} \int V_{in}(t) dt$$

$$= -\frac{1}{10 \text{ K} \times 10 \text{ nF}} \int 1 \sin 2\pi 5000t dt$$

$$V_{out}(t) = -10^4 \int 1 \sin 2\pi 5000t dt$$

$$V_{out}(t) = -10^4 \frac{1}{2\pi 5000} \int \sin 2\pi 5000t dt$$

$$V_{out}(t) = -0.318 (-\cos 2\pi 5000t)$$

$$V_{out}(t) = 0.318 \cos 2\pi 5000t$$

29) Repeat problem 25, if $V_1 = V_2 = V_3 = 5 \text{ V}$, $R_1 = R_2 = R_3 = R = 1 \text{ K}$, $R_F = 10 \text{ K}$. Find V_o . Consider non-inverting amplifier.

$$\text{Ans: } V_o = \left(1 + \frac{R_F}{R_i}\right) V_i$$

Here, $V_i = 5 \text{ V}$, $R_i = 1 \text{ K}$, $R_F = 10 \text{ K}$.

$$V_o = \left(1 + \frac{10 \text{ K}}{1 \text{ K}}\right) 5$$

$$= 11 \times 5$$

$$= 55 \text{ Volts.}$$