

Module 2:

Module:2 MOSFET Power Amplifiers 4 hours

- Power Amplifiers, Power Transistors, Classes of Amplifiers, Class A Power Amplifiers, **Class B, Class AB Push-Pull Complementary Output Stages.**

Design

Class A design

$$V_{DS} = V_{DD} - I_D R_D$$

$$V_{DS} = 20 - (28 \times 10^{-3})(120) = 16.64V \approx 17V$$

$$V_{DS}(\text{sat}) = V_{GS} - V_{TN}$$

$$I_D = K_n (V_{GS} - V_{TN})^2$$

$$V_{DS}(\text{sat}) = V_{DD} - K_n R_D V_{DS}^2(\text{sat})$$

To obtain the maximum symmetrical swing under the conditions specified, we want the Q-point midway between $V_{DS} = 0.4$ and $V_{DS} = 17$

Give

$$I_D = 0.028 = 28\text{mA}$$

$$K_n = 1\text{A} / \text{V}^2$$

$$V_{DD} = 20\text{V}$$

$$R_D = 120\Omega$$

$$V_{DS(\text{sat})} = V_{DD} - K_n R_D V_{DS}^2(\text{sat})$$

$$V_{DS(\text{sat})} = 20 - 1(120)V_{DS}^2$$

$$V_{DS(\text{sat})} + 1(120)V_{DS}^2 - 20 = 0$$

solving :

$$V_{DS(\text{sat})} = 0.404$$

$$V_{DSQ} = \frac{V_{DS} + V_{DS(sat)}}{2} = \frac{17 + 0.4}{2} = 8.702$$

$$v_P = V_{DS} - V_{DSQ} = 17 - 8.702 = 8.3 \sin \omega t$$

$$P_L = \frac{1}{2} \frac{(V_P)^2}{R_D} = \frac{1}{2} \frac{(8.3)^2}{120k} = 0.28mW$$

$$P_s = V_{DD} I_{DQ}$$



$$I_{DQ} = \frac{V_{DD} - V_{DSQ}}{R_D} = \frac{20 - 8.702}{120k} = 0.09415mA$$

$$P_s = V_{DD} I_{DQ} = 20 \times 0.09415mA = 1.88mW$$

$$\eta = \frac{P_L}{P_s} = \frac{0.28mW}{1.88mW} \times 100 = 14\%$$

Class B operation (Ideal)



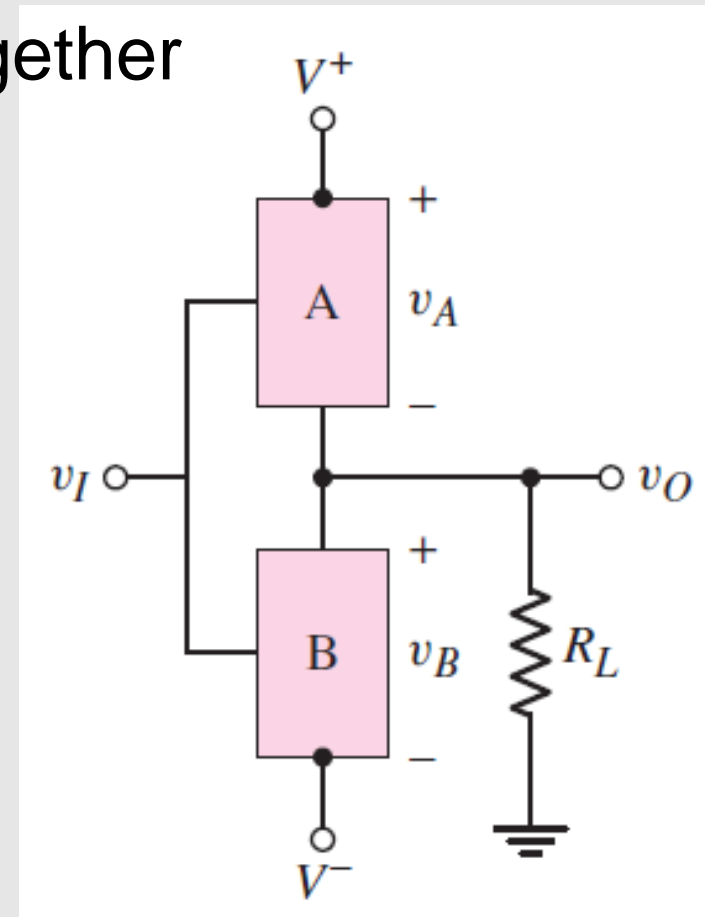
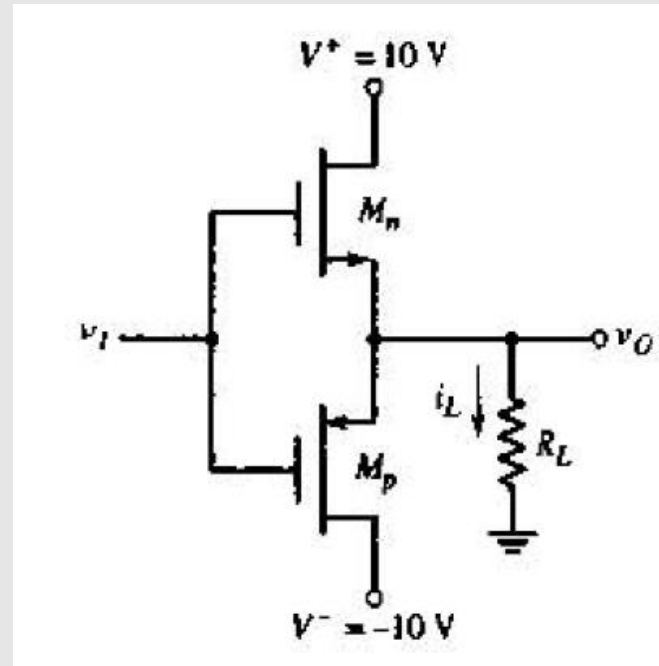
- Complementary pair of electronic devices (NMOS and PMOS)
- Device A: NMOS ; Device B: PMOS
- Output is at drain (v_o) Note: Source is connected together
- **Case 1:** $v_I = 0$: Both devices are OFF:
Zero bias currents: $v_o = 0$



Class B operation (Ideal)

- Complementary pair of electronic devices (NMOS and PMOS)
- Device A: NMOS ; Device B: PMOS
- Output is at drain (v_O) **Note: Source is connected together**
- Case 1: $v_I = 0$: Both devices are OFF:
Zero bias currents: $v_O = 0$
- **Case 2:** $v_I > 0$: **Device A is ON**
Device B is OFF

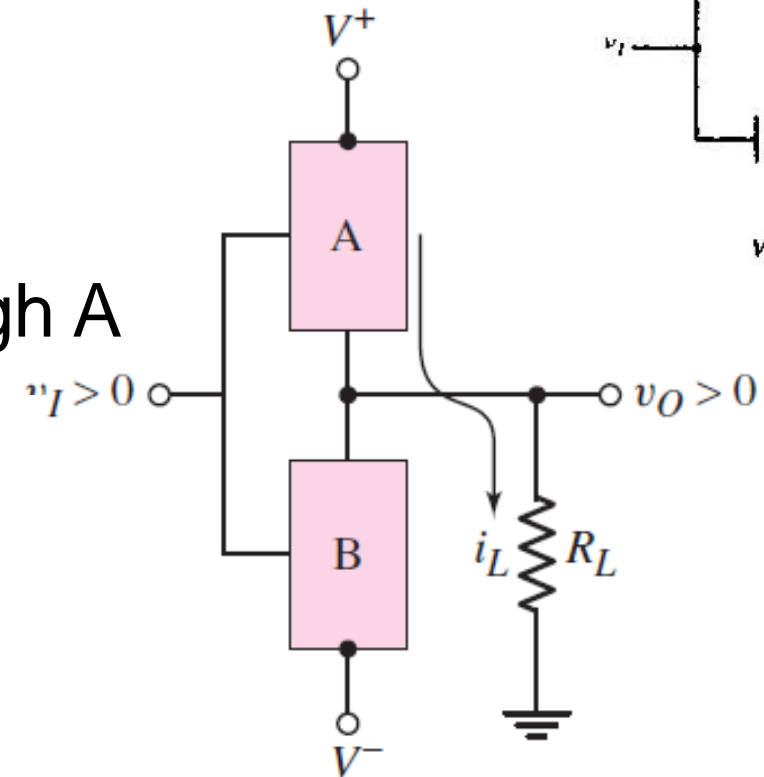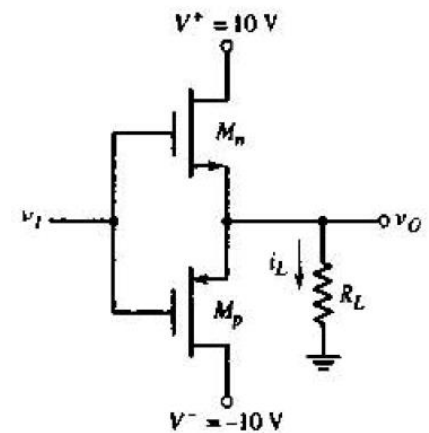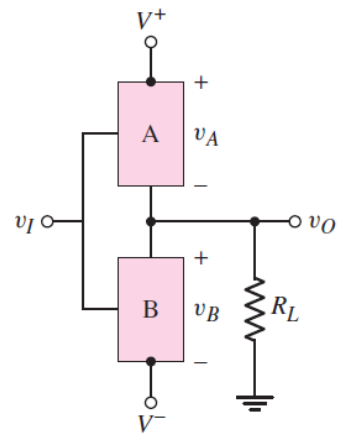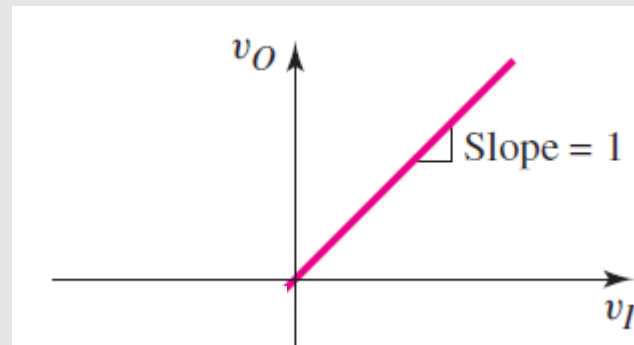Current supplied from V^+ to load R_L through A




Class B operation (Ideal)

- Complementary pair of electronic devices (NMOS and PMOS)
- Device A: NMOS ; Device B: PMOS

- Output is at drain (v_O) Note: Source is connected together

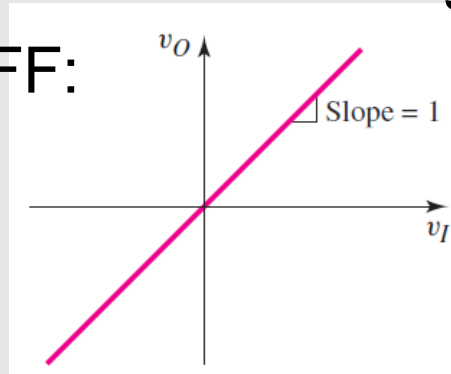- Case 1: $v_I = 0$: Both devices are OFF:
Zero bias currents: $v_O = 0$







- Case 2: $v_I > 0$: Device A is ON
Device B is OFF

Current supplied from V^+ to load R_L through A





- **Case 3:** $v_I < 0$: Device B is ON
Device A is OFF

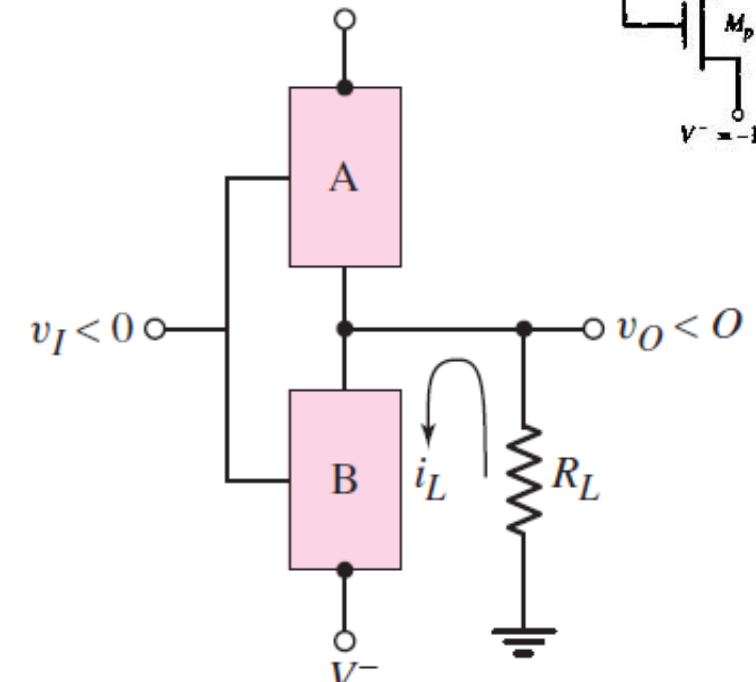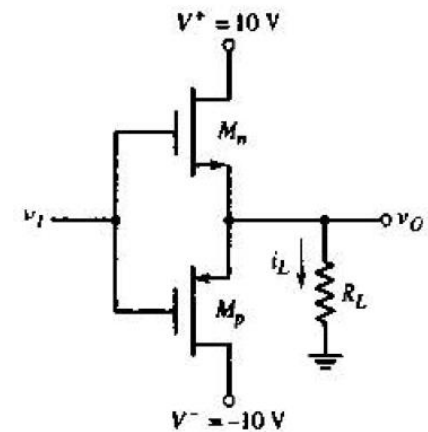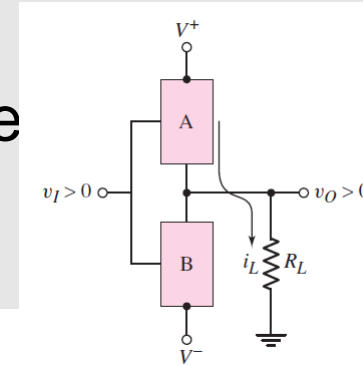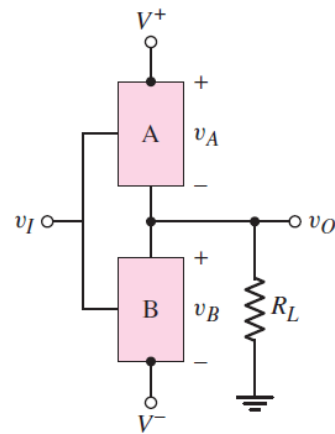Current supplied from V^- to load R_L through
(**Sinking current from load**: Output negativ



Class B operation (Practical) – Threshold Cross over distortion


- Threshold voltages :

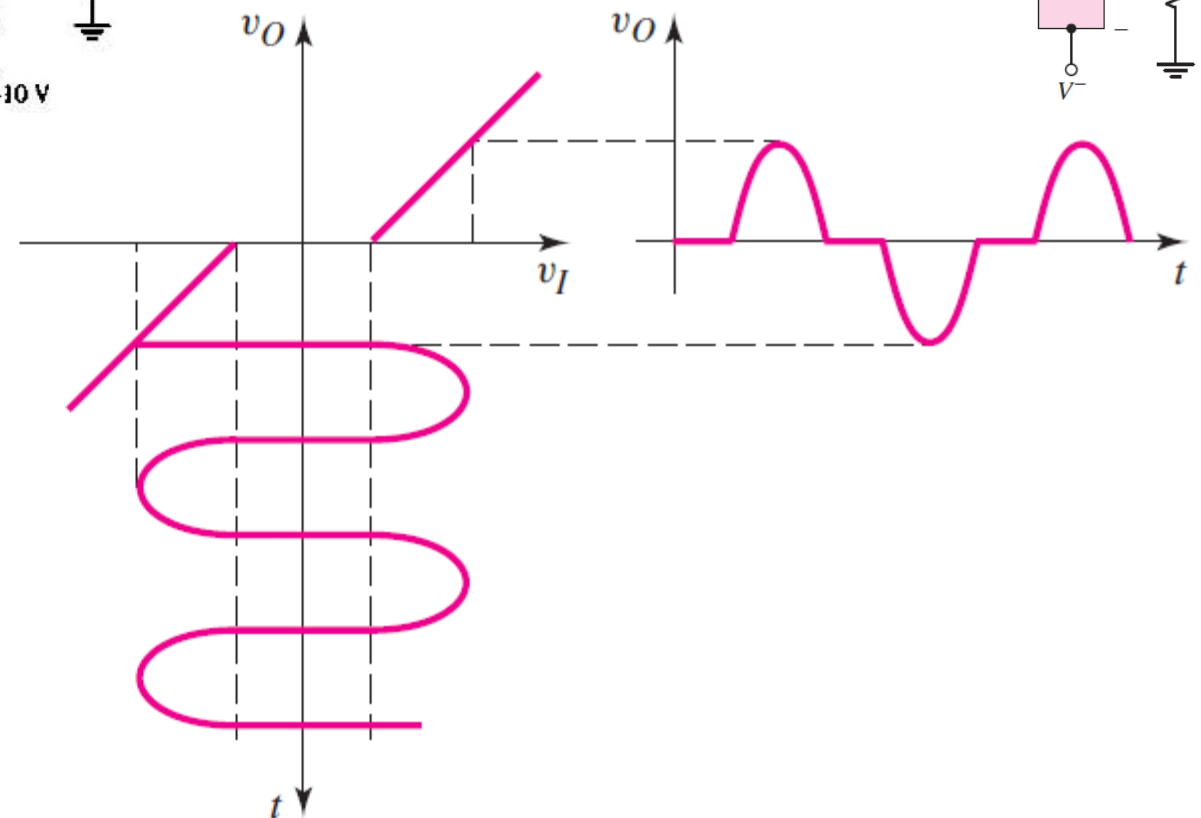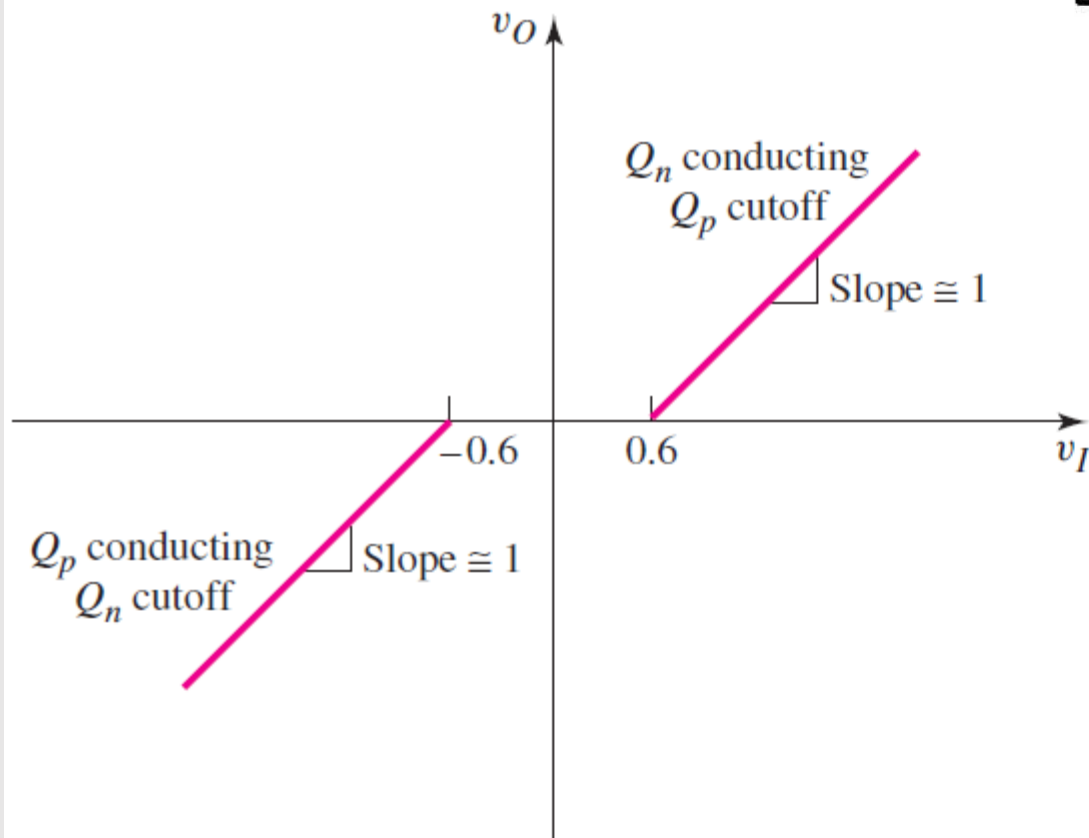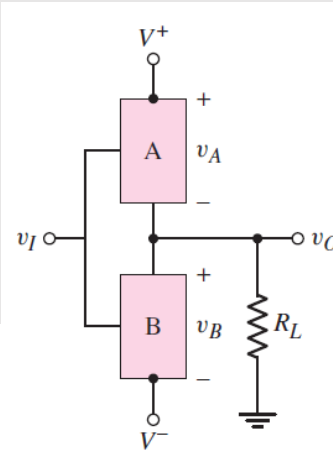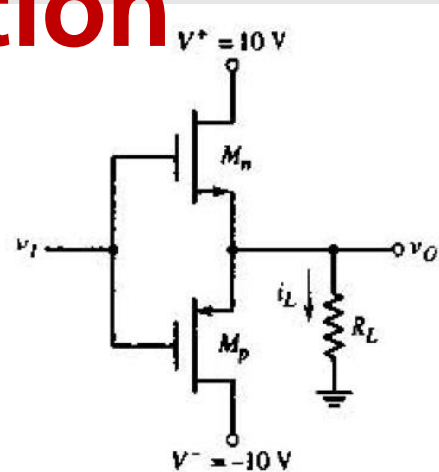

- Crossover distortion can be virtually eliminated by biasing both PMOS and NMOS with a small quiescent drain current when v_I is zero. The crossover distortion effect can also be minimized with an op-amp used in a feedback configuration.

Conversion efficiency of Class B MOSFET amplifier

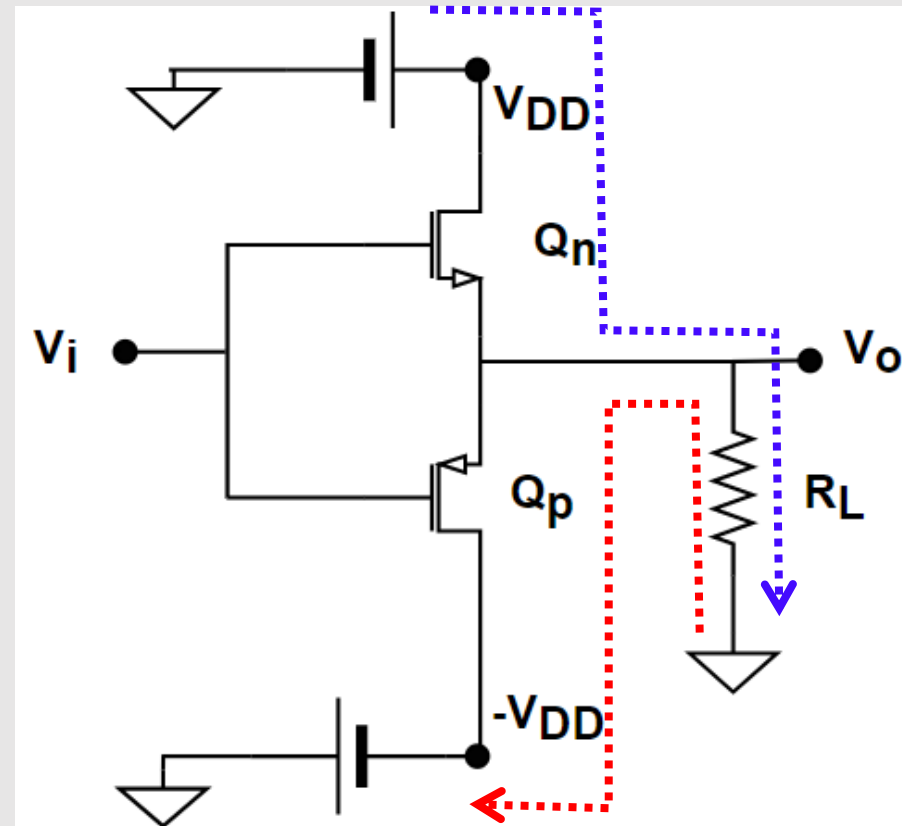- as $\omega t = 2\pi f t = 2\pi \cdot \frac{1}{T} \cdot t$ Based on t , ωt will be the respective angle
- **At $0 \leq \omega t \leq \pi : v_i \geq 0$; NMOS is ON; PMOS is OFF**
- **At $\pi \leq \omega t \leq 2\pi : v_i \leq 0$; NMOS is OFF; PMOS is ON**
- Output of class B amplifier: $v_o = V_P \sin \omega t$ with V_P (maximum possible output is V_{DD})



Conversion efficiency of Class B MOSFET amplifier


- $v_o = V_P \sin \omega t$
- **Consider only NMOS Q_n:**
- $0 \leq \omega t \leq \pi : v_i \geq 0$: NMOS ON

Sinusoidal Drain current: $i_{Dn} = \frac{v_o}{R_L} = \frac{V_P}{R_L} \sin \omega t$

$$V_{DSn} = V_{DD} - v_o = V_{DD} - V_P \sin \omega t$$

At $0 \leq \omega t \leq \pi : v_i \geq 0$; NMOS is ON; PMOS is OFF

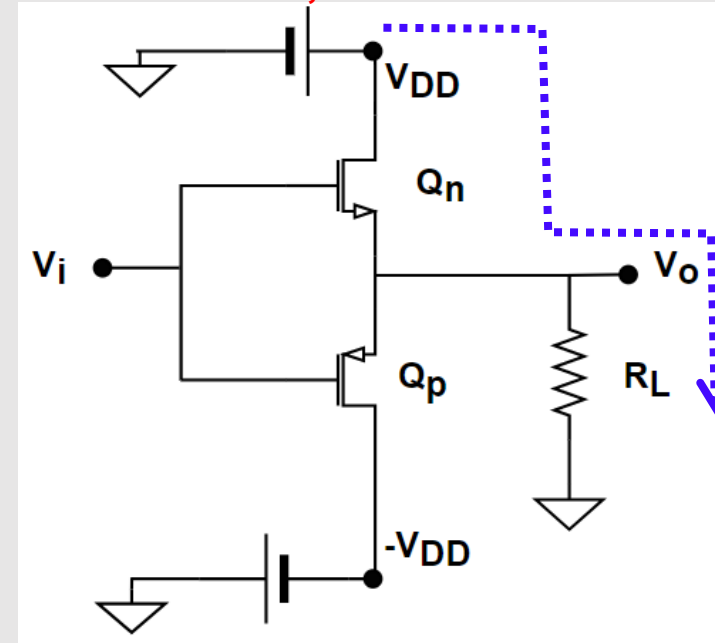At $\pi \leq \omega t \leq 2\pi : v_i \leq 0$; NMOS is OFF; PMOS is ON



Conversion efficiency of Class B MOSFET amplifier

- $v_o = V_P \sin \omega t$
- **Consider only NMOS Q_n :**
- $0 \leq \omega t \leq \pi : v_i \geq 0$: NMOS ON

Sinusoidal Drain current: $i_{Dn} = \frac{v_o}{R_L} = \frac{V_P}{R_L} \sin \omega t$

$$V_{DSn} = V_{DD} - v_o = V_{DD} - V_P \sin \omega t$$


Instantaneous value of power dissipation in NMOS Q_n :

$$P_{Qn(inst)} = V_{DSn} i_{Dn}$$

$$P_{Qn(inst)} =$$

At $0 \leq \omega t \leq \pi : v_i \geq 0$; NMOS is ON; PMOS is OFF

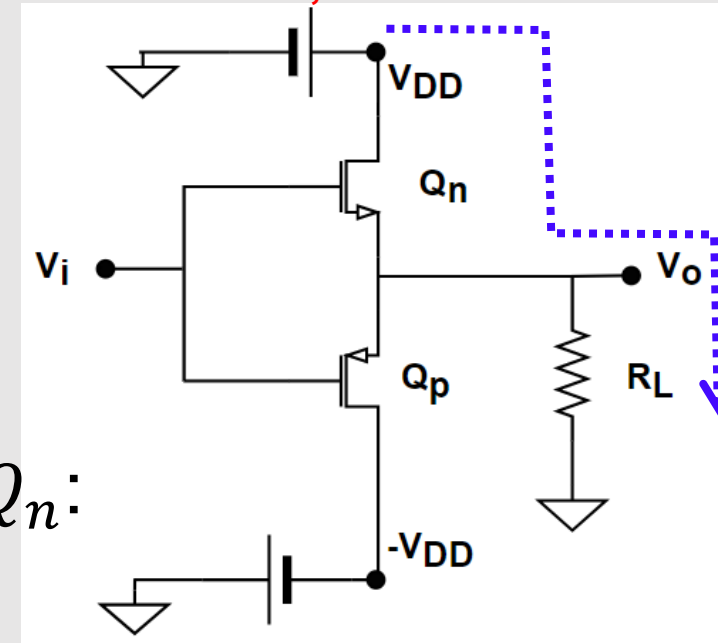At $\pi \leq \omega t \leq 2\pi : v_i \leq 0$; NMOS is OFF; PMOS is ON



Conversion efficiency of Class B MOSFET amplifier

- $v_o = V_P \sin \omega t$
- **Consider only NMOS Q_n :**
- $0 \leq \omega t \leq \pi : v_i \geq 0$: NMOS ON

Sinusoidal Drain current: $i_{Dn} = \frac{v_o}{R_L} = \frac{V_P}{R_L} \sin \omega t$

$$V_{DSn} = V_{DD} - v_o = V_{DD} - V_P \sin \omega t$$

Instantaneous value of power dissipation in NMOS Q_n :


$$P_{Qn(inst)} = V_{DSn} i_{Dn}$$

$$P_{Qn(inst)} = (V_{DD} - V_P \sin \omega t) \frac{V_P}{R_L} \sin \omega t = \frac{V_{DD} V_P}{R_L} \sin \omega t - \frac{V_P^2}{R_L} \sin^2 \omega t$$

- $\pi \leq \omega t \leq 2\pi : v_i \leq 0$; NMOS is OFF : $P_{Qn(inst)} = 0$

At $0 \leq \omega t \leq \pi : v_i \geq 0$; NMOS is ON; PMOS is OFF

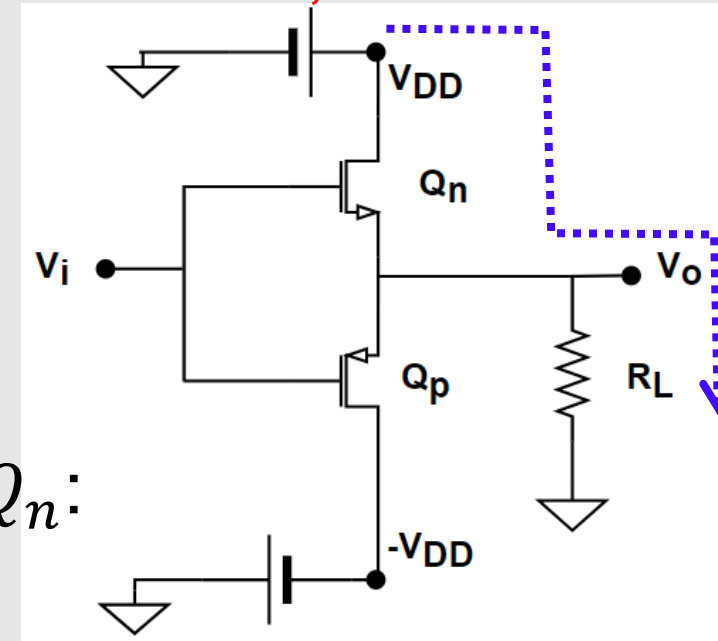At $\pi \leq \omega t \leq 2\pi : v_i \leq 0$; NMOS is OFF; PMOS is ON



Conversion efficiency of Class B MOSFET amplifier

- $v_O = V_P \sin \omega t$

- Consider only NMOS Q_n:

- $0 \leq \omega t \leq \pi : v_i \geq 0$: NMOS ON

At $0 \leq \omega t \leq \pi : v_i \geq 0$; NMOS is ON; PMOS is OFF

At $\pi \leq \omega t \leq 2\pi : v_i \leq 0$; NMOS is OFF; PMOS is ON


$$i_{Dn} = \frac{v_O}{R_L} = \frac{V_P}{R_L} \sin \omega t \quad ; \quad V_{DSn} = V_{DD} - V_P \sin \omega t$$

$$P_{Qn(inst)} = \frac{V_{DD}V_P}{R_L} \sin \omega t - \frac{V_P^2}{R_L} \sin^2 \omega t \quad ; \quad P_{Qn(inst)} = 0 \quad (\pi \leq \omega t \leq 2\pi)$$

$$\text{Average power } P_{Qn} = \frac{1}{2\pi} \int_0^{2\pi} P_{Qn(inst)} d(\omega t)$$

$$= \frac{1}{2\pi} \int_0^{\pi} P_{Qn(inst)} d(\omega t) + \frac{1}{2\pi} \int_{\pi}^{2\pi} P_{Qn(inst)} d(\omega t)$$

=

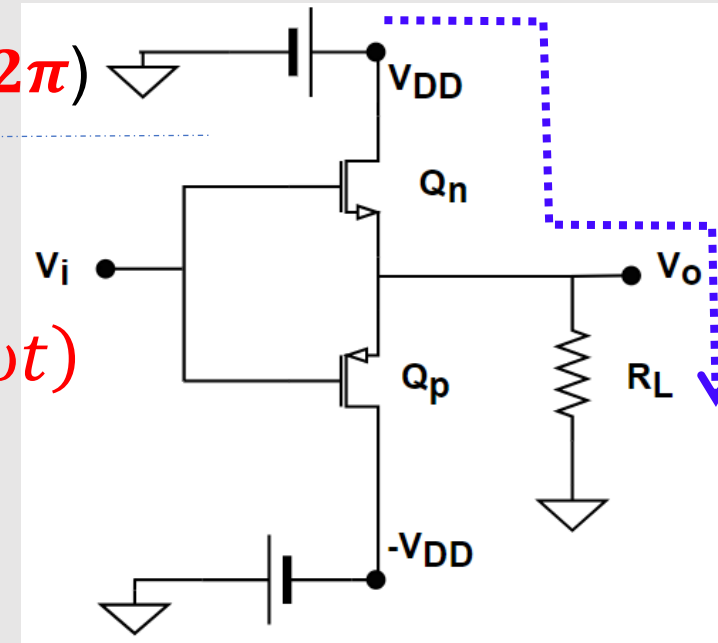

Conversion efficiency of Class B MOSFET amplifier

- $v_O = V_P \sin \omega t$

- Consider only NMOS Q_n:

- $0 \leq \omega t \leq \pi : v_i \geq 0$: NMOS ON

$$i_{Dn} = \frac{v_O}{R_L} = \frac{V_P}{R_L} \sin \omega t \quad ; \quad V_{DSn} = V_{DD} - V_P \sin \omega t$$

$$P_{Qn(inst)} = \frac{V_{DD}V_P}{R_L} \sin \omega t - \frac{V_P^2}{R_L} \sin^2 \omega t \quad ; \quad P_{Qn(inst)} = 0 \quad (\pi \leq \omega t \leq 2\pi)$$

$$\text{Average power } P_{Qn} = \frac{1}{2\pi} \int_0^{2\pi} P_{Qn(inst)} d(\omega t)$$


$$= \frac{1}{2\pi} \int_0^{\pi} P_{Qn(inst)} d(\omega t) + \frac{1}{2\pi} \int_{\pi}^{2\pi} P_{Qn(inst)} d(\omega t)$$

$$= \frac{1}{2\pi} \int_0^{\pi} \left(\frac{V_{DD}V_P}{R_L} \sin \omega t - \frac{V_P^2}{R_L} \sin^2 \omega t \right) d(\omega t)$$

$$= \frac{1}{2\pi} \left[\frac{V_{DD}V_P}{R_L} \int_0^{\pi} \sin \omega t d(\omega t) - \frac{V_P^2}{R_L} \int_0^{\pi} (\sin^2 \omega t) d(\omega t) \right]$$

At $0 \leq \omega t \leq \pi : v_i \geq 0$; NMOS is ON; PMOS is OFF

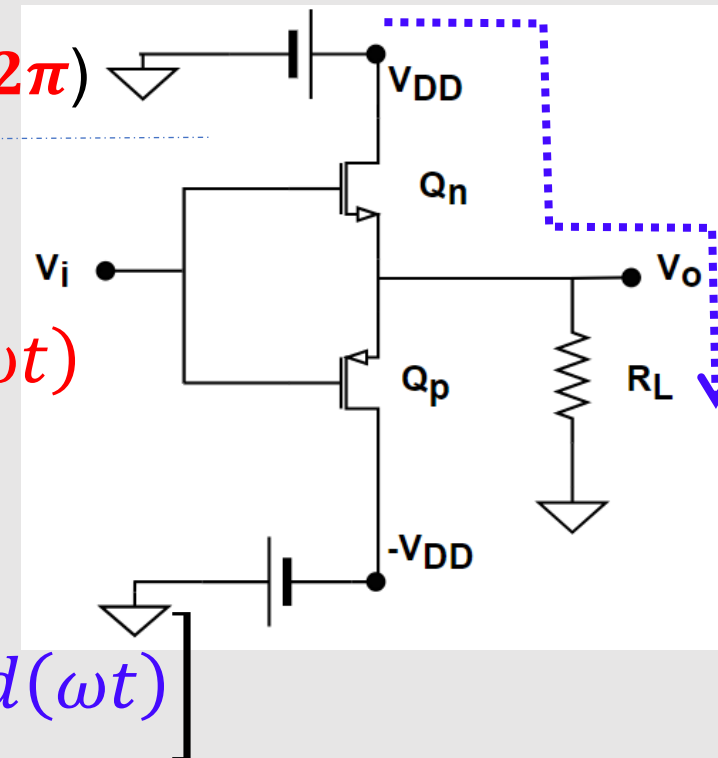At $\pi \leq \omega t \leq 2\pi : v_i \leq 0$; NMOS is OFF; PMOS is ON



Conversion efficiency of Class B MOSFET amplifier

- $v_O = V_P \sin \omega t$

- Consider only NMOS Q_n:

- $0 \leq \omega t \leq \pi : v_i \geq 0$: NMOS ON $i_{Dn} = \frac{v_O}{R_L} = \frac{V_P}{R_L} \sin \omega t$; $V_{DSn} = V_{DD} - V_P \sin \omega t$

$$P_{Qn(inst)} = \frac{V_{DD}V_P}{R_L} \sin \omega t - \frac{V_P^2}{R_L} \sin^2 \omega t ; P_{Qn(inst)} = 0 \quad (\pi \leq \omega t \leq 2\pi)$$


$$\text{Avg } P_{Qn} = \frac{1}{2\pi} \left[\frac{V_{DD}V_P}{R_L} \int_0^\pi \sin \omega t d(\omega t) - \frac{V_P^2}{R_L} \int_0^\pi (\sin^2 \omega t) d(\omega t) \right]$$

$$\text{Let } \theta = \omega t \quad \int_0^\pi \sin \theta d(\theta) = -\cos \theta \Big|_0^\pi =$$

$$\int_0^\pi \sin^2 \theta d(\theta) =$$

At $0 \leq \omega t \leq \pi : v_i \geq 0$; NMOS is ON; PMOS is OFF

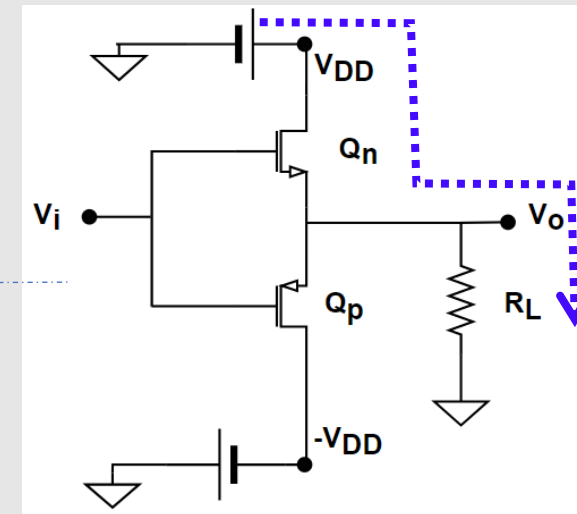At $\pi \leq \omega t \leq 2\pi : v_i \leq 0$; NMOS is OFF; PMOS is ON



Conversion efficiency of Class B MOSFET amplifier

- $v_O = V_P \sin \omega t$

- Consider only NMOS Q_n:

- $0 \leq \omega t \leq \pi : v_i \geq 0$: NMOS ON $i_{Dn} = \frac{v_O}{R_L} = \frac{V_P}{R_L} \sin \omega t$; $V_{DSn} = V_{DD} - V_P \sin \omega t$

$$P_{Qn(inst)} = \frac{V_{DD}V_P}{R_L} \sin \omega t - \frac{V_P^2}{R_L} \sin^2 \omega t ; P_{Qn(inst)} = 0 \quad (\pi \leq \omega t \leq 2\pi)$$


$$\text{Avg } P_{Qn} = \frac{1}{2\pi} \left[\frac{V_{DD}V_P}{R_L} \int_0^\pi \sin \omega t d(\omega t) - \frac{V_P^2}{R_L} \int_0^\pi (\sin^2 \omega t) d(\omega t) \right]$$

$$\text{Let } \theta = \omega t \quad \int_0^\pi \sin \theta d(\theta) = -\cos \theta \Big|_0^\pi = -[\cos(\pi) - \cos 0] = -(-1 - 1) = 2$$

$$\begin{aligned} \int_0^\pi \sin^2 \theta d(\theta) &= \int_0^\pi \frac{1 - \cos(2\theta)}{2} d(\theta) = \frac{1}{2} \int_0^\pi d(\theta) - \frac{1}{2} \int_0^\pi \cos(2\theta) d(\theta) \\ &= \frac{1}{2} \cdot (\theta) \Big|_0^\pi - \frac{1}{2} \cdot \frac{\sin 2\theta}{2} \Big|_0^\pi = \frac{\pi}{2} - \frac{1}{4} (\sin(2\pi) - \sin 0) = \frac{\pi}{2} - 0 = \frac{\pi}{2} \end{aligned}$$

At $0 \leq \omega t \leq \pi : v_i \geq 0$; NMOS is ON; PMOS is OFF

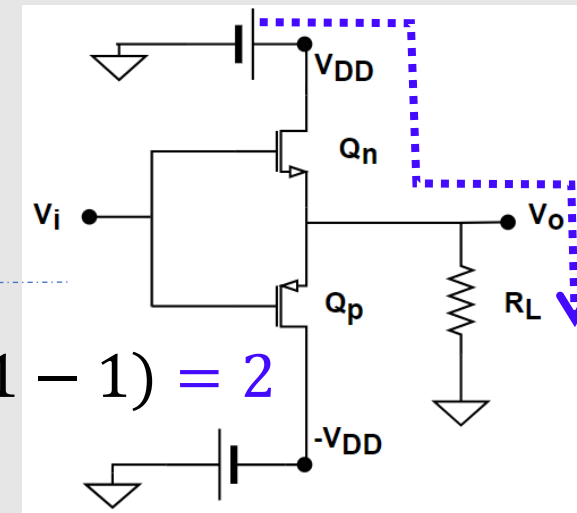At $\pi \leq \omega t \leq 2\pi : v_i \leq 0$; NMOS is OFF; PMOS is ON



Conversion efficiency of Class B MOSFET amplifier

- $v_O = V_P \sin \omega t$

- Consider only NMOS Q_n:

- $0 \leq \omega t \leq \pi : v_i \geq 0$: NMOS ON


$$i_{Dn} = \frac{v_O}{R_L} = \frac{V_P}{R_L} \sin \omega t \quad ; \quad V_{DSn} = V_{DD} - V_P \sin \omega t$$

$$P_{Qn(inst)} = \frac{V_{DD}V_P}{R_L} \sin \omega t - \frac{V_P^2}{R_L} \sin^2 \omega t \quad ; \quad P_{Qn(inst)} = 0 \quad (\pi \leq \omega t \leq 2\pi)$$

$$\begin{aligned} \text{Avg } P_{Qn} &= \frac{1}{2\pi} \left[\frac{V_{DD}V_P}{R_L} \int_0^\pi \sin \omega t d(\omega t) - \frac{V_P^2}{R_L} \int_0^\pi (\sin^2 \omega t) d(\omega t) \right] \\ &= \frac{1}{2\pi} \left[\frac{V_{DD}V_P}{R_L} (2) - \frac{V_P^2}{R_L} \left(\frac{\pi}{2} \right) \right] \\ &= \end{aligned}$$

At $0 \leq \omega t \leq \pi : v_i \geq 0$; NMOS is ON; PMOS is OFF

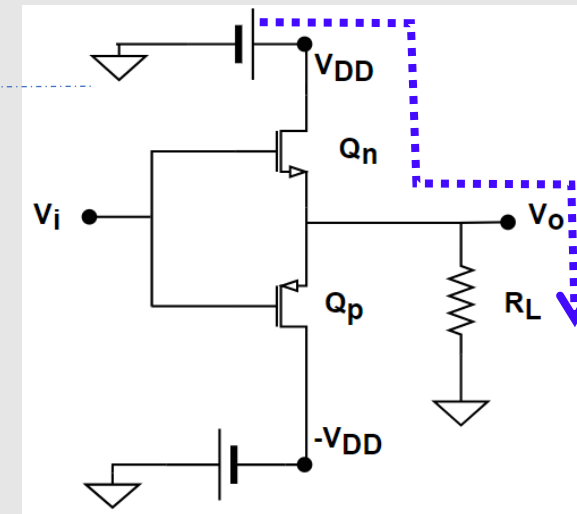At $\pi \leq \omega t \leq 2\pi : v_i \leq 0$; NMOS is OFF; PMOS is ON



Conversion efficiency of Class B MOSFET amplifier

- $v_O = V_P \sin \omega t$

- Consider only NMOS Q_n:

- $0 \leq \omega t \leq \pi : v_i \geq 0$: NMOS ON

At $0 \leq \omega t \leq \pi : v_i \geq 0$; NMOS is ON; PMOS is OFF

At $\pi \leq \omega t \leq 2\pi : v_i \leq 0$; NMOS is OFF; PMOS is ON

$$i_{Dn} = \frac{v_O}{R_L} = \frac{V_P}{R_L} \sin \omega t \quad ; \quad V_{DSn} = V_{DD} - V_P \sin \omega t$$


$$P_{Qn(inst)} = \frac{V_{DD}V_P}{R_L} \sin \omega t - \frac{V_P^2}{R_L} \sin^2 \omega t \quad ; \quad P_{Qn(inst)} = 0 \quad (\pi \leq \omega t \leq 2\pi)$$

$$\text{Avg } P_{Qn} = \frac{1}{2\pi} \left[\frac{V_{DD}V_P}{R_L} \int_0^\pi \sin \omega t d(\omega t) - \frac{V_P^2}{R_L} \int_0^\pi (\sin^2 \omega t) d(\omega t) \right]$$

$$= \frac{1}{2\pi} \left[\frac{V_{DD}V_P}{R_L} (2) - \frac{V_P^2}{R_L} \left(\frac{\pi}{2} \right) \right]$$

$$= \frac{V_{DD}V_P}{R_L\pi} - \frac{V_P^2}{4R_L}$$

$$\text{At max power: } \left. \frac{\partial P_{Qn}}{\partial V_P} \right|_{P_{max}} = 0$$

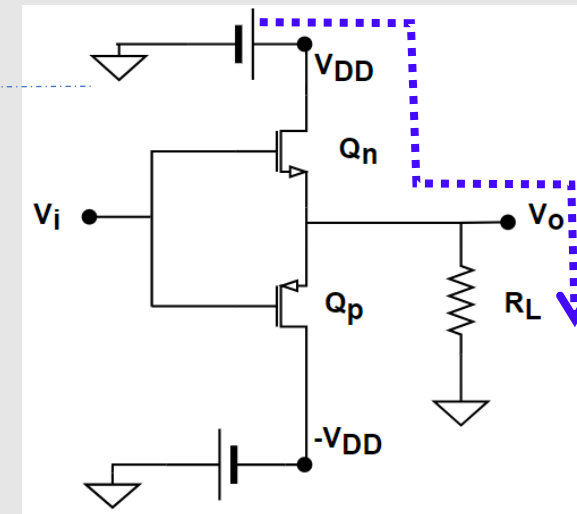

Example: If y has maxima,

$$\text{At } \left. \frac{\partial y}{\partial x} \right|_{y_{max}} = 0$$

Conversion efficiency of Class B MOSFET amplifier

- $v_o = V_P \sin \omega t$

- Consider only NMOS Qn:

- $0 \leq \omega t \leq \pi : v_i \geq 0$: NMOS ON $i_{Dn} = \frac{v_o}{R_L} = \frac{V_P}{R_L} \sin \omega t$; $V_{DSn} = V_{DD} - V_P \sin \omega t$

$$P_{Qn(inst)} = \frac{V_{DD}V_P}{R_L} \sin \omega t - \frac{V_P^2}{R_L} \sin^2 \omega t ; P_{Qn(inst)} = 0 \quad (\pi \leq \omega t \leq 2\pi)$$

$$\text{Avg } P_{Qn} = \frac{V_{DD}V_P}{R_L\pi} - \frac{V_P^2}{4R_L}$$

Note: $\frac{\partial P_{Qn}}{\partial V_P} = \frac{V_{DD}}{R_L\pi} - \frac{2V_P}{4R_L}$

At max power: $\left. \frac{\partial P_{Qn}}{\partial V_P} \right|_{P \text{ max}} = 0$


$$\frac{V_{DD}}{R_L\pi} - \frac{2V_P}{4R_L} = 0 \quad \text{On rearranging: } V_P = \frac{2V_{DD}}{\pi}$$

Max power: when $V_P = \frac{2V_{DD}}{\pi}$

$$P_{Qn(max)} =$$

At $0 \leq \omega t \leq \pi : v_i \geq 0$; NMOS is ON; PMOS is OFF

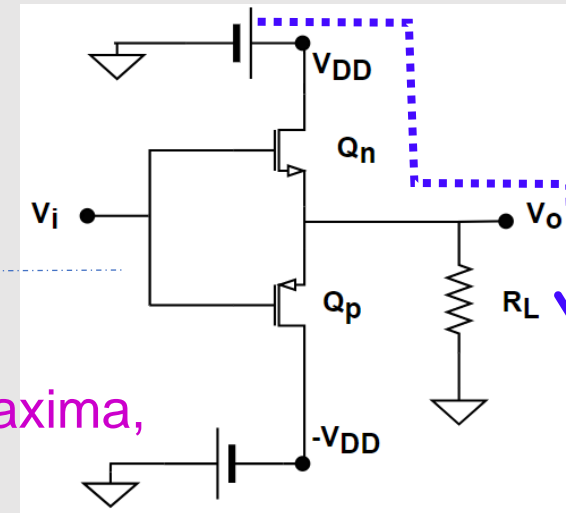At $\pi \leq \omega t \leq 2\pi : v_i \leq 0$; NMOS is OFF; PMOS is ON



Example: If y has maxima,
At $\left. \frac{\partial y}{\partial x} \right|_{y \text{ max}} = 0$

Conversion efficiency of Class B MOSFET amplifier

- $v_o = V_P \sin \omega t$

- Consider only NMOS Qn:

- $0 \leq \omega t \leq \pi : v_i \geq 0$: NMOS ON $i_{Dn} = \frac{v_o}{R_L} = \frac{V_P}{R_L} \sin \omega t$; $V_{DSn} = V_{DD} - V_P \sin \omega t$

$$P_{Qn(inst)} = \frac{V_{DD}V_P}{R_L} \sin \omega t - \frac{V_P^2}{R_L} \sin^2 \omega t ; P_{Qn(inst)} = 0 \quad (\pi \leq \omega t \leq 2\pi)$$

$$\text{Avg } P_{Qn} = \frac{V_{DD}V_P}{R_L\pi} - \frac{V_P^2}{4R_L}$$

Note: $\frac{\partial P_{Qn}}{\partial V_P} = \frac{V_{DD}}{R_L\pi} - \frac{2V_P}{4R_L}$

At max power: $\left. \frac{\partial P_{Qn}}{\partial V_P} \right|_{P \text{ max}} = 0$


$$\frac{V_{DD}}{R_L\pi} - \frac{2V_P}{4R_L} = 0 \quad \text{On rearranging: } V_P = \frac{2V_{DD}}{\pi}$$

Max power: when $V_P = \frac{2V_{DD}}{\pi}$

$$P_{Qn(max)} = \frac{V_{DD}V_P}{R_L\pi} - \frac{V_P^2}{4R_L} = \frac{V_{DD}}{\pi R_L} \cdot \frac{2V_{DD}}{\pi} - \frac{1}{4R_L} \left(\frac{2V_{DD}}{\pi} \right)^2 = \frac{V_{DD}^2}{\pi^2 R_L}$$

At $0 \leq \omega t \leq \pi : v_i \geq 0$; NMOS is ON; PMOS is OFF

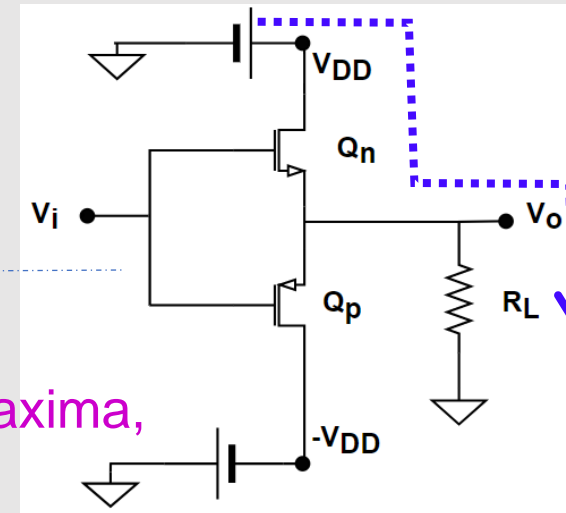At $\pi \leq \omega t \leq 2\pi : v_i \leq 0$; NMOS is OFF; PMOS is ON



Example: If y has maxima,
At $\left. \frac{\partial y}{\partial x} \right|_{y \text{ max}} = 0$

Conversion efficiency of Class B MOSFET amplifier

- $v_o = V_P \sin \omega t$

- Consider only NMOS Qn:

- $0 \leq \omega t \leq \pi : v_i \geq 0$: NMOS ON $i_{Dn} = \frac{v_o}{R_L} = \frac{V_P}{R_L} \sin \omega t$; $V_{DSn} = V_{DD} - V_P \sin \omega t$

$$P_{Qn(inst)} = \frac{V_{DD}V_P}{R_L} \sin \omega t - \frac{V_P^2}{R_L} \sin^2 \omega t ; P_{Qn(inst)} = 0 \quad (\pi \leq \omega t \leq 2\pi)$$

$$\text{Avg } P_{Qn} = \frac{V_{DD}V_P}{R_L\pi} - \frac{V_P^2}{4R_L}; \text{ Max power: when } V_P = \frac{2V_{DD}}{\pi} : P_{Qn(max)} = \frac{V_{DD}^2}{\pi^2 R_L}$$


$$\text{Average current: } i_{Dn(avg)} = \frac{1}{2\pi} \left[\int_0^\pi \frac{V_P}{R_L} \sin \omega t d(\omega t) + \int_\pi^{2\pi} (0) d(\omega t) \right]$$

$$= \frac{1}{2\pi} \cdot \frac{V_P}{R_L} (2) = \frac{V_P}{\pi R_L}$$

$$\begin{aligned} \int_0^\pi \sin \theta d(\theta) &= -\cos \theta \Big|_0^\pi \\ &= -[\cos(\pi) - \cos 0] = -(-1 - 1) \\ &= 2 \end{aligned}$$

At $0 \leq \omega t \leq \pi : v_i \geq 0$; NMOS is ON; PMOS is OFF

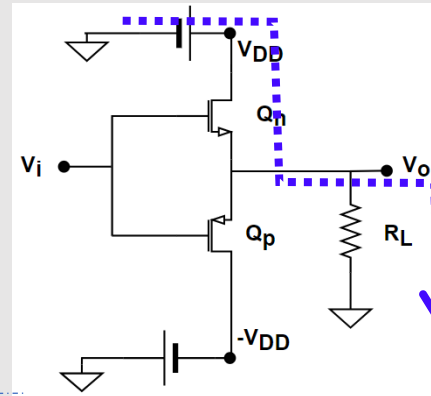At $\pi \leq \omega t \leq 2\pi : v_i \leq 0$; NMOS is OFF; PMOS is ON



Conversion efficiency of Class B MOSFET amplifier

- $v_O = V_P \sin \omega t$

- Consider only NMOS Q_n:

- $0 \leq \omega t \leq \pi : v_i \geq 0$: NMOS ON $i_{Dn} = \frac{v_O}{R_L} = \frac{V_P}{R_L} \sin \omega t$; $V_{DSn} = V_{DD} - V_P \sin \omega t$

$$P_{Qn(inst)} = \frac{V_{DD}V_P}{R_L} \sin \omega t - \frac{V_P^2}{R_L} \sin^2 \omega t ; P_{Qn(inst)} = 0 \quad (\pi \leq \omega t \leq 2\pi)$$

$$\text{Avg } P_{Qn} = \frac{V_{DD}V_P}{R_L\pi} - \frac{V_P^2}{4R_L}; \text{ Max power: when } V_P = \frac{2V_{DD}}{\pi} : P_{Qn(max)} = \frac{V_{DD}^2}{\pi^2 R_L}$$


$$\text{Average current: } i_{Dn(avg)} = \frac{V_P}{\pi R_L}$$

Consider only PMOS Q_p: $\pi \leq \omega t \leq 2\pi : v_i \leq 0$: PMOS ON (through $-V_{DD}$)

$$P_{Qp(max)} = \frac{V_{DD}^2}{\pi^2 R_L} \quad \text{and avg current through } Q_p: i_{Dp(avg)} = \frac{V_P}{\pi R_L}$$

At $0 \leq \omega t \leq \pi : v_i \geq 0$; NMOS is ON; PMOS is OFF

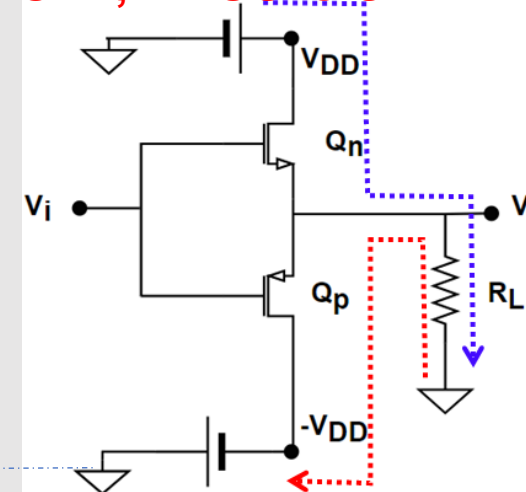At $\pi \leq \omega t \leq 2\pi : v_i \leq 0$; NMOS is OFF; PMOS is ON



Conversion efficiency of Class B MOSFET amplifier

- $v_o = V_P \sin \omega t$

- Consider only NMOS Qn:

- $0 \leq \omega t \leq \pi : v_i \geq 0$: NMOS ON $i_{Dn} = \frac{v_o}{R_L} = \frac{V_P}{R_L} \sin \omega t$; $V_{DSn} = V_{DD} - V_P \sin \omega t$

$$P_{Qn(inst)} = \frac{V_{DD}V_P}{R_L} \sin \omega t - \frac{V_P^2}{R_L} \sin^2 \omega t ; P_{Qn(inst)} = 0 \quad (\pi \leq \omega t \leq 2\pi)$$

$$\text{Avg } P_{Qn} = \frac{V_{DD}V_P}{R_L\pi} - \frac{V_P^2}{4R_L}; \text{ Max power: when } V_P = \frac{2V_{DD}}{\pi} : P_{Qn(max)} = \frac{V_{DD}^2}{\pi^2 R_L}$$

$$\text{Average current: } i_{Dn(avg)} = \frac{V_P}{\pi R_L}$$

Consider only PMOS Qp: $\pi \leq \omega t \leq 2\pi : v_i \leq 0$: PMOS ON (through $-V_{DD}$)


$$P_{Qp(max)} = \frac{V_{DD}^2}{\pi^2 R_L} \text{ and avg current through } Q_p: i_{Dp(avg)} = \frac{V_P}{\pi R_L}$$

$$\text{Average power supplied by 2 sources: } P_S = 2V_{DD} \left(\frac{V_P}{\pi R_L} \right) \text{ (Voltage x current)}$$

$$\text{Average power delivered to load: } P_L = \frac{1}{2} \frac{V_P^2}{R_L}$$

At $0 \leq \omega t \leq \pi : v_i \geq 0$; NMOS is ON; PMOS is OFF

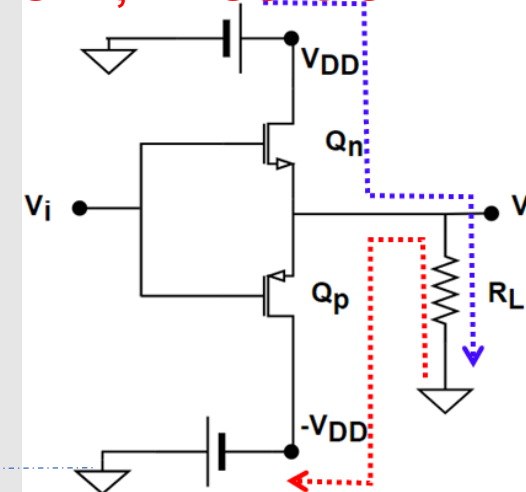At $\pi \leq \omega t \leq 2\pi : v_i \leq 0$; NMOS is OFF; PMOS is ON




Conversion efficiency of Class B MOSFET amplifier

Average power supplied by 2 sources: $P_S = 2V_{DD} \left(\frac{V_P}{\pi R_L} \right)$ (Voltage x current)

Average power delivered to load: $P_L = \frac{1}{2} \frac{V_P^2}{R_L}$

Power conversion efficiency: $\eta = \frac{P_L}{P_S}$
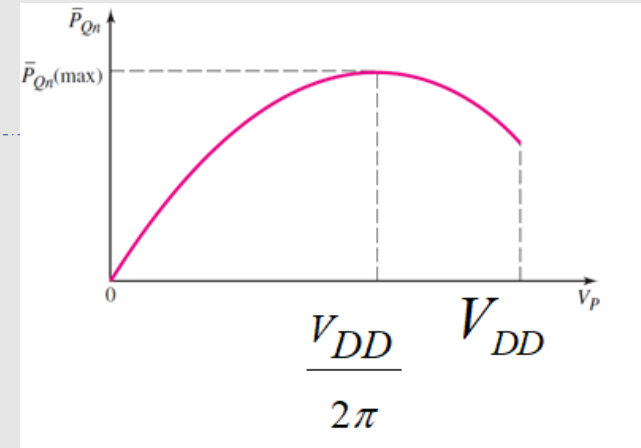
$$\eta = \frac{1}{2} \frac{V_P^2}{R_L} \cdot \frac{1}{2V_{DD} \left(\frac{V_P}{\pi R_L} \right)} = \frac{\pi}{4} \cdot \frac{V_P}{V_{DD}}$$



Max power conversion efficiency: Ideally when $V_P = V_{DD}$

$$\eta_{max} = \frac{\pi}{4} \cdot \frac{V_P}{V_{DD}} = \frac{\pi}{4} = \frac{3.1416}{4} \times 100\% = 78.5\% \quad \text{and} \quad P_{Lmax} = \frac{1}{2} \cdot \frac{V_{DD}^2}{R_L}$$

But, we know that $V_P = \frac{2V_{DD}}{\pi}$ is the maximum possible value:

$$\eta_{max} = \frac{\pi}{4} \cdot \frac{V_P}{V_{DD}} = \frac{\pi}{4} \cdot \frac{2V_{DD}}{\pi V_{DD}} \times 100\% = 50\%$$