

C1 slot

Monday 3A2 key


STUDENT'S NAME

CLASS


SUBJECT

ROLL NO

DATE

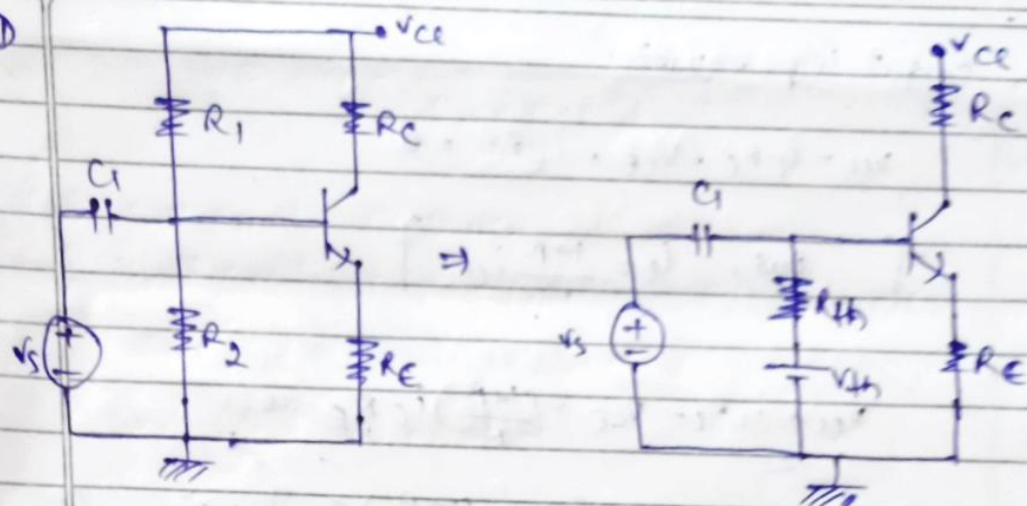

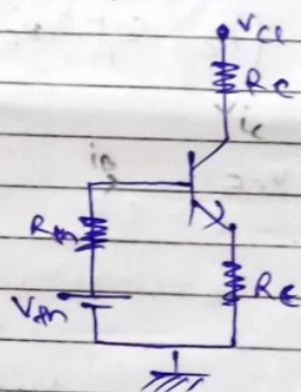(a) DC analysis  $\Rightarrow$  short circuit AC sources & Capacitors are open circuited.



$$\therefore V_{th} = \frac{R_2 V_{ce}}{R_1 + R_2}$$

$$R_{th} = \frac{R_1 R_2}{R_1 + R_2}$$

input loop equation,

$$V_{th} - i_B R_{th} - V_{BE} - i_E R_E = 0 \quad (\because i_E = (1 + \beta) i_B)$$

$$V_{th} - i_B R_{th} - V_{BE} - (1 + \beta) i_B R_E = 0$$

$$i_B = \frac{V_{th} - V_{BE}}{R_{th} + (1 + \beta) R_E}$$

Output loop equation,

$$V_{CC} - i_C R_C - V_{CE} - i_E R_E = 0$$

$$\left[ \text{But, } i_E = \frac{1+\beta}{\beta} i_C \right]$$


$$V_{CC} - i_C R_C - V_{CE} - \left(\frac{1+\beta}{\beta}\right) i_C R_E = 0$$

$$V_{CC} - V_{CE} - i_C \left[ R_C + \left(\frac{1+\beta}{\beta}\right) R_E \right] = 0 \quad \text{--- (1)}$$

Q-point,

$$V_{CE} = 0 \Rightarrow i_C = \frac{V_{CC}}{\left[ R_C + \left(\frac{1+\beta}{\beta}\right) R_E \right]}$$

$$i_C = 0 \Rightarrow V_{CC} = V_{CE}$$

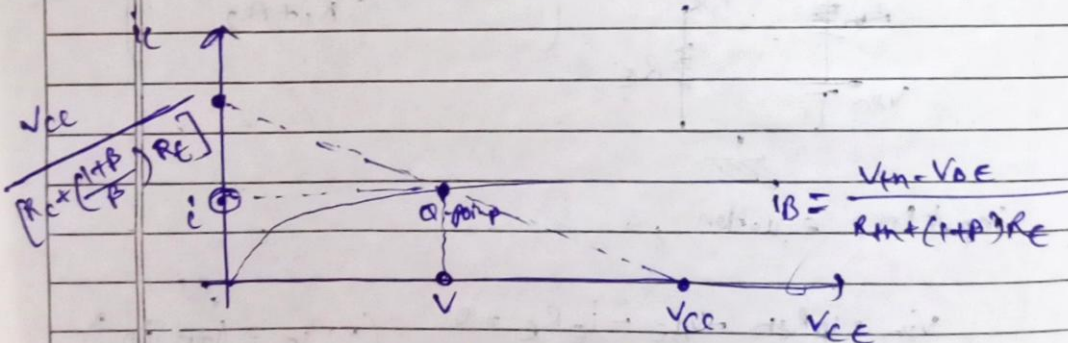

$$i = \beta I_B \Rightarrow i = \frac{\beta (V_{th} - V_{BE})}{(R_{th} + (1+\beta) R_E)}$$

Substitute 'i' in eq(1),

$$V_{CC} - V = i \left( R_C + \left(\frac{1+\beta}{\beta}\right) R_E \right)$$




STUDENT'S NAME	
CLASS	SUBJECT
ROLL NO.	DATE

$$V = V_{CC} - \frac{\beta(V_{in} - V_{BE})}{(R_{in} + (1+\beta)R_E)} \cdot \left( R_C + \left( \frac{1+\beta}{\beta} \right) R_E \right)$$

(b) Short circuit DC sources  
 Short circuit Coupling Capacitor  
 open circuit load capacitor } AC analysis

Small signal eq. model  $\Rightarrow$

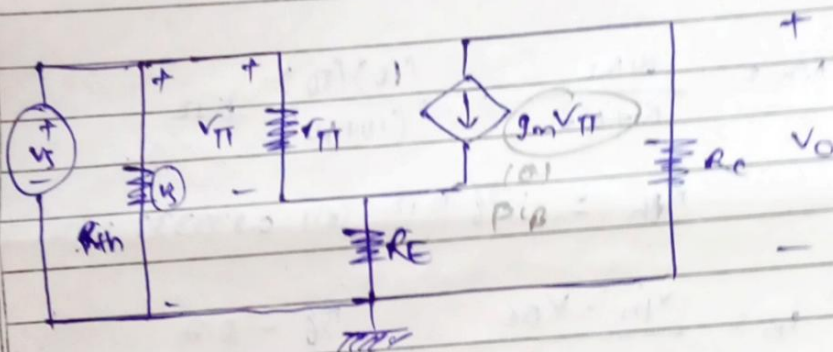

$$i_b = \frac{v_s}{R_{ib}} \rightarrow \text{resistance seen into base.}$$

$$\therefore R_{ib} = r_{\pi} + (1+\beta)R_E$$

$$i_b = \frac{v_s}{(r_{\pi} + (1+\beta)R_E)}$$

$$v_o = -\beta i_b R_C \Rightarrow -\beta \left[ \frac{v_s}{r_{\pi} + (1+\beta)R_E} \right] R_C$$

$$\frac{v_o}{v_s} = \frac{-\beta R_C}{(r_{\pi} + (1+\beta)R_E)} = A_v$$

(c). from (a) & (b)

$$i_B = \frac{V_{Th} - V_{BE}}{R_{Th} + (1+\beta)R_E}$$

$$V_{Th} = \frac{R_2 V_{CC}}{R_1 + R_2} \Rightarrow \frac{10(10)}{(10+50)} = \frac{10(10)}{60}$$

$$V_{Th} = \frac{10}{6} \text{ V (or)} 1.666667 \text{ V}$$

$$R_{Th} = \frac{R_1 R_2}{R_1 + R_2} = \frac{(10)(50)}{(10+50)} \text{ k}\Omega$$

$$R_{Th} = \frac{5}{6} \text{ k}\Omega \text{ (or)} 0.833333 \text{ k}\Omega$$

$$i_B = \frac{V_{Th} - V_{BE}}{R_{Th} + (1+\beta)R_E} = \frac{\frac{10}{6} - 0.7}{\frac{5}{6} + (1+100)(0.4)} \text{ mA}$$
$$= \frac{0.9666667}{41.2333333}$$

$$i_B = 0.0234438165 \text{ mA}$$

$$i_C = \beta i_B \Rightarrow i_C = 2.34438165 \text{ mA}$$

$$r_{\pi} = \frac{V_T}{i_B} \Rightarrow \frac{0.026}{0.0234438165} \text{ k}\Omega$$

$$r_{\pi} = 1.10903444 \text{ k}\Omega$$


$$A_V = \frac{-\beta R_C}{r_{\pi} + (1+\beta)R_E} \quad (\because \text{from (b)})$$

$$= \frac{-(100)(2)}{1.10903444 + (101)0.4}$$

$$= \frac{-200}{41.5090344}$$


$$A_V = -4.8182282$$

(2)

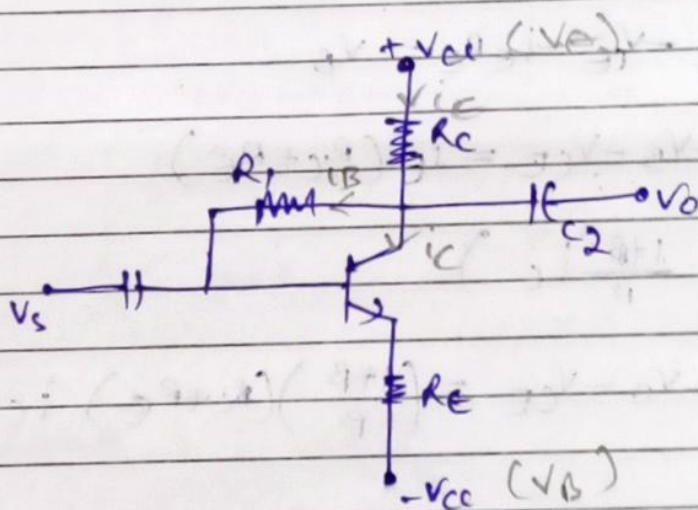

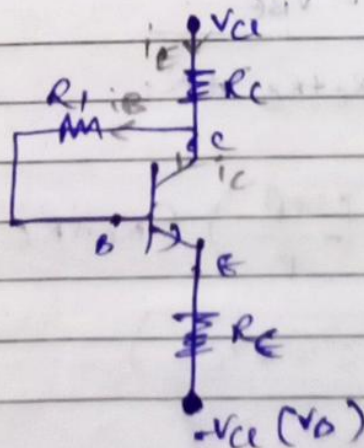(a) DC analysis

(short circuit - AC voltages)  
(open circuit - Capacitors)





loop equation)

$$\Rightarrow V_A - i_E R_E - i_B R_1 - V_{BE} - i_E R_E = V_B$$

$$V_A - V_B - V_{BE} = i_E (R_E + R_E) + i_B R_1$$

$$V_A - V_B - V_{BE} = (1+\beta) i_B (R_E + R_E) + i_B R_1$$

$$i_B = \frac{V_A - V_B - V_{BE}}{(1+\beta)(R_E + R_E) + R_1} \quad \text{--- (1)}$$

$$\Rightarrow V_A - i_E R_E - V_{CE} - i_E R_E = V_B$$

$$V_A - V_B - V_{CE} = i_E (R_E + R_E)$$

$$\left( \because i_E = \frac{1+\beta}{\beta} i_C \right)$$

$$V_A - V_B - V_{CE} = \left( \frac{1+\beta}{\beta} \right) (R_E + R_E) i_C \quad \text{--- (2)}$$

$$\Rightarrow V_A = V_{CE} \quad / \quad V_B = -V_{CC}$$

Substitute in eq (1), (2).

$$i_B = \frac{2V_{CC} - V_{BE}}{(1+\beta)(R_E + R_E) + R_1}$$

$$2V_{CC} - V_{CE} = \left( \frac{1+\beta}{\beta} \right) (R_E + R_E) i_C \quad \text{--- (3)}$$

$$i_C = 0 \Rightarrow \boxed{V_{CE} = 2V_{CC}}$$

STUDENT'S NAME


CLASS

SUBJECT

ROLL NO

DATE
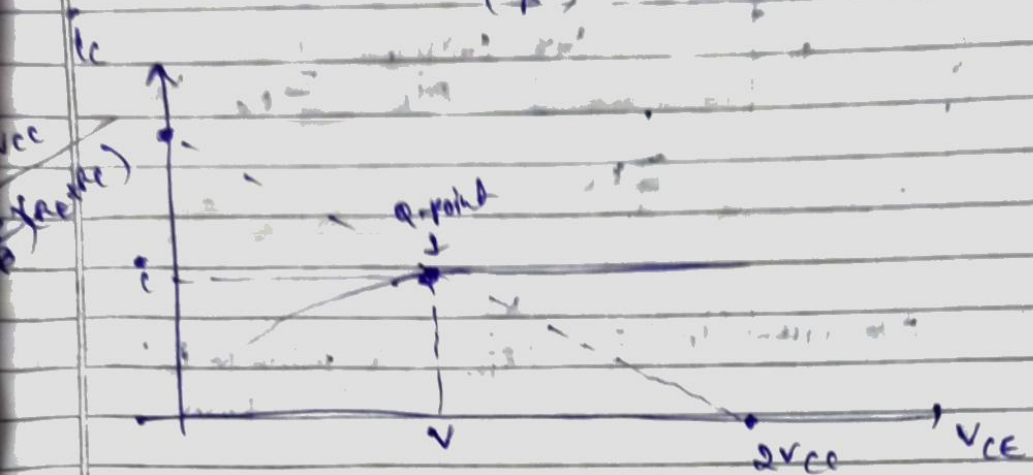
$$V_{CE} = 0 \Rightarrow I_C = \frac{2V_{CC}}{\left(\frac{1+\beta}{\beta}\right)(R_C + R_E)}$$



$$I_B = \frac{2V_{CC} - V_{CE}}{\left(\frac{1+\beta}{\beta}\right)(R_C + R_E) + R_1}$$

$$I_C = \beta I_B \Rightarrow \frac{\beta(2V_{CC} - V_{CE})}{(1+\beta)(R_C + R_E) + R_1} = I$$


Substitute 'I' in eq (3),

$$V \Rightarrow V_{CE} = 2V_{CC} - \left(\frac{1+\beta}{\beta}\right)(R_C + R_E) \left[ \frac{\beta(2V_{CC} - V_{CE})}{(1+\beta)(R_C + R_E) + R_1} \right]$$

(b) short circuit — DC sources, Coupling capacitor

open circuit — Load capacitor

AC  
analysis

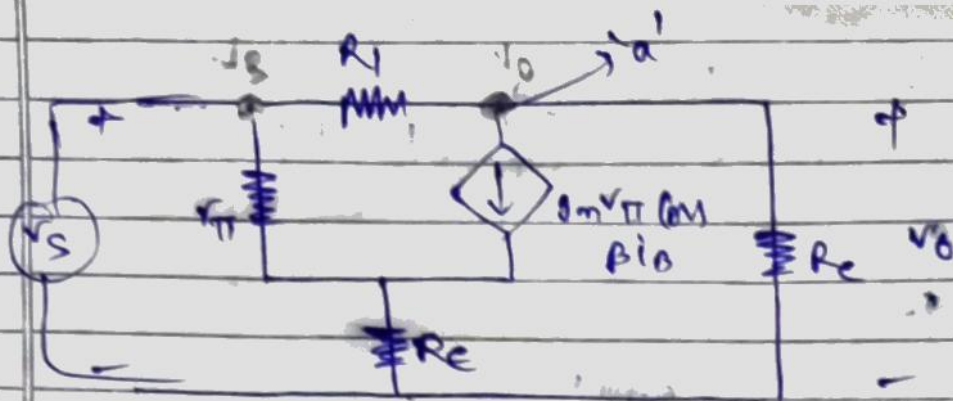

Base Current ( $i_b$ ) =  $\frac{V_s}{R_{ib}}$   $\rightarrow$  resistance looked into base

$$i_b = \frac{V_s}{r_{\pi} + (1 + \beta)R_e}$$

$$g_m V_{\pi} (\approx \beta i_b) = \frac{\beta V_s}{r_{\pi} + (1 + \beta)R_e}$$

KCL at node 'a',

$$\frac{V_s - V_o}{R_1} = g_m V_{\pi} + \frac{V_o}{R_c}$$

$$\frac{V_s - V_o}{R_1} = \frac{\beta V_s}{r_{\pi} + (1 + \beta)R_e} + \frac{V_o}{R_c}$$

$$V_o \left[ \frac{1}{R_c} + \frac{1}{R_1} \right] = -V_s \left[ \frac{\beta}{r_{\pi} + (1 + \beta)R_e} - \frac{1}{R_1} \right]$$

$$V_o \left[ \frac{R_1 + R_c}{R_1 R_c} \right] = -V_s \left[ \frac{\beta R_1 - (r_{\pi} + (1 + \beta)R_e)}{R_1 (r_{\pi} + (1 + \beta)R_e)} \right]$$



$$\frac{V_o}{V_s} = \frac{-[\beta R_1 - (r_{\pi} + (1+\beta)R_e)]R_c}{(R_1 + R_c)[r_{\pi} + (1+\beta)R_e]}$$

$$A_v = \frac{-R_c[\beta R_1 - (r_{\pi} + (1+\beta)R_e)]}{(R_c + R_1)[r_{\pi} + (1+\beta)R_e]}$$

(c) Q-point ( $V, I$ ) ( $\because$  from (a))

$$V = 2V_{cc} - \left(\frac{1+\beta}{\beta}\right)(R_c + R_e) \left[ \frac{\beta(2V_{cc} - V_{BE})}{(1+\beta)(R_c + R_e) + R_1} \right]$$

$$= 2(10) - \left(\frac{101}{100}\right)(11) \left[ \frac{100(20 - 0.7)}{(101)(11) + 100} \right]$$

$$V = 20 - 11.1 \left[ \frac{1930}{1211} \right]$$


$$= 20 - 17.70623581$$

$$V = 2.293724195 \text{ V}$$

$$i = \frac{\beta(2V_{cc} - V_{BE})}{(1+\beta)(R_c + R_e) + R_1} = \frac{100(20 - 0.7)}{(101)(11) + 100}$$

$$= \frac{1930}{1211}$$

$$i = 1.593724195 \text{ mA}$$

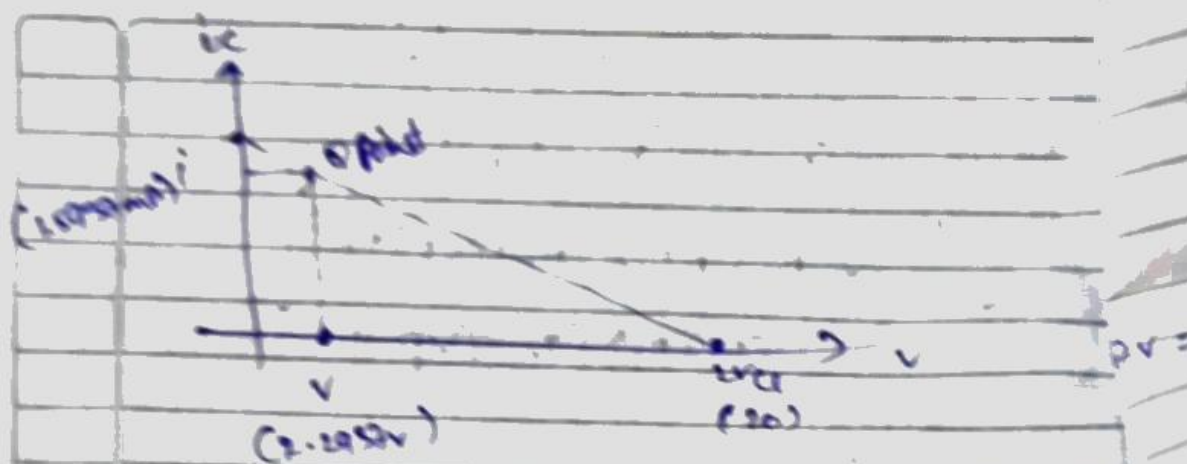

voltage gain ( $A_v$ )  $\rightarrow$  ( $\therefore$  from (B))

$$A_v = \frac{-R_c [ \beta R_1 - (r_{\pi} + (1+\beta) R_c) ]}{(R_c + R_1) [ r_{\pi} + (1+\beta) R_c ]}$$

$$i_B = \frac{2V_{cc} - V_{BE}}{(1+\beta)(R_c + R_E) + R_1} \quad (\therefore \text{from DC analysis})$$

$$= \frac{20 - 0.7}{(101)(11) + 100} \text{ mA}$$

$$= \frac{19.3}{1211}$$

$$i_B = 0.0159372419 \text{ mA}$$

$$r_{\pi} = \frac{V_T}{i_B} = \frac{0.026}{0.0159372419} \text{ k}\Omega$$

$$r_{\pi} = 1.63139892 \text{ k}\Omega$$

Substitute in  $A_v$

$$A_v = \frac{-R_c [ \beta R_1 - (r_{\pi} + (1+\beta)R_c) ]}{(R_c + R_1) [ r_{\pi} + (1+\beta)R_c ]}$$

$$\Rightarrow \frac{-10 [ 100(100) - (1.63139892 + (101)10) ]}{(110) [ 1.63139892 + 1010 ]}$$

$$= \frac{-8988.3686}{11127.9454}$$

$$A_v = -0.807729395$$

(d) Q-point ( $V, i$ )

$$V = V_{cc} - \left( \frac{1+\beta}{\beta} \right) (R_c + R_e) \left[ \frac{\beta (V_{cc} - V_{BE})}{(1+\beta)(R_c + R_e) + R_1} \right]$$

$\therefore$  as  $-V_{cc} = 0$ ,  $(2V_{cc})$  in 1(c) becomes  $(V_{cc})$

$$= 10 - \left( \frac{101}{100} \right) (11) \left[ \frac{100(10 - 0.7)}{(101)(11) + 100} \right]$$

$$= 10 - 11.1 \left[ \frac{930}{1211} \right] \Rightarrow 10 - 8.53203963$$

Sagar




$$V = 1.46796037 \text{ V}$$

$$i = \frac{\beta(V_{CC} - V_{BE})}{(1+\beta)(R_E + R_C) + R_1}$$

$$\Rightarrow \frac{100(10 - 0.7)}{(101)(11) + 100} = \frac{930}{121}$$

$$i = 0.00767960363 \text{ mA}$$

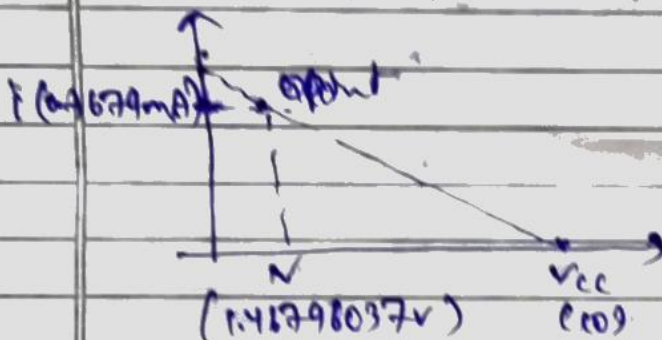

$$i_B = \frac{i_C}{\beta} \Rightarrow \frac{i_C}{\beta} = 0.0000767960363 \text{ mA}$$

$$r_{\pi} = \frac{V_T}{i_B} \Rightarrow \frac{0.021}{0.0000767960363}$$


$$r_{\pi} = 3.3855914 \text{ k}\Omega$$

$$A_V = \frac{-R_C[\beta R_1 - (r_{\pi} + (1+\beta)R_E)]}{(R_C + R_E)[r_{\pi} + (1+\beta)R_E]}$$


$$\Rightarrow \frac{-10[100(100) - (3.3855914 + (101)10)]}{(110)[3.3855914 + 1010]} = \frac{-8986.6144}{11147.2415}$$

$$A_V = -0.806173833$$

8

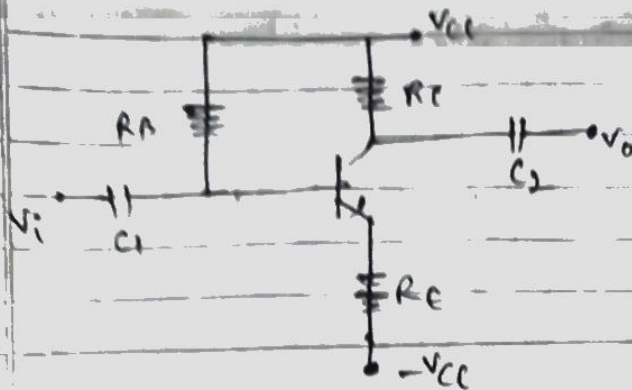

(a) DC analysis

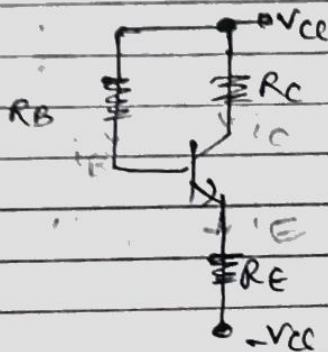

input loop equation,

$$V_{CC} - R_B i_B - V_{BE} - i_E R_E = -V_{CC}$$

$$2V_{CC} - R_B i_B - V_{BE} - (1+\beta) i_B R_E = 0$$

$$i_B = \frac{2V_{CC} - V_{BE}}{R_B + (1+\beta) R_E}$$

Output loop equation,


$$V_{CC} - i_C R_C - V_{CE} - \frac{(1+\beta) i_C}{\beta} R_E = -V_{CC}$$

$$2V_{CC} - V_{CE} = i_C \left[ R_C + \left( \frac{1+\beta}{\beta} \right) R_E \right] \quad \text{--- (1)}$$

Sagar

$$i_c = 0 \Rightarrow V_{CE} = 2V_{CC}$$
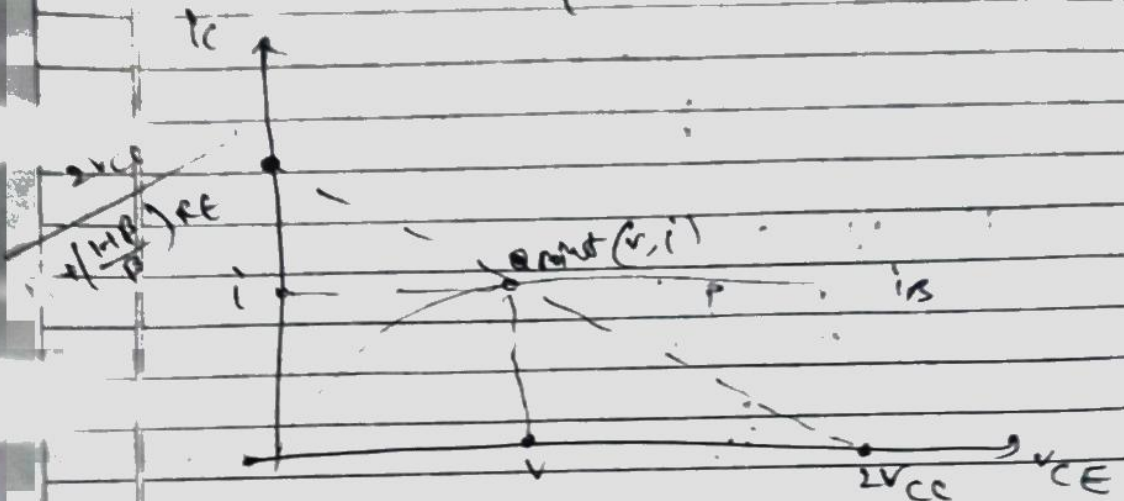
$$V_{CE} = 0 \Rightarrow i_c = \frac{2V_{CC}}{\left[R_C + \left(\frac{1+\beta}{\beta}\right)R_E\right]}$$



$$i_B = \frac{2V_{CC} - V_{BE}}{R_B + (1+\beta)R_E}$$

$$i = \beta i_B \Rightarrow i = \frac{\beta(2V_{CC} - V_{BE})}{(R_B + (1+\beta)R_E)}$$

Substitute  $i$  in eq (1),

$$V = 2V_{CC} - \frac{\beta(2V_{CC} - V_{BE})}{(R_B + (1+\beta)R_E)} \left( R_C + \left( \frac{1+\beta}{\beta} \right) R_E \right)$$

- (b)  $\left\{ \begin{array}{l} \text{short circuit} - \text{DC voltages, } C_1 \\ \text{open circuit} - C_2 \end{array} \right.$

DC analysis




STUDENT'S NAME

CLASS

SUBJECT

ROLL NO

DATE

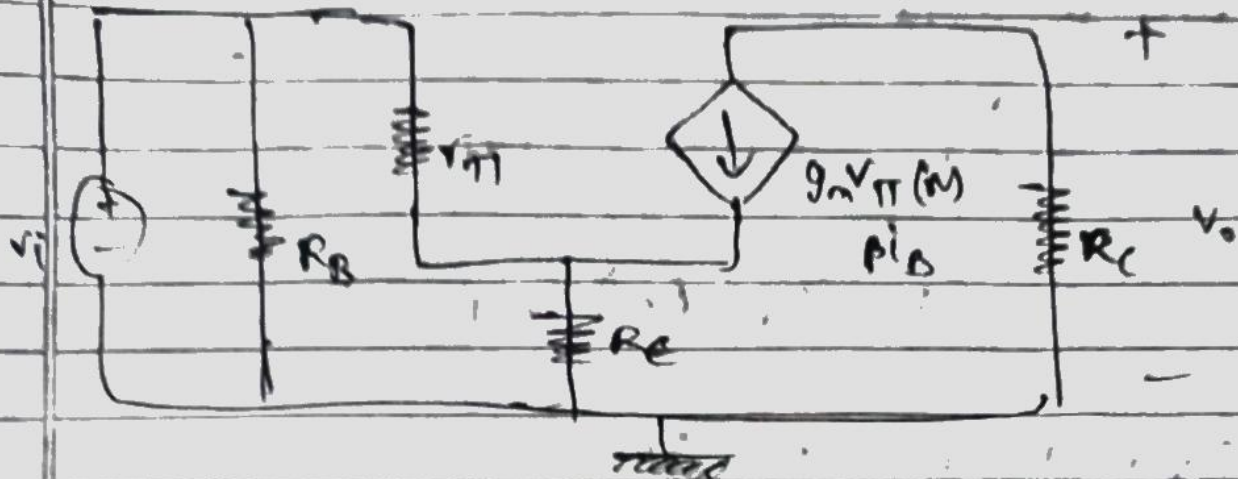

$$i_B = \frac{V_i}{R_{ib}} \quad \Rightarrow \quad i_B = \frac{V_i}{r_{\pi} + (1+\beta)R_E}$$


Case 1:  $v_o = -\beta i_B R_C$  (for  $V_A = \infty$ )

$$= -\beta \left[ \frac{V_i}{r_{\pi} + (1+\beta)R_E} \right] R_C$$

$$A_V = \frac{v_o}{v_i} = \frac{-\beta R_C}{r_{\pi} + (1+\beta)R_E} \quad \text{✓ 2M}$$

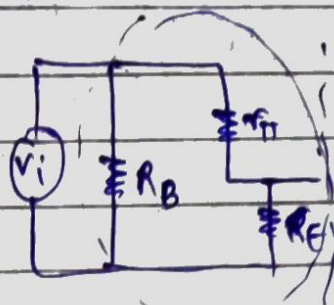(c) input resistance  $\left( \frac{V_i}{I_{in}} \right)$

$$\Rightarrow \frac{V_i}{I_{in}} = R_{ib} \parallel R_B$$



$$(i/p)_{resist} = (r_{\pi} + (1+\beta)R_E) \parallel R_B$$

Output resistance  $\left( \frac{V_o}{I_c} \right) \Rightarrow$

$$\frac{V_o}{I_c} = \frac{-\beta r_{\pi} R_E}{-\beta r_{\pi}}$$

$$o/p \text{ resistance} = R_E$$

(d)  $A_v = \frac{-\beta R_E}{r_{\pi} + (1+\beta)R_E}$  ( $\because$  from (b))

$$I_B = \frac{2V_{CC} - V_{BE}}{R_B + (1+\beta)R_E} = \frac{40 - 0.7}{300 + (101)} \text{ mA}$$

$$I_B = \frac{39.3}{601} \text{ mA} \Rightarrow I_B = 0.065391015 \text{ mA}$$

$$r_{\pi} = \frac{V_T}{I_B} \Rightarrow \frac{0.026}{0.065391015} \text{ k}\Omega$$

$$r_{\pi} = 0.399608142 \text{ k}\Omega$$

$$A_v = \frac{-\beta R_c}{r_{\pi} + (1+\beta) R_e}$$

$$= \frac{-100 (5)}{0.39700814 + (101)1}$$

$$= \frac{-500}{101.397608}$$

$$A_v = -4.93108299$$

(e)

$$I_B = 0.065391015 \text{ mA} \quad (\because \text{from (d)})$$


$$I_C = \beta I_B \Rightarrow I_C = 6.5391015 \text{ mA}$$

$$V_A = 100 \text{ V}$$

$$r_o = \frac{V_A}{I_C} = \frac{100}{6.5391015} \text{ k}\Omega$$

$$r_o = 15.2926209 \text{ k}\Omega$$

Small signal eq. model  $\Rightarrow$

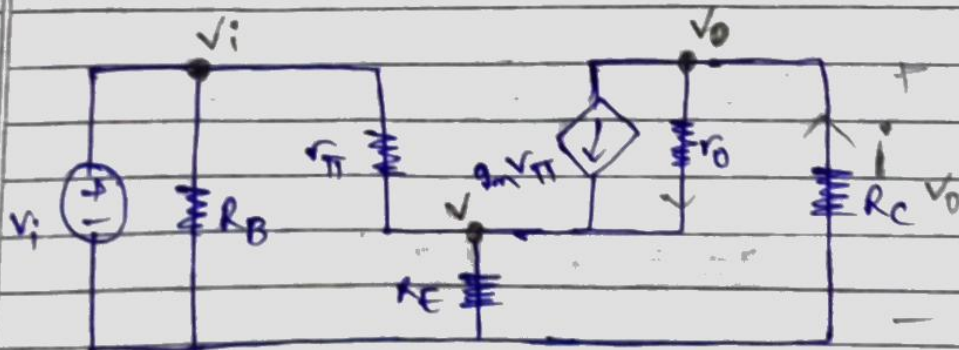



$$V_{\pi} = V_i - V$$

$$\rightarrow \frac{V_i - V}{r_{\pi}} + g_m V_{\pi} + \frac{V_o - V}{r_o} = \frac{V}{R_E}$$

$$\frac{V_i - V}{r_{\pi}} + g_m (V_i - V) + \frac{V_o - V}{r_o} = \frac{V}{R_E}$$

$$V_i \left[ g_m + \frac{1}{r_{\pi}} \right] + V_o \left[ \frac{1}{r_o} \right] = V \left[ \frac{1}{R_E} + \frac{1}{r_{\pi}} + \frac{1}{r_o} + g_m \right]$$

$$V = \frac{V_i \left[ g_m + \frac{1}{r_{\pi}} \right] + V_o \left[ \frac{1}{r_o} \right]}{\left( \frac{1}{R_E} + \frac{1}{r_{\pi}} + \frac{1}{r_o} + g_m \right)}$$

at output  $\rightarrow$

$$V_o = -i R_E$$

$$= - \left[ \frac{V_o - V}{r_o} + g_m V_{\pi} \right] R_E$$

$$= - \left[ \frac{V_o - V}{r_o} + g_m (V_i - V) \right] R_E$$

$$\rightarrow - \left[ V_o - V + g_m r_o (V_i - V) \right] \left( \frac{R_E}{r_o} \right)$$

$$\rightarrow - (V_o - V) \left( \frac{R_E}{r_o} \right) = g_m r_o (V_i - V) \left( \frac{R_E}{r_o} \right)$$

$$\Rightarrow - (v_o - v) \frac{R_E}{r_o}$$

$$\Rightarrow - \left( v_o - \frac{v_i (g_m + \frac{1}{r_{\pi}}) + v_o (\frac{1}{r_o})}{\frac{1}{R_E} + \frac{1}{r_{\pi}} + \frac{1}{r_o} + g_m} \right) \frac{R_E}{r_o}$$

$$\Rightarrow - \left[ \frac{\frac{v_o}{R_E} + \frac{v_o}{r_{\pi}} + \frac{v_o}{r_o} + g_m v_o - v_i g_m - \frac{v_i}{r_{\pi}} - \frac{v_o}{r_o}}{\frac{1}{R_E} + \frac{1}{r_{\pi}} + \frac{1}{r_o} + g_m} \right] \frac{R_E}{r_o}$$

$$\Rightarrow \frac{-v_o \left[ \frac{1}{R_E} + \frac{1}{r_{\pi}} + g_m \right] + v_i \left[ g_m + \frac{1}{r_{\pi}} \right]}{\frac{1}{R_E} + \frac{1}{r_{\pi}} + \frac{1}{r_o} + g_m} \left[ \frac{R_E}{r_o} \right]$$

$$\Rightarrow -g_m r_o (v_i - v) \frac{R_E}{r_o}$$

$$\Rightarrow -g_m R_E \left[ v_i - \frac{v_i (g_m + \frac{1}{r_{\pi}}) + v_o (\frac{1}{r_o})}{\frac{1}{R_E} + \frac{1}{r_{\pi}} + \frac{1}{r_o} + g_m} \right]$$

$$\Rightarrow -g_m R_E \left[ \frac{\frac{v_i}{R_E} + \frac{v_i}{r_{\pi}} + \frac{v_i}{r_o} + g_m v_i - v_i g_m - \frac{v_i}{r_{\pi}} - \frac{v_o}{r_o}}{\frac{1}{R_E} + \frac{1}{r_{\pi}} + \frac{1}{r_o} + g_m} \right]$$

$$\Rightarrow \frac{-g_m R_E \left[ \frac{1}{R_E} + \frac{1}{r_o} \right] v_i}{\frac{1}{R_E} + \frac{1}{r_{\pi}} + \frac{1}{r_o} + g_m} + \frac{g_m R_E v_o}{r_o \left( \frac{1}{R_E} + \frac{1}{r_{\pi}} + \frac{1}{r_o} + g_m \right)}$$



$$v_o = -(v_o - v_i) \frac{R_E}{r_o} - g_m r_o (v_i - v_o) \frac{R_E}{r_o}$$

$$v_o = \frac{-v_o \left[ \frac{1}{R_E} + \frac{1}{r_{\pi}} + g_m \right] \left( \frac{R_E}{r_o} \right)}{\frac{1}{R_E} + \frac{1}{r_{\pi}} + \frac{1}{r_o} + g_m} + \frac{v_i \left[ g_m + \frac{1}{r_{\pi}} \right] \left( \frac{R_E}{r_o} \right)}{\frac{1}{R_E} + \frac{1}{r_{\pi}} + \frac{1}{r_o} + g_m}$$

$$- \frac{g_m R_E \left[ \frac{1}{R_E} + \frac{1}{r_o} \right] v_i}{\frac{1}{R_E} + \frac{1}{r_{\pi}} + \frac{1}{r_o} + g_m} + \frac{g_m R_E v_o}{r_o \left[ \frac{1}{R_E} + \frac{1}{r_{\pi}} + \frac{1}{r_o} + g_m \right]}$$

$$v_o + \frac{v_o \left[ g_m + \frac{1}{r_{\pi}} + \frac{1}{R_E} \right] \left( \frac{R_E}{r_o} \right)}{\frac{1}{R_E} + \frac{1}{r_{\pi}} + \frac{1}{r_o} + g_m} - \frac{v_o \left[ g_m R_E \right]}{r_o \left( \frac{1}{R_E} + \frac{1}{r_{\pi}} + \frac{1}{r_o} + g_m \right)}$$

$$= \frac{v_i \left[ g_m + \frac{1}{r_{\pi}} \right] \left( \frac{R_E}{r_o} \right)}{\left( \frac{1}{R_E} + \frac{1}{r_{\pi}} + \frac{1}{r_o} + g_m \right)} - \frac{v_i g_m R_E \left[ \frac{1}{R_E} + \frac{1}{r_o} \right]}{\left( \frac{1}{R_E} + \frac{1}{r_{\pi}} + \frac{1}{r_o} + g_m \right)}$$

$$v_o \left[ \frac{r_o}{R_E} + \frac{r_o}{r_{\pi}} + 1 + g_m r_o + g_m R_E + \frac{R_E}{r_{\pi}} + \frac{R_E}{R_E} - g_m R_E \right]$$

$$r_o \left[ \frac{1}{R_E} + \frac{1}{r_{\pi}} + \frac{1}{r_o} + g_m \right]$$

$$= \frac{v_i \left[ \frac{g_m R_E}{r_o} + \frac{R_E}{r_{\pi} r_o} - \frac{g_m R_E}{r_o} - \frac{g_m R_E}{R_E} \right]}{\left[ \frac{1}{R_E} + \frac{1}{r_{\pi}} + \frac{1}{r_o} + g_m \right]}$$



$$P_v = \frac{V_o}{V_i}$$

$$\Rightarrow r_o \left[ \frac{R_c}{r_{\pi} r_o} - \frac{g_m R_c}{R_c} \right]$$

$$\left( \frac{r_o}{R_c} + \frac{r_o}{r_{\pi}} + 1 + g_m r_o + \frac{R_c}{r_{\pi}} + \frac{R_c}{R_c} \right)$$

$$r_o = 15.2926209 \text{ k}\Omega$$

$$r_{\pi} = 0.399608142 \text{ k}\Omega$$

$$g_m = \frac{i_c}{V_T} = \frac{6.5391015}{0.026} \text{ mA/V}$$


$$g_m = 251.503904 \text{ mA/V}$$

$$12.5751952 - 19230.7693$$

$$P_v = \frac{12.5751952 - 19230.7693}{(15.2926209 + 38.4615386 + 1 + 3846.15386 + 12.5751952 + 5)}$$

$$= \frac{-19218.1941}{3918.48321}$$

$$A_v = -4.90449826$$

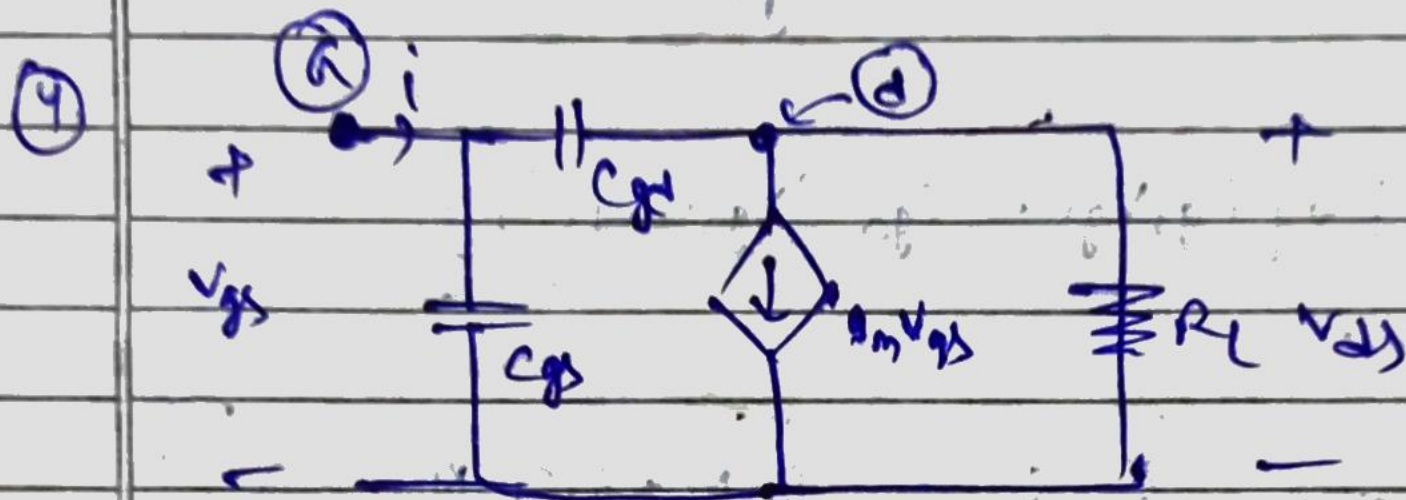

KCL at node 'd',

$$\frac{V_{gs} - V_{ds}}{(1/j\omega C_{gd})} = g_m V_{gs} + \frac{V_{ds}}{R_L}$$

$$j\omega C_{gd} (V_{gs} - V_{ds}) = g_m V_{gs} + \frac{V_{ds}}{R_L}$$

$$(g_m - j\omega C_{gd}) V_{gs} = - \left( \frac{1}{R_L} + j\omega C_{gd} \right) V_{ds}$$

$$V_{ds} = \frac{-(g_m - j\omega C_{gd})}{\left( \frac{1}{R_L} + j\omega C_{gd} \right)} V_{gs}$$

$$V_{ds} = \frac{-(g_m R_L - j\omega C_{gd} R_L)}{(1 + j\omega R_L C_{gd})} V_{gs}$$

KCL at node 'x',

$$i = \frac{V_{gs}}{\left( \frac{1}{j\omega C_{gs}} \right)} + \frac{V_{gs} - V_{ds}}{\left( \frac{1}{j\omega C_{gd}} \right)}$$

$$= j\omega [C_{gs} V_{gs} + C_{gd} (V_{gs} - V_{ds})]$$

$$= j\omega \left[ C_{gs} V_{gs} + C_{gd} \left( V_{gs} + \frac{g_m R_L - j\omega C_{gd} R_L}{1 + j\omega R_L C_{gd}} V_{gs} \right) \right]$$

$$= j\omega \left[ C_{gs} + C_{gd} \left( 1 + \frac{g_m R_L - j\omega C_{gd} R_L}{1 + j\omega R_L C_{gd}} \right) \right] V_{gs}$$

Miller Capacitance ( $C_M$ ) =

$$C_M = C_{gd} \left[ 1 + \frac{g_m R_L}{1 + j\omega R_L C_{gd}} \right]$$



$$g_m R_L, 1 \gg j\omega C_{gd} R_L$$

$$i = j\omega \left[ C_{gs} + \underbrace{C_{gd} \left( 1 + \frac{g_m R_L}{1} \right)}_{C_M} \right] V_{gs}$$

Miller Capacitance ( $C_M$ )  $\Rightarrow$

$$C_M = C_{gd} (1 + g_m R_L)$$

$$\rightarrow i = j\omega (C_{gs} + C_M) V_{gs}$$

output current, ( $i_d$ )  $\Rightarrow$

$$i_d = -g_m V_{gs}$$

$$A_i = \frac{i_d}{i} = \frac{-g_m V_{gs}}{j\omega (C_{gs} + C_M) V_{gs}}$$

Cutoff frequency ( $f_c$ )  $\Rightarrow$

$$|A_i| = 1 \Rightarrow$$

$$\frac{g_m}{\omega (C_{gs} + C_M)} = 1$$

$$f_c = \frac{g_m}{2\pi (C_{gs} + C_M)}$$

Cut off frequency ( $f_T$ )  $\rightarrow$

$$|A| = 1 \rightarrow$$

$$\frac{g_m}{\omega_f (C_{gs} + C_m)} = 1$$

$$f_T = \frac{g_m}{2\pi (C_{gs} + C_m)}$$