
 


 35. a) Derive the transfer function of low pass filter and plot its frequency response.



NOTE:- fig. 2 is the same as fig. 1.

$$\therefore V_a = V_2$$

Overall ~~gain~~ gain  $\frac{V_o}{V_1}$

$$\frac{V_o}{V_1} = \frac{V_o}{V_i} \times \frac{V_2}{V_2} \quad (\text{multiplying \& dividing by } V_2)$$

$$= \frac{V_o}{V_2} \times \frac{V_2}{V_1} = \left(1 + \frac{R_F}{R_1}\right) \times \left(\frac{1}{1 + sRC}\right)$$

$$\Rightarrow \frac{V_o(s)}{V_1(s)} = A_o \times \frac{1}{1 + sRC} = H(s) \quad (\text{from (1) \& (2)})$$

$$\Rightarrow h\left(\frac{\omega}{f}\right) = \frac{A_o}{1 + j\omega RC}$$

(converting to time domain)

$$\Rightarrow h\left(\frac{\omega}{f}\right) = \frac{A_o}{1 + j2\pi f RC} \quad (\omega = 2\pi f)$$

$$\Rightarrow H(j\omega) = \frac{A_o}{1 + j\frac{f}{f_c}} \quad (f_c = \frac{1}{2\pi RC})$$

Let the gain be  $A_o$

$$\text{from fig. 2, } A_o = \frac{V_o}{V_2} = 1 + \frac{R_F}{R_1} \quad \text{①}$$

[non-inverting op. amp.]

In fig. 1, applying KCL @ node a  $\rightarrow$

$$\frac{V_1 - V_2}{R} = \frac{V_2}{\frac{1}{sC}} \quad (\text{current through a capacitor is } \frac{V}{1/sC})$$

$$\Rightarrow \frac{V_1 - V_2}{R} = V_2 sC$$

$$\Rightarrow \frac{V_1}{R} = V_2 \left(sC + \frac{1}{R}\right)$$

$$\Rightarrow \frac{V_2}{V_1} = \frac{1}{1 + sRC} \quad \text{②}$$

$$1 + \frac{R_F}{R_1} = A_o$$

$$2) \quad |H(j\omega)| = \frac{A_0}{\sqrt{1 + \left(\frac{f}{f_c}\right)^2}}$$

①  $f=0, |H(j\omega)| = A_0$

②  $f=f_c, |H(j\omega)| = 0.707 A_0$

\*  $f_c \rightarrow$  cut off frequency


 


fig-3  $\rightarrow$  FREQUENCY RESPONSE OF LOW PASS FILTER

36. a) Derive the transfer function of a high pass filter and plot its frequency response.

Ans:-

 

Let the pass band (or) closed loop gain be  $A_0$ .

By applying KCL @ node a, we get

$$\frac{V_1 - V_2}{1/sC} = \frac{V_2}{R}$$

$$\star \frac{V_0}{V_2} = A_0$$

$$\Rightarrow RSC(V_1 - V_2) = V_2$$

$$\star H(s) = \frac{V_0(s)}{V_1(s)}$$

$$\Rightarrow RSC V_1 = V_2(1 + SRC)$$

$$\Rightarrow \frac{V_1}{V_2} = \frac{1 + SRC}{SRC}$$

$$\frac{V_0}{V_1} = \frac{V_0}{V_2} \times \frac{V_2}{V_1} \Rightarrow H(s) = A_0 \times \frac{SRC}{1 + SRC}$$

$$= A_0 \times \frac{j\omega RC}{1 + j\omega RC} = A_0 \frac{j2\pi RC f}{1 + j2\pi RC f}$$

$$\therefore H(j\omega) = A_0 \frac{j f}{f_c} \frac{1}{1 + j \frac{f}{f_c}}$$

$$\left( \star f_c = \frac{1}{2\pi RC} \right)$$


$$|H(j\omega)| = \frac{A_0 f / f_c}{\sqrt{1 + (f/f_c)^2}}$$

as  $f \rightarrow \infty$ ,  $|H(j\omega)| = A_0$

(5)

when  $f = f_c$ ,  $|H(j\omega)| = \frac{A_0}{\sqrt{2}} = 0.707 A_0$

FREQUENCY RESPONSE :-

 

b) Design a high pass filter with a cutoff frequency of  $10\text{kHz}$  & a pass band gain of 10.

Ans :-  $A_0 = 10 = 1 + \frac{R_f}{R_i} \Rightarrow \underline{\underline{R_f = 9R_i}}$

$f_c = \frac{1}{2\pi RC}$

Let  $C = 0.1\text{ }\mu\text{F}$

$\Rightarrow 10 \times 10^3 \times 2\pi \times 0.1 \times 10^{-6} = \frac{1}{R}$


$\Rightarrow \underline{\underline{R = 159.15\text{ }\Omega}}$

Let  $R_i = 1\text{ k}\Omega \Rightarrow \underline{\underline{R_f = 9\text{ k}\Omega}}$

Ckt diagram:-




Ckt. diagram :-

 


37. Design a weighted resistor DAC for the i/p 11011. Find the O/P voltage,  $V_R = 20V$ ,  $R_f = R$ . *Assume  $R = 1k\Omega$ .*

Ans :-

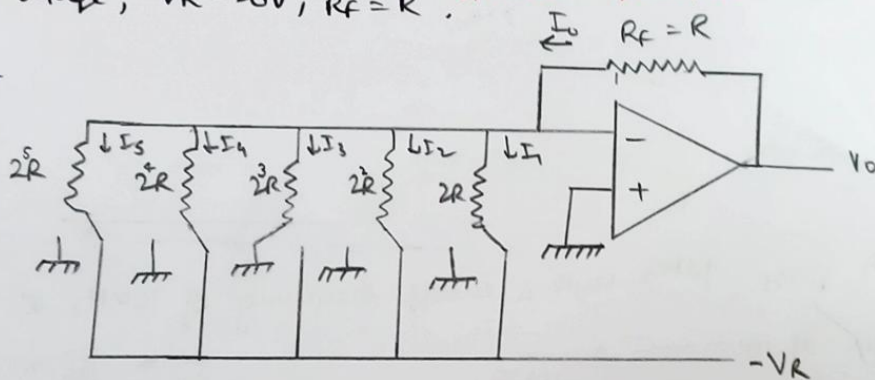

EQUIVALENT Ckt. :-

 

(Assume  $R_f = 1k\Omega$ )

$\therefore 2R = 2k\Omega$

$$V_0 = I_0 R_f$$

$$I_0 = \frac{V_R}{2R} d_1 + \frac{V_R}{2^2 R} d_2 + \dots + \frac{V_R}{2^n R} d_n$$

Here, 
$$I_0 = \frac{20}{2k} (1) + \frac{20}{2^2 k} (1) + \frac{20}{2^3 k} (0) + \frac{20}{2^4 k} (1) + \frac{20}{2^5 k} (1)$$

$$= \frac{1}{k} (16.875) = 16.875 \text{ mA}$$

$$\therefore V_0 = 16.875 \times 10^{-3} \times 10^3$$

$$= 16.875 \text{ V}$$

$d_1$	$d_2$	$d_3$	$d_4$	$d_5$
1	1	0	1	1

### 10.2.2 R-2R Ladder DAC


Wide range of resistors are required in binary weighted resistor type DAC. This can be avoided by using R-2R ladder type DAC where only two values of resistors are required. It is well suited for integrated circuit realization. The typical value of  $R$  ranges from 2.5 k $\Omega$  to 10 k $\Omega$ .

For simplicity, consider a 3-bit DAC as shown in Fig. 10.5 (a), where the switch position  $d_1 d_2 d_3$  corresponds to the binary word 100. The circuit can be simplified to the equivalent form of Fig. 10.5 (b) and finally to Fig. 10.5 (c). Then, voltage at node C can be easily calculated by the set procedure of network analysis as

$$\frac{-V_R \left( \frac{2}{3} R \right)}{2R + \frac{2}{3} R} = -\frac{V_R}{4}$$

The output voltage is


$$V_o = \frac{-2R}{R} \left( -\frac{V_R}{4} \right) = \frac{V_R}{2} = \frac{V_{FS}}{2}$$

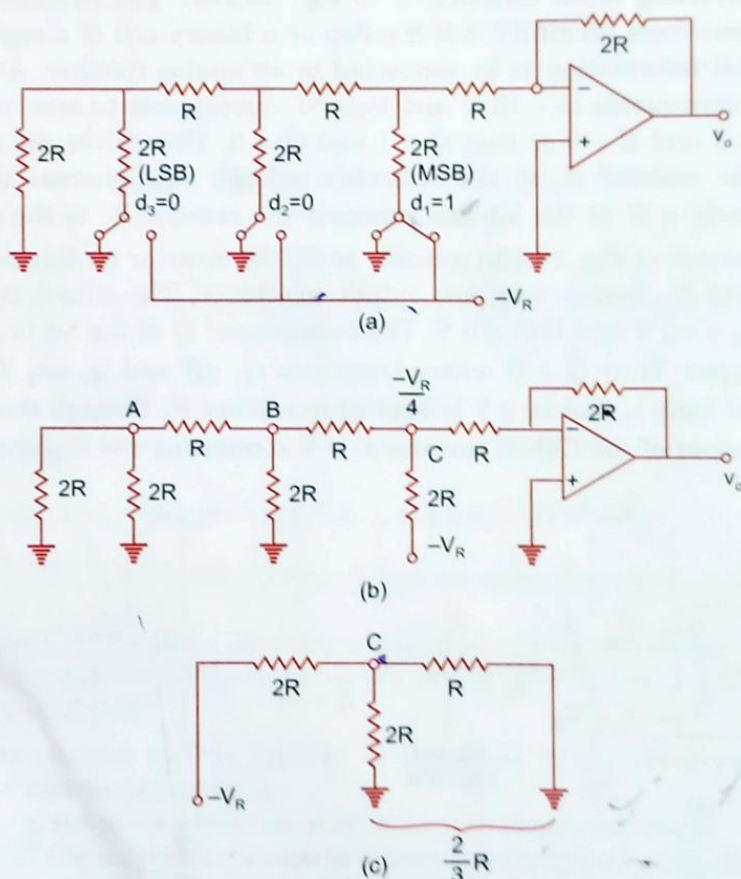

**Fig. 10.5** (a) R-2R ladder DAC (b) Equivalent circuit of (a), (c) Equivalent circuit of (b)

The switch position corresponding to the binary word 001 in 3 bit DAC is shown in Fig. 10.6 (a). The circuit can be simplified to the equivalent form of Fig. 10.6 (b). The voltages at the nodes (A, B, C) formed by resistor branches are easily calculated in a similar fashion and the output voltage becomes

$$V_o = \left(-\frac{2R}{R}\right)\left(-\frac{V_R}{16}\right) = \frac{V_R}{8} = \frac{V_{FS}}{8}$$

 

**Fig. 10.6** (a) R-2R ladder DAC for switch positions 001 (b) Equivalent circuit

In a similar fashion, the output voltage for R-2R ladder type DAC corresponding to other bit binary words can be calculated.




## DIRECT TYPE ADCs

### 10.3.1 The Parallel Comparator (Flash) A/D Converter

This is the simplest possible A/D converter. It is at the same time, the fastest and most expensive technique. Figure 10.10 (a) shows a 3-bit A/D converter. The circuit consists of a resistive divider network, 8 op-amp comparators and a 8-line to 3-line encoder (3-bit priority encoder). The comparator and its truth table is shown in Fig. 10.10 (b). A small amount of hysteresis is built into the comparator to resolve any problems that might occur if both inputs were of equal voltage as shown in the truth table. Coming back to Fig. 10.10 (a), at each node of the resistive divider, a comparison voltage is available. Since all the resistors are of equal value, the voltage levels available at the nodes are equally divided between the reference voltage  $V_R$  and the ground. The purpose of the circuit is to compare the analog input voltage  $V_a$  with each of the node voltages. The truth table for the flash type AD converter is shown in Fig. 10.10 (c). The circuit has the advantage of high speed as the



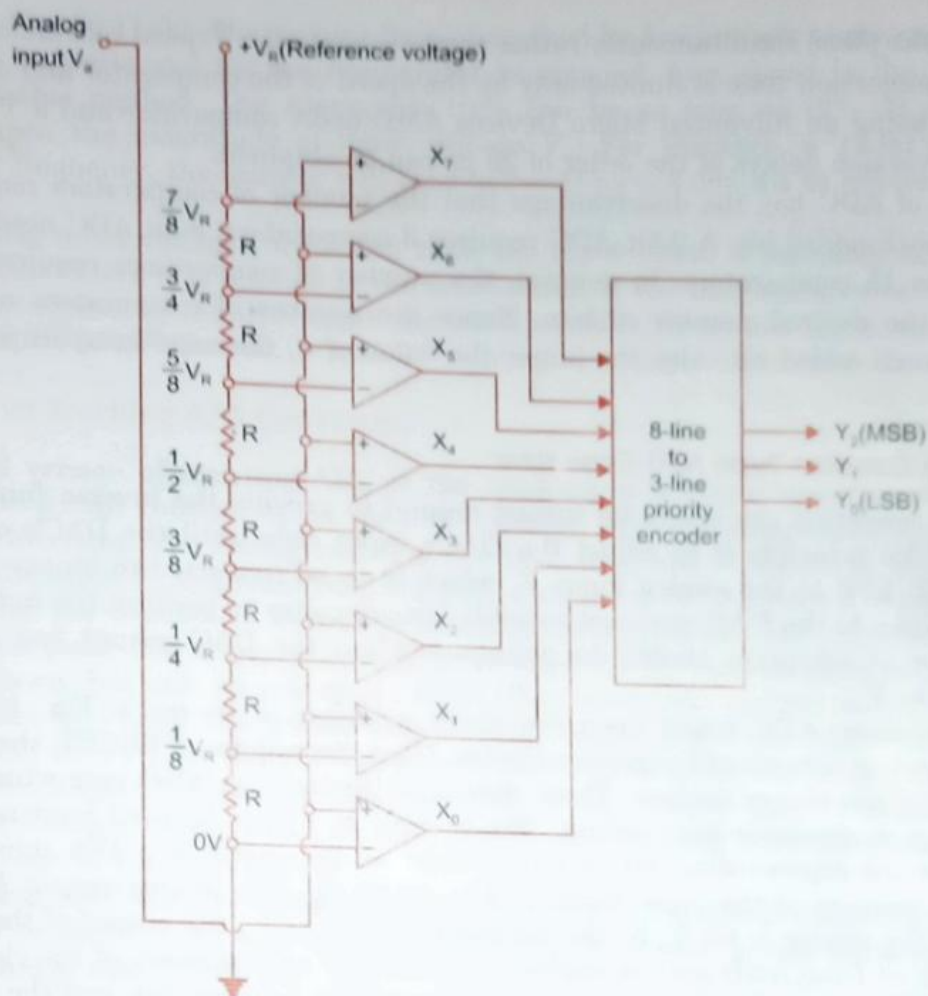

**Fig. 10.10** (a) Basic circuit of a flash type A/D converter

Voltage input	Logic output $X$
$V_a > V_d$	$X = 1$
$V_a < V_d$	$X = 0$
$V_a = V_d$	Previous value



**Fig. 10.10** (b) Comparator and its truth table

Input voltage $V_a$	$X_7$	$X_6$	$X_5$	$X_4$	$X_3$	$X_2$	$X_1$	$X_0$	$Y_2$	$Y_1$	$Y_0$
0 to $V_R/8$	0	0	0	0	0	0	0	1	0	0	0
$V_R/8$ to $V_R/4$	0	0	0	0	0	0	1	1	0	0	1
$V_R/4$ to $3 V_R/8$	0	0	0	0	0	1	1	1	0	1	0
$3 V_R/8$ to $V_R/2$	0	0	0	0	1	1	1	1	0	1	1
$V_R/2$ to $5 V_R/8$	0	0	0	1	1	1	1	1	1	0	0
$5 V_R/8$ to $3 V_R/4$	0	0	1	1	1	1	1	1	1	0	1
$3 V_R/4$ to $7 V_R/8$	0	1	1	1	1	1	1	1	1	1	0
$7 V_R/8$ to $V_R$	1	1	1	1	1	1	1	1	1	1	1

**Fig. 10.10** (c) Truth table for a flash type A/D converter

conversion take place simultaneously rather than sequentially. Typical conversion time is 100 ns or less. Conversion time is limited only by the speed of the comparator and of the priority encoder. By using an Advanced Micro Devices AMD 686A comparator and a T1147 priority encoder, conversion delays of the order of 20 ns can be obtained.

This type of ADC has the disadvantage that the number of comparators required almost doubles for each added bit. A 2-bit ADC requires 3 comparators, 3-bit ADC needs 7, whereas 4-bit requires 15 comparators. In general, the number of comparators required are  $2^n - 1$  where  $n$  is the desired number of bits. Hence the number of comparators approximately doubles for each added bit. Also the larger the value of  $n$ , the more complex is the priority encoder.