

to Explain the functional diagram of 555 timer.

41. Explain the operation of monostable multivibrator using 555 timer and derive the expression for pulse width.

42. Explain the operation of astable multivibrator using 555 timer and derive the expression for duty cycle.

