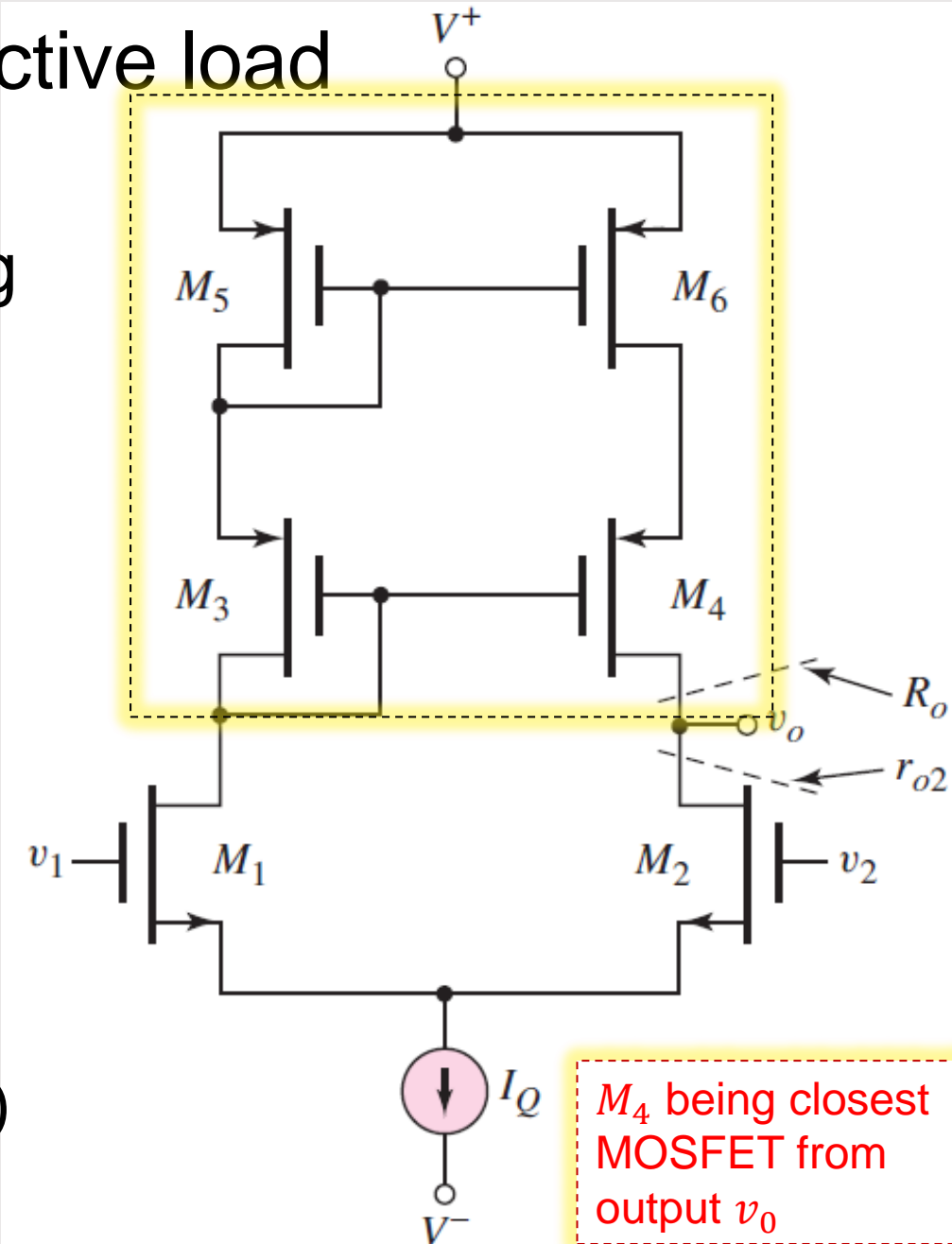


2. MOSFET Diff Amp with Cascode Active load

- The differential-mode voltage gain is proportional to the output resistance looking into the active load transistor. The voltage gain can be increased, therefore, if the output resistance can be increased.
- An increase in output resistance can be achieved by using, for example, a cascode active load.
- Cascode has M_4, M_6 as the MOSFETs in output end of the highlighted load circuit.
- Output resistance $R_0 = r_{o4} + r_{o6}(1 + g_m r_{o4})$




Remembering Cascode current mirror

Comparison of output resistance of Cascode MOSFET current source to that of two transistor current source:

- Two transistor current source:

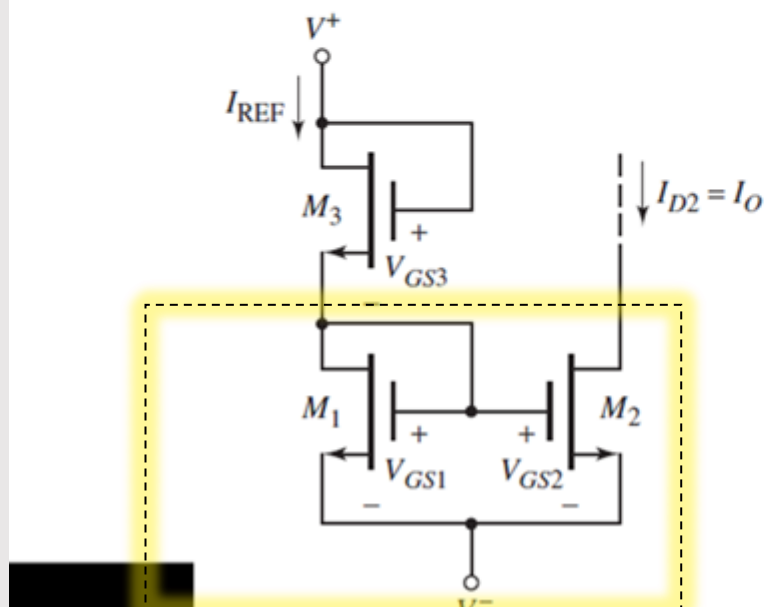
$$\text{Output Resistance } r_0 = \frac{1}{\lambda I_{REF}}$$



Cascode MOSFET Current source



$$R_0 = r_{04} + r_{02}(g_m r_{04} + 1)$$

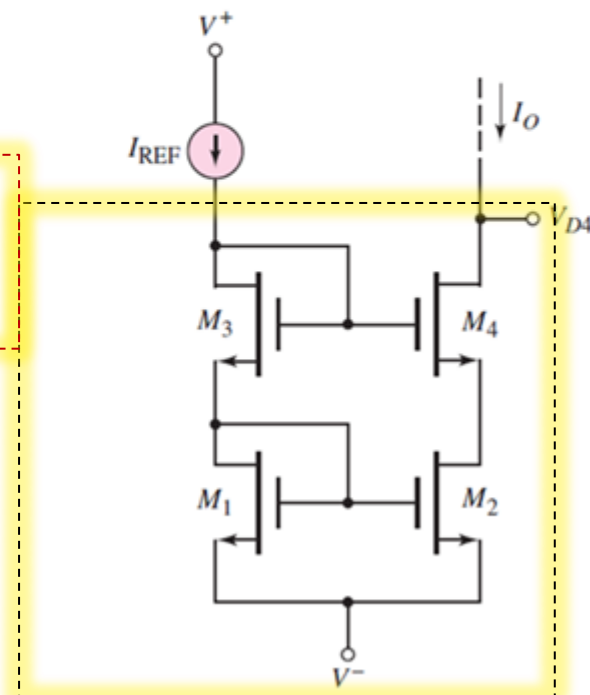M_4 being closest MOSFET from output V_{D4}



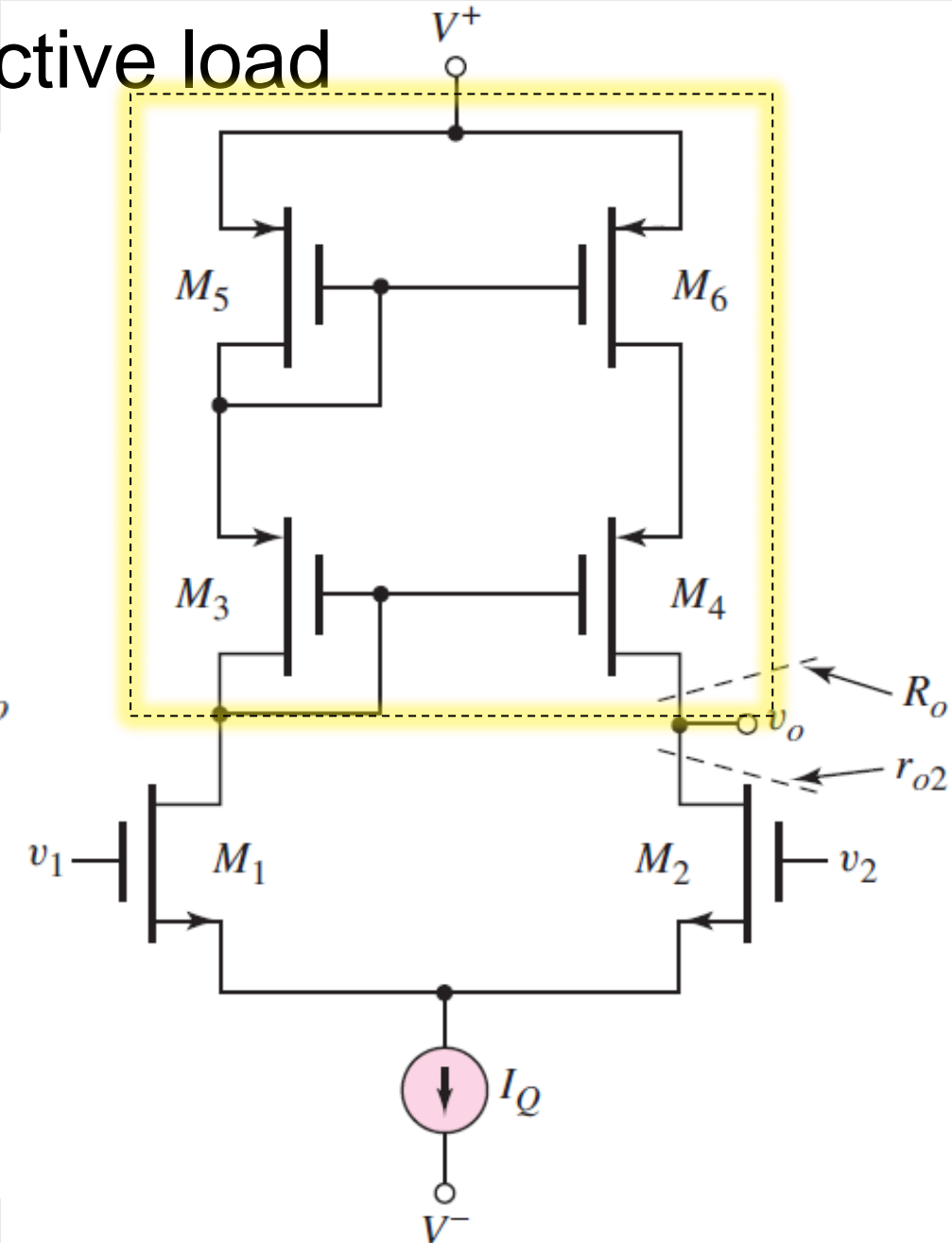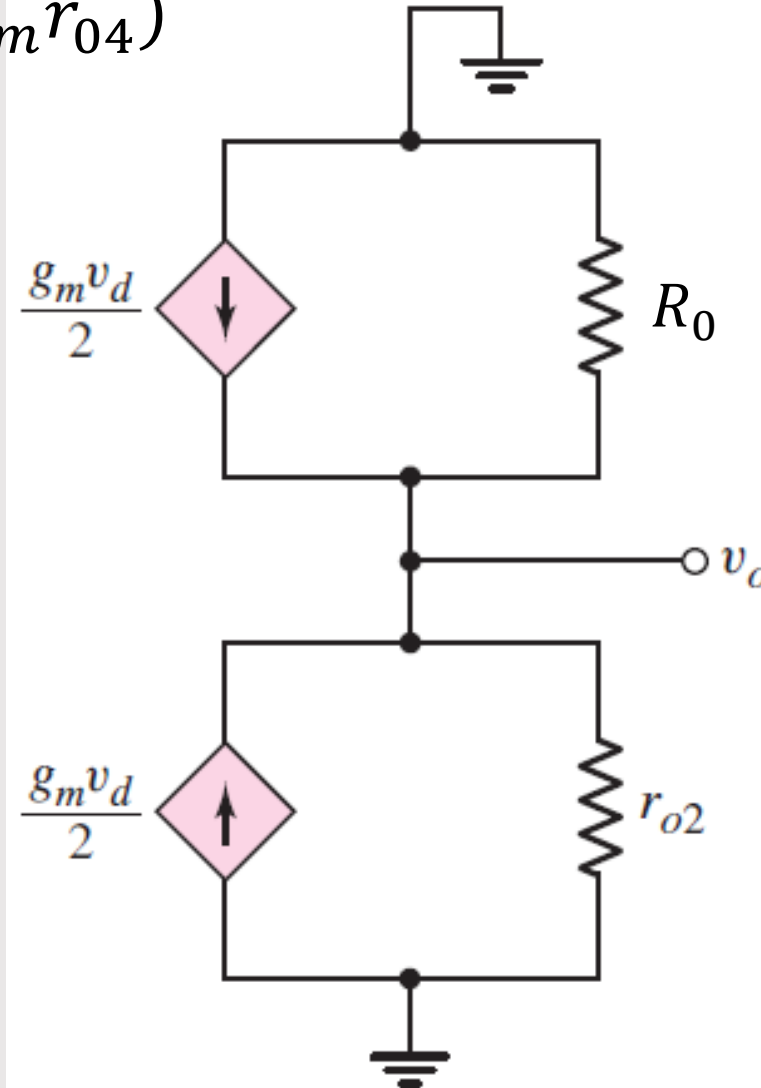2. MOSFET Diff Amp with Cascode Active load




- $R_0 = r_{o4} + r_{o6}(1 + g_m r_{o4})$



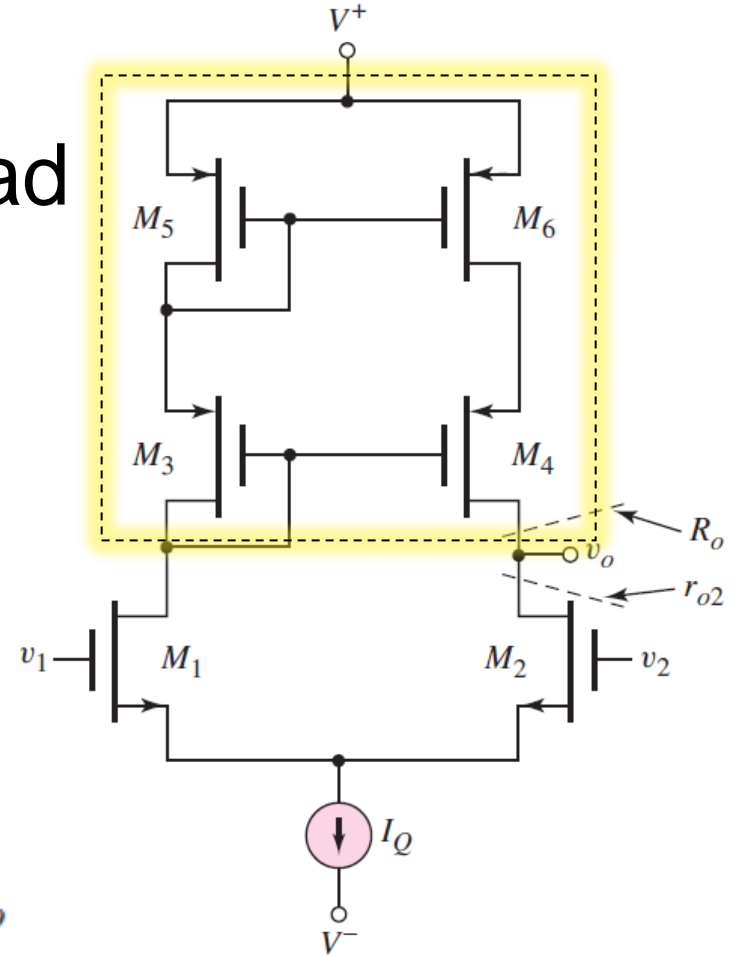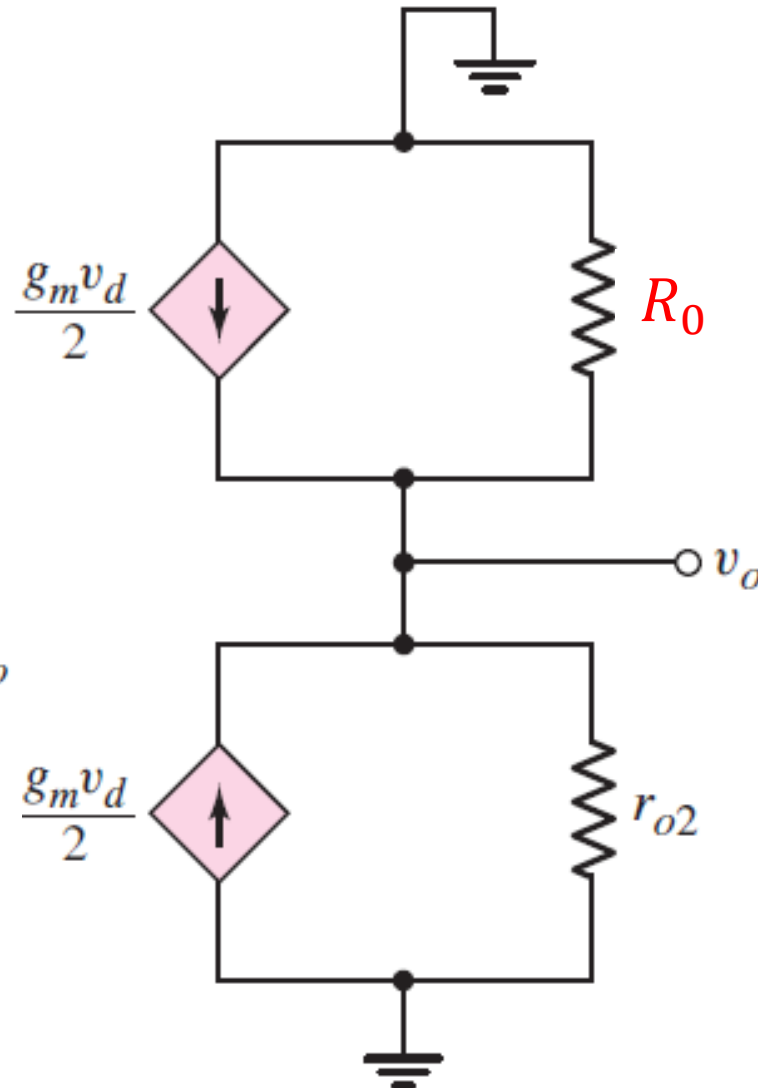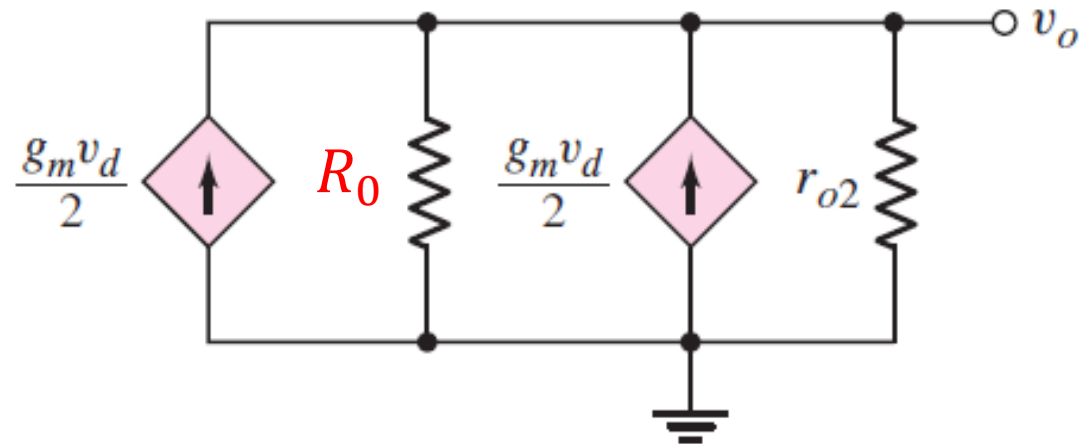2. MOSFET Diff Amp with Cascode Active load

- $R_o = r_{o4} + r_{o6}(1 + g_m r_{o4})$
- $v_o = i(r_{o2} \parallel R_o)$
- $v_o = 2 \left(\frac{g_m v_d}{2} \right) (r_{o2} \parallel R_o)$
- Small signal diff mode voltage gain:

$$A_d = \frac{v_o}{v_d} = g_m (r_{o2} \parallel R_o)$$




Problem: Calculate the differential-mode voltage gain of a MOSFET diff-amp with a cascode active load. Note: $(W/L)_n = 10$; $I_{DQ} = 0.1mA$; $k'_n = 80\mu A/V^2$; $V_{TN} = 0.5V$; $\lambda_n = 0.02V^{-1}$; $V_{TP} = -1V$; $k'_p = 40\mu A/V^2$; $\lambda_p = 0.02V^{-1}$;

- $K_n = \frac{k'_n}{2} \left(\frac{W}{L} \right) = \frac{80 \times 10^{-6}}{2} (10) = 0.4 \times 10^{-3} A/V^2$

- Transconductance: $g_m = 2\sqrt{K_n I_{DQ}}$
 $= 2\sqrt{(0.4 \times 10^{-3})(0.1 \times 10^{-3})}$
 $= 0.4mA/V$

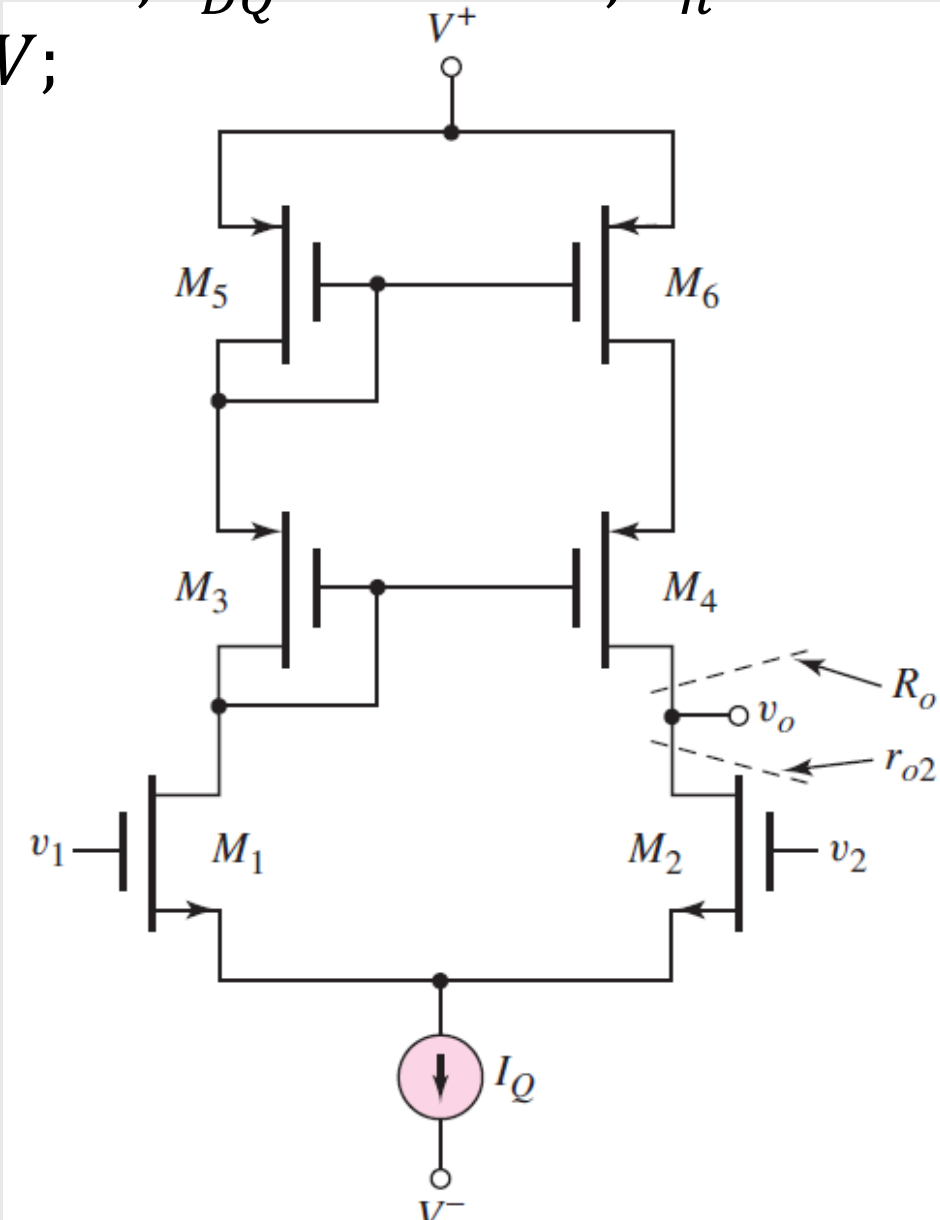- Output resistance of individual transistors:
 $r_o = \frac{1}{\lambda I_{DQ}} = \frac{1}{(0.02)(0.4m)} = 500k\Omega$



Problem: Calculate the differential-mode voltage gain of a MOSFET diff-amp with a cascode active load. Note: $(W/L)_n = 10$; $I_{DQ} = 0.1mA$; $k'_n = 80\mu A/V^2$; $V_{TN} = 0.5V$; $\lambda_n = 0.02V^{-1}$; $V_{TP} = -1V$; $k'_p = 40\mu A/V^2$; $\lambda_p = 0.02V^{-1}$;

- $g_m = 0.4mA/V$ $r_o = 500k\Omega$

- Cascode active load output resistance:

$$\begin{aligned} R_o &= r_{o4} + r_{o6}(1 + g_m r_{o4}) \\ &= 500k + 500k(1 + 0.4m(500k)) \\ &= 500k + 500k(201) \\ &= 101000k = 101M\Omega \end{aligned}$$

Diff mode voltage gain: $A_d = \frac{v_o}{v_d} = g_m(r_{o2} \parallel R_o)$

$$A_d = 0.4m(500k \parallel 101000k) = 200$$

