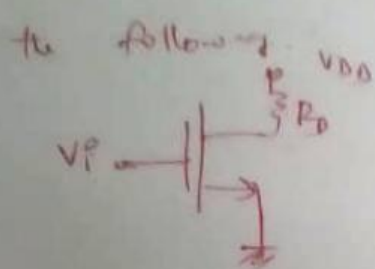


9. For the class A power amplifier shown below, do




$V_{DD} = 10V$, $R_D = 10k\Omega$, $K_n = 0.5 mA/V^2$,
 $V_T = 1V$, $\lambda = 0$. Assume the

Output voltage is limited to the range between the clamping point at $V_{DS} = 9V$ to minimize the non-linear distortion.

Calculate the power conversion efficiency.

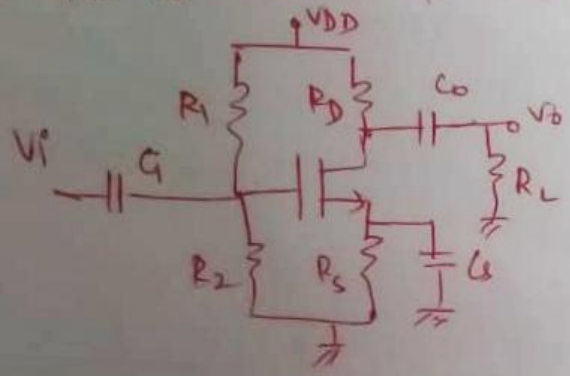10. For the class A power amplifier shown below,



a) Derive the power conversion efficiency.

b) $V_{DD} = 10V$, $R_1 = 100k\Omega$, $R_2 = 50k\Omega$,
 $R_D = 5k\Omega$, $R_S = 1k\Omega$, $V_T = 1V$,
 $K_n = 0.5 mA/V^2$, calculate I_{DQ} , V_{DSQ} .

c) Due to the input signal, the output drain current goes between $500mA$ and $50mA$. The V_{DS} swings between $10V$ and $1V$. Determine the conversion efficiency.

11. For class B power MOSFET amp, derive the power efficiency and max power efficiency.

12. Compare the characteristics of class A and class B power amplifier.

B. Consider the class AB power MOSFET, determine the required biasing if $V_{DD} = 20V$ and $R_L = 10\Omega$, the transistors are matched and the parameters are $k_n = 0.5 \text{ mA/V}^2$ and $V_T = 1V$, the quiescent drain current is 20% of the load current when $V_o = 8V$.

