
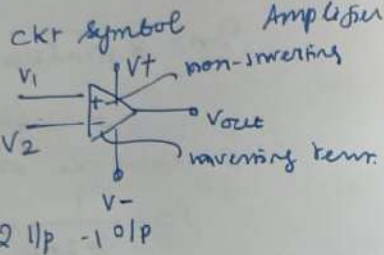


Module-4 Operational Amplifiers

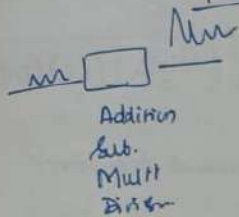


2 I/p - 1 O/p
2 power supply. Sometimes

Amplifiers -

1 Difference b/w the 2 I/p signals


Gain A

$$O/p = A(V_1 - V_2)$$

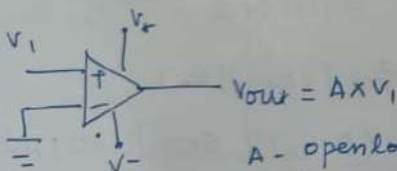

A - open loop gain
ie) no feedback

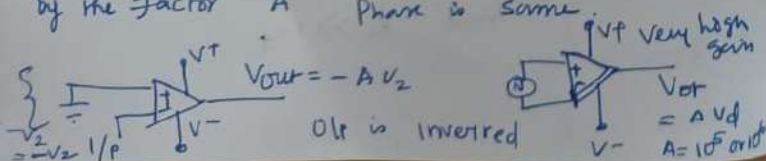If I/p is sin O/p sine wave must be multiplied by the factor A. Phase is same.




High gain differential Amplifier

$$1 \text{ mV} - \text{O/p} \quad A \text{ Vd} \\ 1 \text{ mV} \times 10^5 = 100 \text{ V} \\ 1 \times 10^5 = 10^5 \text{ V (not possible)}$$

O/p is limited by biasing voltages
Application
Comparator
Open loop gain
2) oscillator 3) Waveform converter 4) ADC & DAC

Equivalent ckt

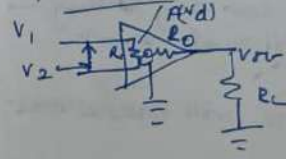

$$R_i = \infty \\ R_o = 0$$


BW = ∞
or Ideal. Supports all frequencies
Gain of the ideal A = ∞

Slew rate, CMRR

Virtual Ground

O/p should be linear, in open loop linear region is very small, Fb, will control the linear region

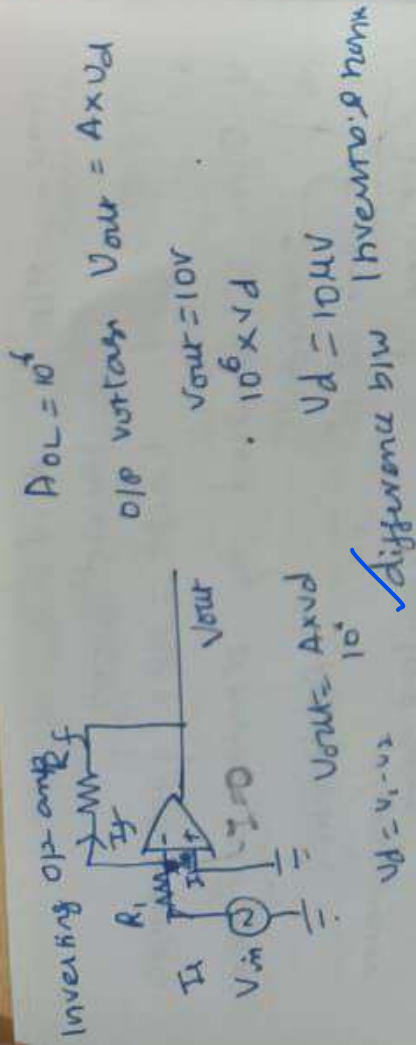Feedback
O/p - +ve - Non-Inverting amplifier
O/p - -ve - Inverting amplifier



$A_{OL} = 10^4$
 o/p voltage $V_{out} = A \times V_d$
 $V_{out} = 10V$
 $10^6 \times 10^{-4}$
 $V_d = 10\text{mV}$
 Difference b/w Inverting & non-inverting

$V^+ - V^- = 10\text{mV}$
 $V^+ - V^- \approx 0V$
 $V^+ = V^-$
 Inverting & non-inverting are at same potential
 or we can say they are virtual short
 V^+ is grounded
 $V^+ = 0$ then $V^- = 0$

Negative feedback resistor will ensure that $V_d = 0$ or negligible

I_1 is current flowing through R_i
 I_f is " " " " " " R_f
 Ideal op-amp $R_{in} = \infty$ at this point when no current is entering into op-amp
 $I_1 = I_f$
 $\frac{V_1 - V^-}{R_i} = \frac{V^- - V_{out}}{R_f}$
 so $I = 0$

Applying Virtual ground, $V_x = 0$


$\frac{V_{in}}{R_i} = -\frac{V_{out}}{R_f} \Rightarrow \frac{V_{out}}{V_{in}} = -\frac{R_f}{R_i}$

closed loop gain of inverting amplifier

— indicates 180° out of phase.

$R_1 = 1\text{K}\Omega$ $R_2 = 2\text{K}\Omega$

Non-Inverting amplifier

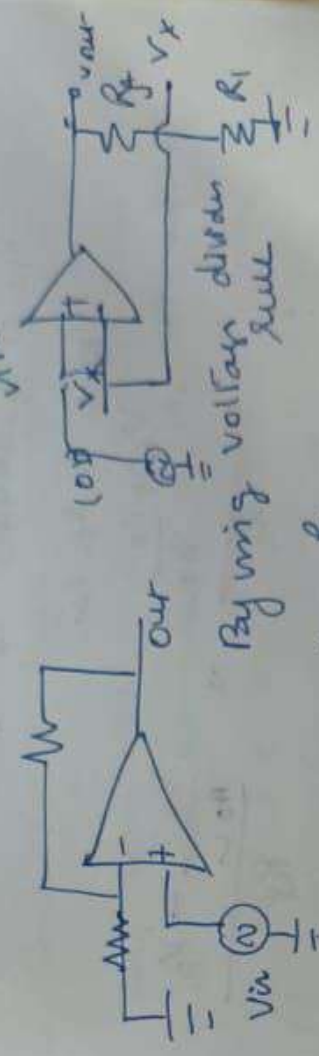


By using voltage divider rule
 $V_x = \frac{R_1}{R_1 + R_f} \times V_{out}$
 $V^+ = V^-$ (\because virtual short)

$V^+ = V_{in}$
 $V^- = V_{in} = V_x$

$V_{in} = \frac{R_1}{R_1 + R_f} \times V_{out}$

$\frac{V_{out}}{V_{in}} = \frac{R_1 + R_f}{R_1} = 1 + \frac{R_f}{R_1}$

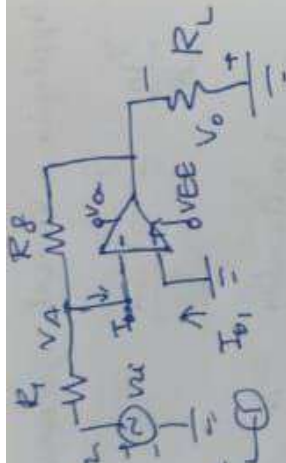Closed loop gain of non-inverting amplifier



Practical Inverting amplifier

$$R_i \neq \infty \quad I_{i1} = I_f + I_{b2} = I_f \quad I_{b1} = I_{b2}$$

$$\frac{V_i - V_A}{R_i} = \frac{V_o - V_o}{R_f} \quad (3)$$

$$V_o = A_{OL} V_A = A_{OL} (V_1 - V_2)$$

$$V_1 = 0 \text{ grounded} \quad V_2 = V_A$$

$$V_o = -A_{OL} V_A$$

$$\text{Sub. in} \quad \frac{V_i + \frac{V_o}{A_{OL}}}{R_i} = \frac{-\frac{V_o}{A_{OL}} - V_o}{R_f}$$

$$\therefore V_i R_f + V_o \frac{R_f}{A_{OL}} = -\frac{R_i}{A_{OL}} V_o - R_i V_o$$

$$V_i R_f = -V_o \left[\frac{R_i}{A_{OL}} + R_i + \frac{R_f}{A_{OL}} \right]$$

$$A_{CL} = V_o / V_i$$

$$\therefore A_{CL} = \frac{A_{OL} R_f}{R_i + R_f + R_i A_{OL}}$$

Now ideally A_{OL} is very large tending to ∞
 $A_{CL} R_i \gg R_i + R_f \quad A_{CL} = \frac{R_f}{R_i}$

DC Characteristics

An ideal op-amp draws no current from

source & its response is also independent of temp.

→ Real op-amp - Current taken from source to Op-amp I_{PS}

→ 2 I_{PS} respond differently to current & voltage

due to mismatch in transistors.

→ Real op-amp shifts temperature

These non-ideal dc characteristics that add error components to dc output voltage

- (i) I_{PS} bias current
- (ii) I_{PS} offset current
- (iii) I_{PS} offset voltage
- (iv) Thermal drift

I_{PS} Bias current

I_{PS} to op-amp → Differential amplification

FET (or) BJT

Both must be biased in linear region by supplying current into bases or by the external circuit


Ideal op-amp - no current drawn to I/P
 Practical I/P terminals conduct small value
 of dc current to bias the I/P transistors

→ Bias currents entering +, - terminals are

$$I_B^+ \times I_B^-$$

They are not exactly equal
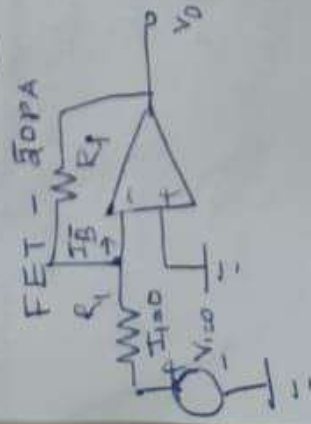
$$I_B = \frac{I_B^+ + I_B^-}{2} \quad (\text{Manufacturers specify the average of } I_B)$$



If V_i is set at 0V

then $V_0 = 0V$


instead we find o/p voltage is off set by

$$V_0 = (I_B^-) R_f$$

$$\text{For 741 } V_0 = (50 \text{ nA}) \times 1 \text{ M}\Omega = 500 \text{ mV}$$

→ Not acceptable

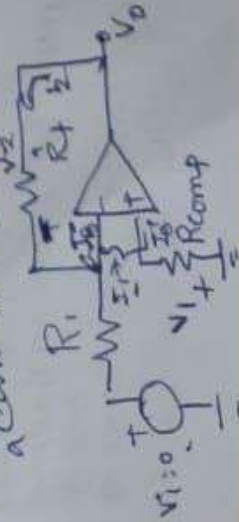This effect can be compensated by R_{comp}



Current I_B^+ flowing through R_{comp} develops V_i across

By KVL,

$$-V_1 + 0 + V_2 - V_0 = 0; V_0 = V_2 - V_1$$

By selecting proper value of R_{comp}

V_2 can be cancelled with $V_1 \times$

V_0 will be zero.

$$V_1 = I_B^+ R_{comp}$$

$$I_B^+ = \frac{V_1}{R_{comp}}$$

The node 'a' is at voltage $(-V_1)$ due to voltage at non-inverting I/P terminal is $(-V_1)$
 So with $V_1 = 0$

$$I_1 = \frac{V_1}{R_1}$$

$$I_2 = \frac{V_2}{R_f}$$

For compensation V_0 should be zero for $V_1 = 0$

$$\therefore V_0 = V_2 - V_1 \therefore V_2 = V_1$$

$$I_2 = V_1 / R_f$$

KCL at 'a' gives

$$I_B^- = I_2 + I_1 = \frac{V_1}{R_f} + \frac{V_1}{R_1} \\ = V_1 \left(\frac{1}{R_f} + \frac{1}{R_1} \right) / R_{comp}$$

Assuming $\underline{I_B} = I_B^+$ for bias current compensation

$$V_1 \times \frac{(R_{FE})}{R_1 R_4} = \frac{V_1}{R_{comp}}$$

$$R_{comp} = \frac{R_1 R_4}{R_1 + R_4} = R_1 || R_4$$

I/p offset current

Bias current compensation will work if both bias currents I_B^+ & I_B^- are equal

∵ I/p transistors are not identical, hence will be small difference b/w I_B^+ & I_B^-

This difference is called offset current I_{os}

$$|I_{os}| = I_B^+ - I_B^-$$

One way to predict which I_B is will be larger

I_{os} for BJT - 200nA

FET - 10 pA

Offset current will produce an o/p voltage when

I/p voltage $V_1 = 0$

$$V_1 = I_B^+ R_{comp}$$

$$I_1 = V_1 / R_1$$

KCL at node 'a'

$$I_2 = (I_B^- - I_1) = I_B^- - \left(I_B^+ \frac{R_{comp}}{R_1} \right)$$

$$V_o = I_2 R_3 - V_1 = I_2 R_4 - I_B^+ R_{comp}$$

$$= (I_B^- - (I_B^+ \frac{R_{comp}}{R_1})) R_4 - I_B^+ R_{comp}$$

$$\text{Substituting } R_{comp} = R_1 || R_4 \times$$

Amplification


$$V_o = R_4 (I_B^- - I_B^+)$$

$$V_o = R_4 I_{os}$$

T-feedback network is a good solution

I/p offset voltage

V_{os} can be applied to make o/p zero

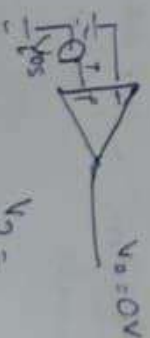

$$V_2 =$$

$$\text{If } V_1 = 0$$

$$V_2 = \left(\frac{R_1}{R_1 + R_4} \right) V_o$$

$$V_o = \left(\frac{R_1 + R_4}{R_1} \right) V_2$$

$$= (1 + R_4/R_1) V_2$$


$$V_{os} = |V_1 - V_2| \text{ at } V_1 = 0$$

$$V_{os} = |V_1 - V_2| \text{ at } V_1 = 0 \Rightarrow V_{os} = V_2$$

$$V_o \leq \left(1 + \frac{R_f}{R_1}\right) V_{ios}$$

DC Characteristics

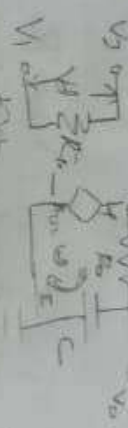- Ideally an op-amp should have infinite B.W
- If its open loop gain is 90dB, with dc signal its gain should remain 90dB through audio and on to high radio frequencies.



Op-amp applications:-

Scale changer / Inverter

Summing amplifier:-

- Op-amp may be used to design a CR where O/P is sum of several I/P signals $V_o = \sum V_i$
- Such CR is Summer

Inverting Summing Amplifier

3 I/P Voltages V_1, V_2, V_3 with R_1, R_2, R_3 feedback resistors R_f

Assume ideal op-amp

$A_{OL} = \infty$ $R_1 = \infty$ $V_{P, \text{current}} = 0$, No

Voltage drop across R_{comp} , non-inverting I/P terminal is grounded

V_{O1} at node 'a' is zero, as non-inverting terminal is grounded

$$\frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3} + \frac{V_o}{R_f} = 0$$



$$V_o = - \left(\frac{R_f}{R_1} V_1 + \frac{R_f}{R_2} V_2 + \frac{R_f}{R_3} V_3 \right)$$

O/P is an inverted, weighted sum of I/Ps

If $R_1 = R_2 = R_3 = R_f$

$$V_o = -(V_1 + V_2 + V_3)$$

V_o - inverted sum of 1/3 I/P signals

We may also set $R_1 = R_2 = R_3 = 3R_f$


$$V_o = - \left(\frac{V_1 + V_2 + V_3}{3} \right)$$

In practical CR

$$R_{comp} = R_1 \parallel R_2 \parallel R_3 \parallel R_f$$

Non-Inverting Summer

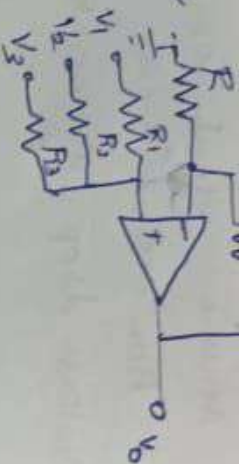A Summer that gives non-inverting summing amplifier,



also +, -1/p terminal - V_a

$$\frac{V_1 - V_a}{R_1} + \frac{V_2 - V_a}{R_2} + \frac{V_3 - V_a}{R_3} = 0$$

from which we have

$$V_a = \frac{\frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3}}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}}$$

Op-amp and 2 resistors R_f and R_i constitute a non-inverting amplifier

$$V_0 = \left(1 + \frac{R_f}{R_i}\right) V_a$$


Therefore the o/p voltage

$$V_0 = \left(1 + \frac{R_f}{R_i}\right) \left(\frac{\frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3}}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}} \right)$$

Non-inverting weighted sum of I/Ps

Subtractor

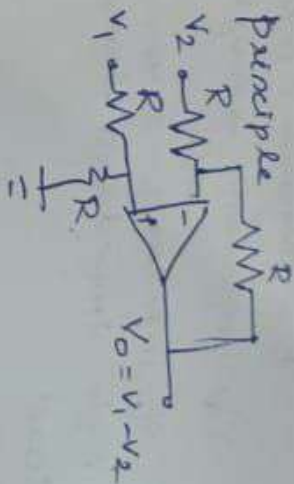If all resistors are equal in value then O/p voltage can be derived by superposition



To find V_{01} due to V_1 alone
make $V_2 = 0$

Then the ckt becomes non-inverting amplifier having I/P voltage $V_1/2$ at the non-inverting I/P terminal & the o/p becomes

$$V_{01} = \frac{V_1}{2} \left(1 + \frac{R}{R}\right) = V_1 \Rightarrow$$


$$V_{02} = -V_2$$

O/p voltage V_0 due to both I/Ps

$$V_0 = V_{01} + V_{02} = V_1 - V_2$$

Differential amplifier
Integrator
Differentiator
I/Ps V_1, V_2

Voltage follower

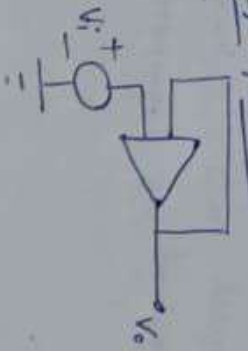

$$R_f = 0 \quad R_i = \infty$$

$$V_o = V_i$$

O/P voltage = I/P voltage
both magnitude & phase

I/P impedance is very high
MSD

O/P impedance = zero

used to connect high impedance sources to low impedance load.

Instrumentation amplifier

Measurement of a control of temperature, humidity, light intensity, vibrations etc. \rightarrow measured using transducers

O/P of transducer is amplified so that it can drive the indicator/display system. This is done by an instrumentation amplifier.

Features


- 1) High gain accuracy
- 2) High CMRR
- 3) High gain stability with low temp. coefficient
- 4) Low dc offset
- 5) Low O/P impedance

Requirements

MA 725 - Special Op-amp to meet stated

Single chip IC available - AD521, AD524

AD600, AD605, LM363 etc

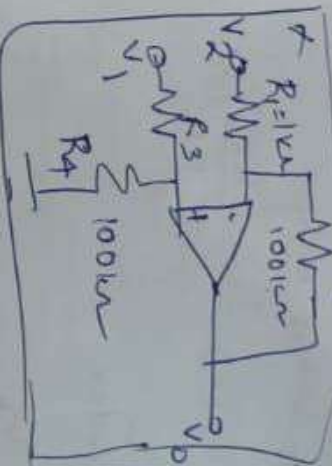

$$V_o = -\frac{R_2}{R_1} V_2 + \frac{1}{1 + \frac{R_2}{R_1}} V_1 \left(1 + \frac{R_2}{R_1}\right)$$

$$(V^+ = \frac{R_4}{R_3 + R_4} V_1)$$

$$V_1 = V_x, V_2 = V_y$$

$$\frac{V_x - V_y}{R_2} = \frac{V_x - V_y}{R_3} \Rightarrow V_o = \frac{R_2}{R_3} (V_x - V_y)$$

From (1)


$$\frac{V_x - V_y}{R_3} = \frac{V_y - V_x}{R_2}$$

$$V_b = V_y - \frac{R_2}{R_3} (V_x - V_y)$$

$$V_o = \frac{R_4}{R_1} (V_b - V_a)$$

$$= \frac{R_4}{R_1} \left\{ V_y - V_x - \frac{R_2}{R_3} (V_x - V_y) \right\}$$
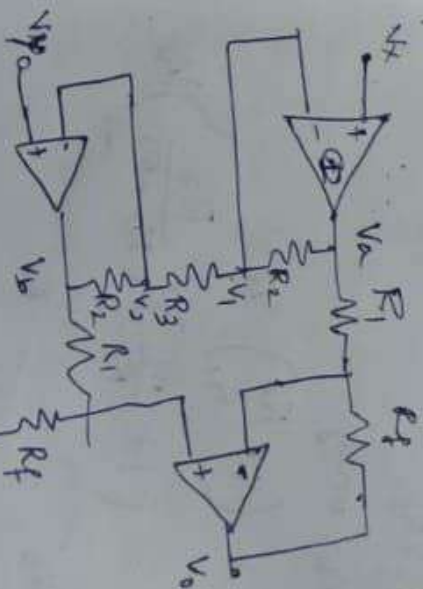
$$V_o = -\frac{R_4}{R_1} \left(1 + \frac{R_2}{R_3}\right) \frac{R_2}{R_1} (V_x - V_y)$$




$$V_1 = V_x$$

$$V_2 = V_y$$

$$\frac{V_a - V_1}{R_2} = \frac{V_1 - V_2}{R_3} \quad (1)$$

$$\frac{V_1 - V_2}{R_3} = \frac{V_2 - V_1}{R_2} \quad (2)$$

Differential amplifier

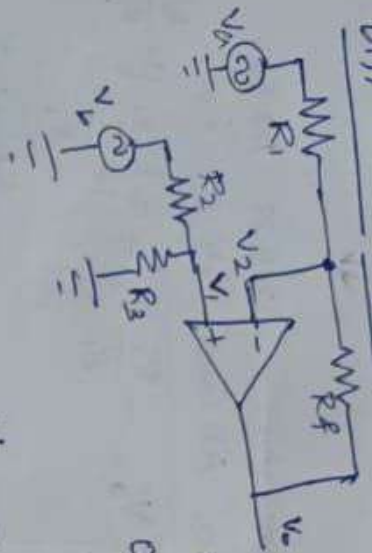

2 I/Ps superposition theorem can be used to find O/P voltages

When $V_b = 0$; inverting O/P due to V_a only

$$V_0(a) = -\left(\frac{R_f}{R_1}\right) V_a$$

Similarly when $V_a = 0$ - non-inverting divider

$$V_1 = \frac{R_3}{R_2 + R_3} V_b$$

O/P due to V_b only

$$V_0(b) = \left(1 + \frac{R_f}{R_1}\right) V_1 = \left(1 + \frac{R_f}{R_1}\right) \left(\frac{R_3}{R_2 + R_3}\right) V_b$$


If $R_1 = R_2$ & $R_f = R_3$

$$V_0(b) = \left(\frac{R_1 + R_f}{R_1}\right) \left(\frac{R_3}{R_2 + R_3}\right) V_b = \left(\frac{R_2 + R_f}{R_1}\right) \left(\frac{R_f}{R_2 + R_f}\right) V_b = \left(\frac{R_f}{R_1}\right) V_b$$

∴ total voltage

$$V_0 = V_0(a) + V_0(b)$$

$$= \frac{R_f}{R_1} (-V_a + V_b)$$

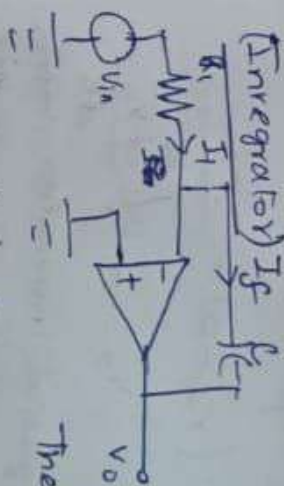

There is feedback element is capacitor

current is zero $V_2 = V_1 = 0$

Therefore $i_1 = i_f$ & $V_2 = V_1 = 0$

$$i_1 = \frac{dQ}{dt} = C_f \frac{dV_0}{dt} = -\int_0^t \frac{V_1}{R_1} dt = -C_f \int_0^t \frac{V_{in}}{R_1} dt$$

$$= -C_f V_{out}$$

$$V_{out} = -\frac{1}{R_1 C_f} \int_0^t V_{in} dt$$



Integrating both sides with respect to time from 0 to t

I/P is sine wave

O/P is cosine wave



Differentiator

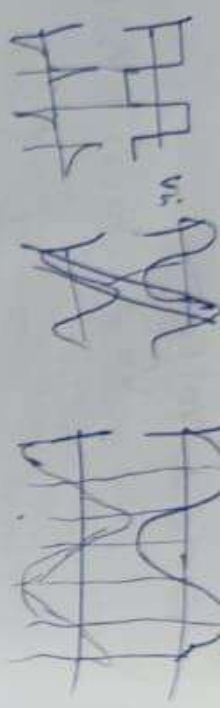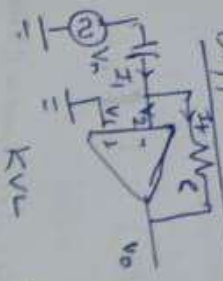


$\therefore \frac{d(V_1 - V_2)}{dt} = \frac{d(V_1 - 0)}{dt} = \frac{dV_1}{dt}$
 $\therefore \frac{d(V_1 - V_2)}{dt} = \frac{dV_1}{dt}$
 $\therefore \frac{d(V_1 - V_2)}{dt} = \frac{dV_1}{dt}$

$V_0 - R C$ times negative increment voltage
 Rate of change of I/P voltage V_{in} with t
 Positive wave I/P produces V_{out} of

I/P signal will be differentiated properly if no
 time period T of the I/P signal is larger
 than or equal to $R C$ $T \geq R C$

As freq changes gain changes Also as higher
 freq \therefore \therefore susceptible at high freq
 noise gets amplified

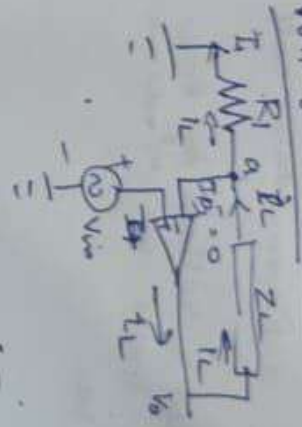Voltage to current converter (transconductance)




$V_0 = I_L R_L$ (as $I_B = 0$)

$I_L = \frac{V_i}{R_1}$

I/P voltage V_i is
 converted to V_i/R_1
 o/p current

$I_1 + I_2 = I_L$

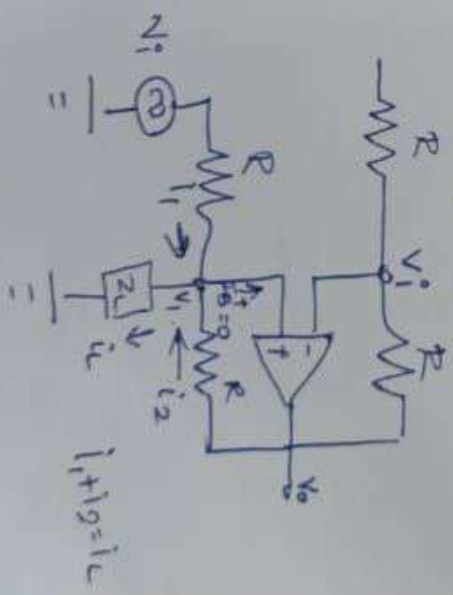

$\frac{V_i - V_0}{R} + \frac{V_0 - V_i}{R} = I_L$
 $V_i + V_0 - 2V_0 = I_L R$

$V_1 = \frac{V_i - V_0 - I_L R}{2}$

Since op-amp is in
 non-inverting mode

Gain $1 + \frac{R_f}{R_i} = 2$

o/p voltage $V_0 = 2V_1$

$V_0 = V_i + V_0 - I_L R$

$V_i = I_L R_1$

$V_i = I_L R_1$

$I_L = V_i / R$

$V_1 = \frac{V_i - V_0 - I_L R}{2}$

$2V_1 = V_i - V_0 - I_L R$

$2V_1 - 2V_1 = V_i - I_L R$

$V_i - I_L R = 0$

$V_i = I_L R$

$I_L = V_i / R$